
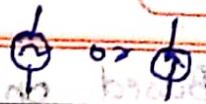


Energy Sources

Independent

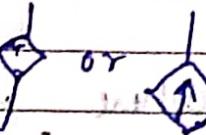


Dependent




or




VCVS

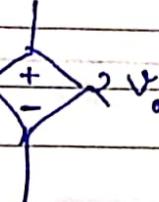


CCVS

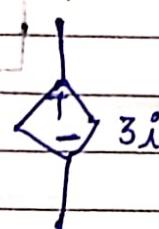

VCCS

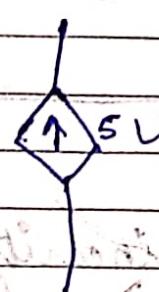

CCCS

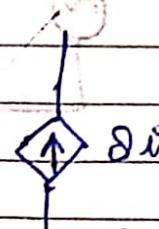

Energy Sources Classification -

Network Classification

1.) Based on direction of Current.

Unilateral

circuits connected
with diode

Bilateral

circuits connected
with R, L & C,

2.) Based on separability.

Lumped

(circuits which
are not distributed.
particular value of R, L & C is given)



Distributed.

↳ [R, L & C, e.g., transmission
are connected
throughout length of
the circuit]

3. Based on presence or absence of source.

the circuit where
energy source Active
is present

Passive. energy source
is not present

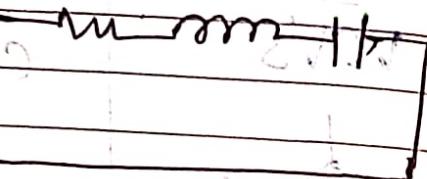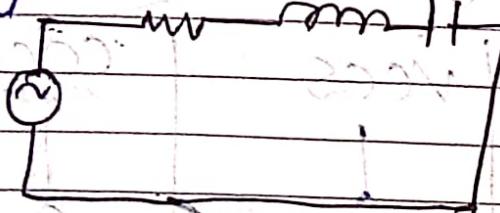

4. Based on linearity.

Linear

Non Linear

• principle of \propto

homogeneity &

principle of
Superposition

followed. Linearity Test sign's

$$\textcircled{1} \quad F(x_1 + x_2) = F(x_1) + F(x_2).$$


$$\textcircled{2} \quad F(ax) = aF(x)$$

Source Transformation -

Voltage Source can be converted into Current Source







\downarrow
with
series






Current Source
with
Parallel







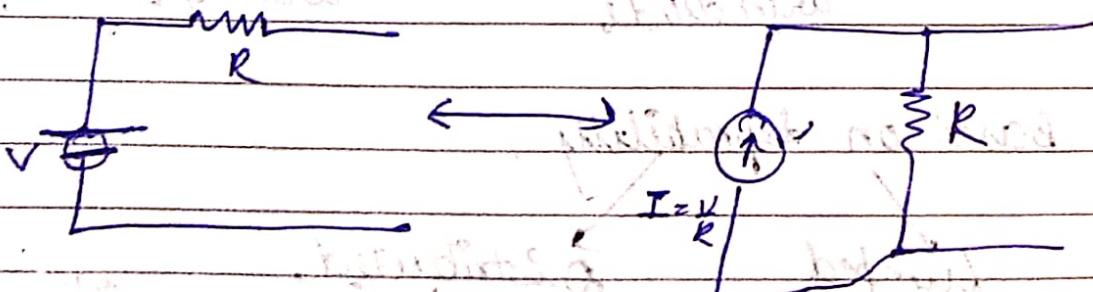



7.5

PAGE No:
DATE: / / 201

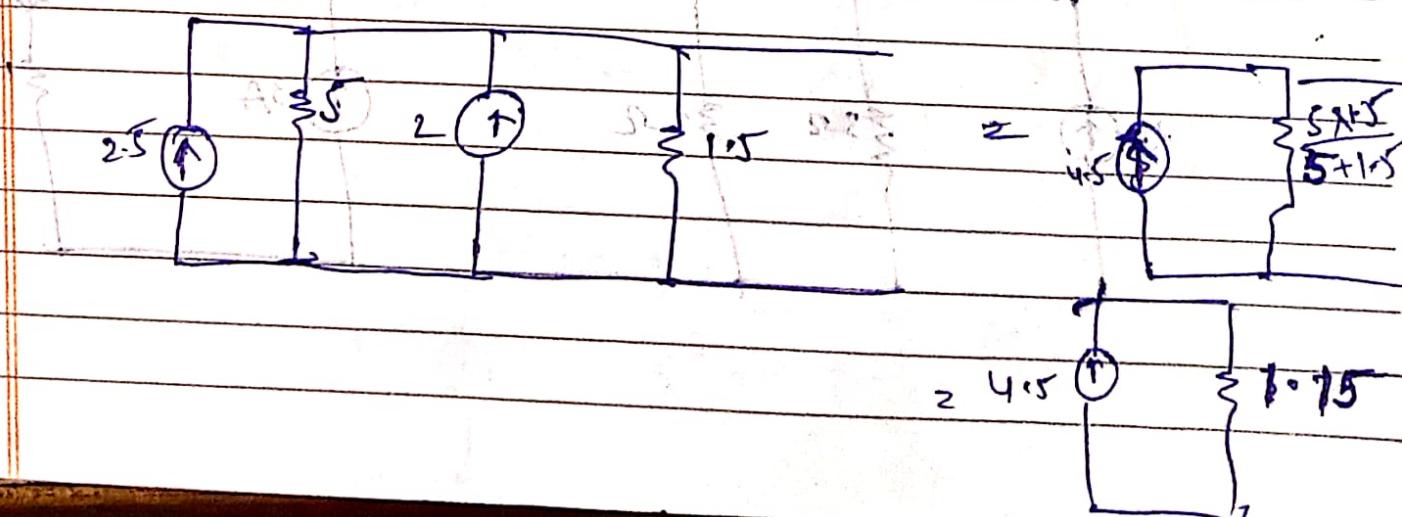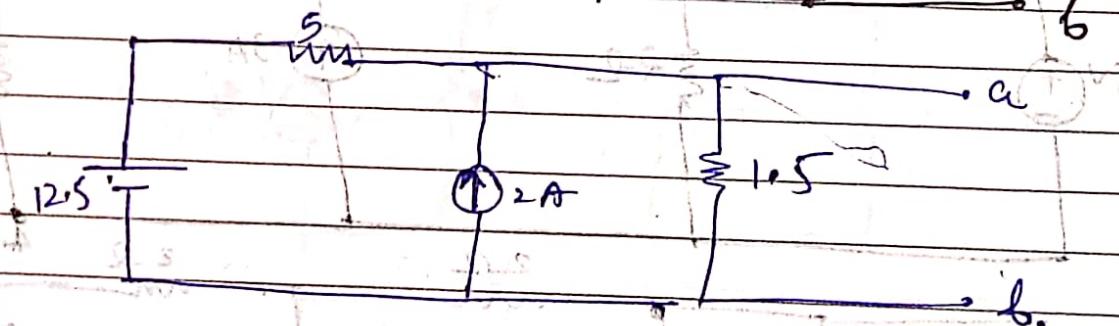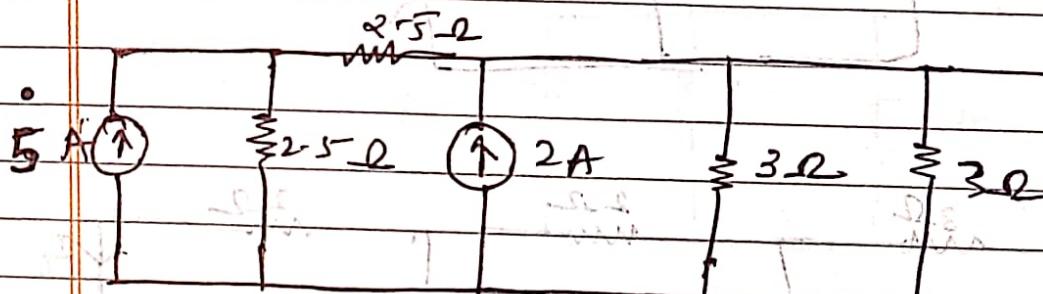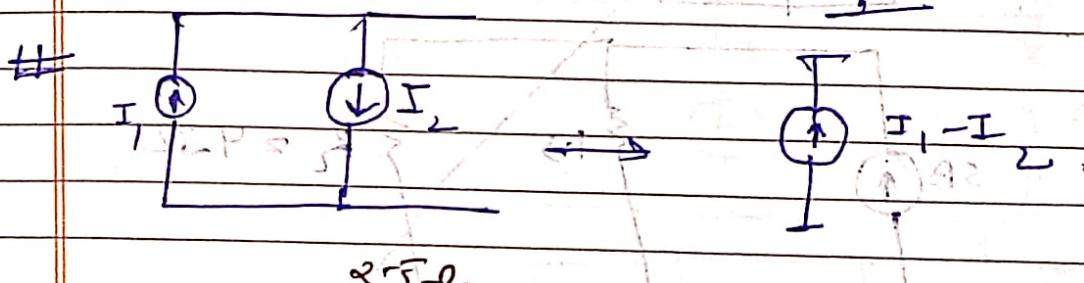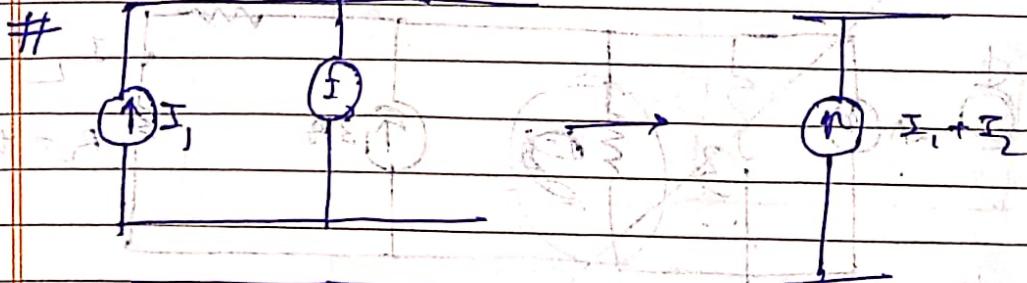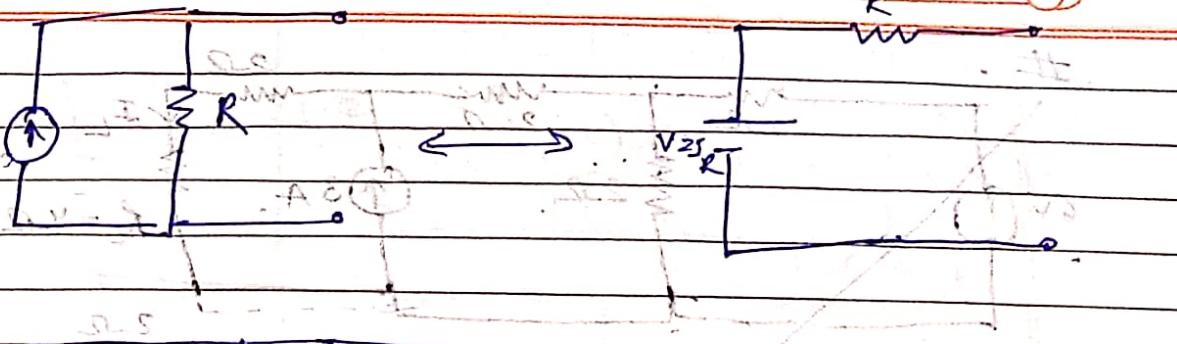

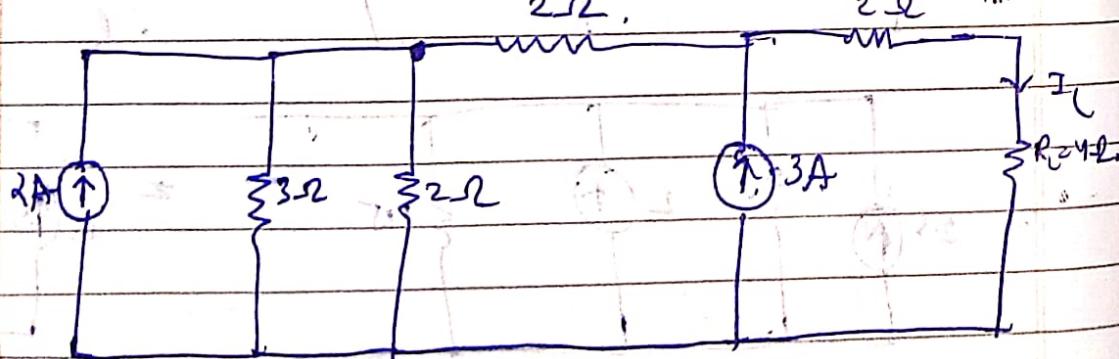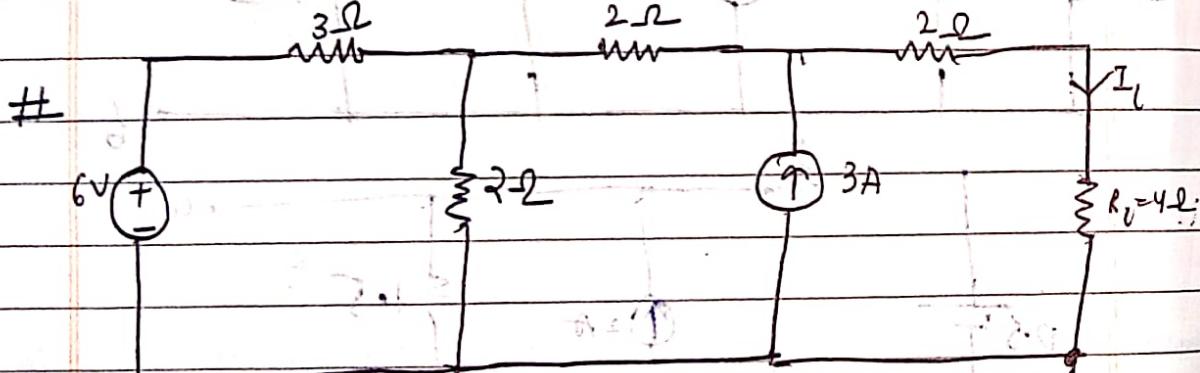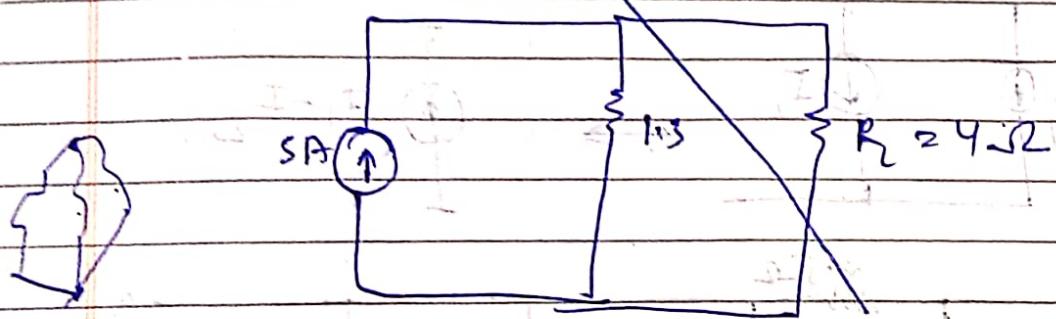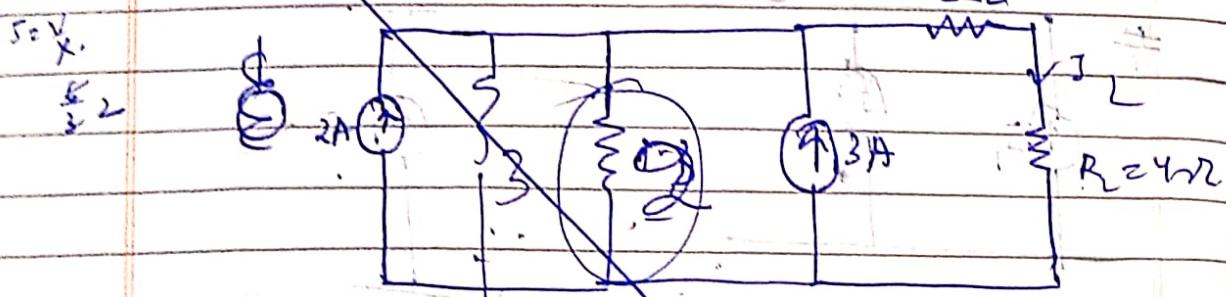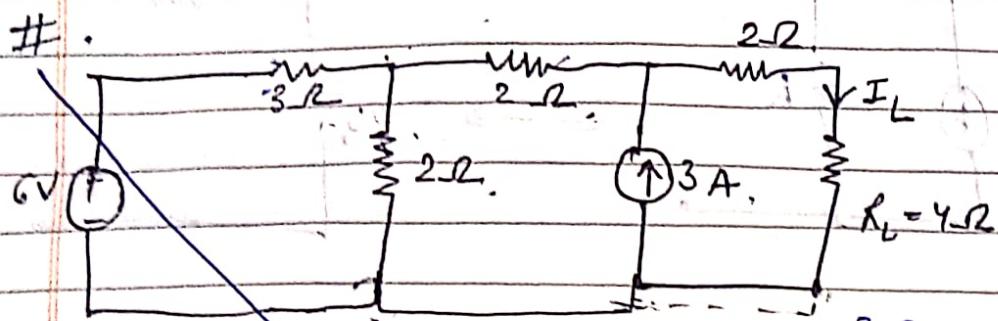

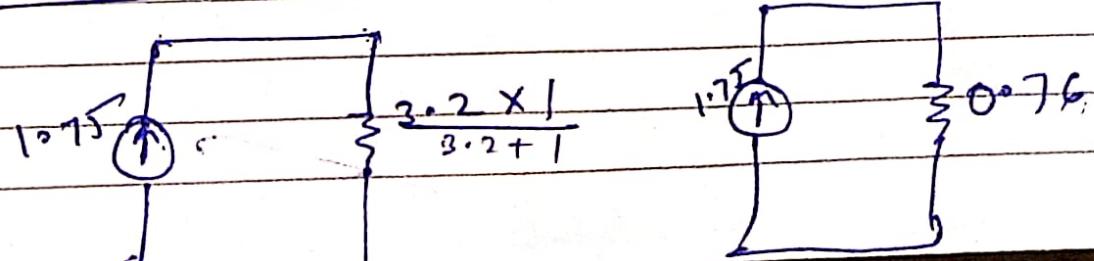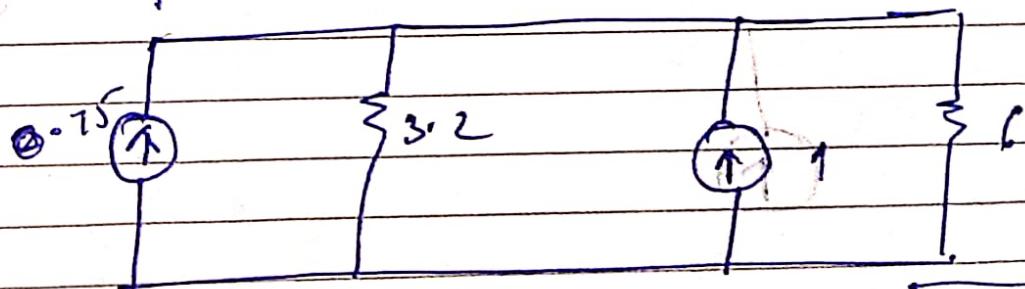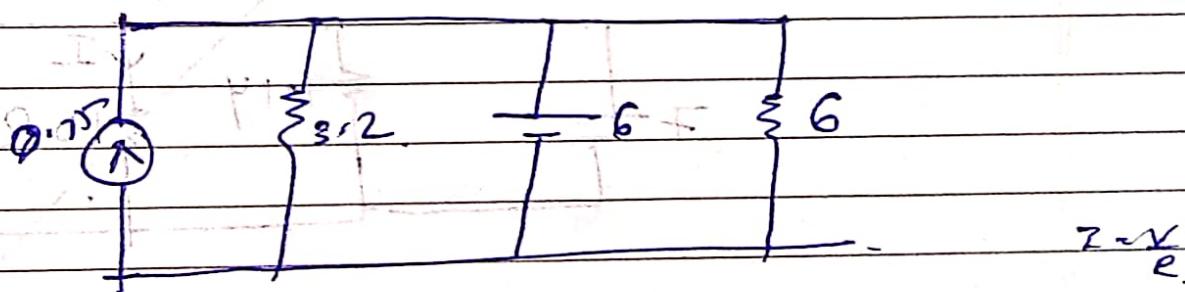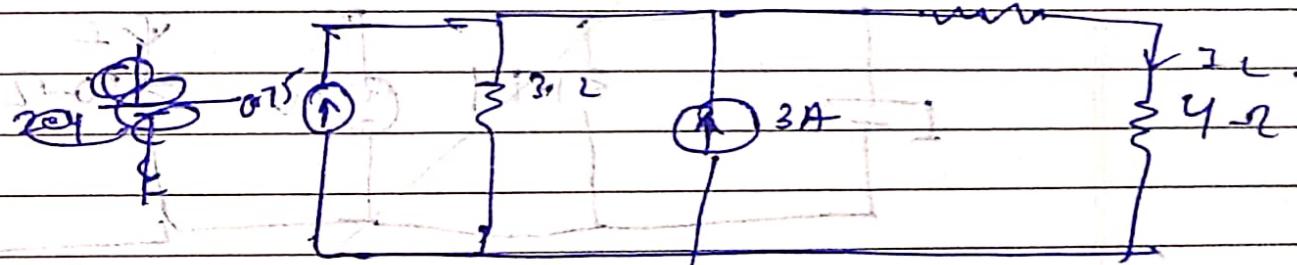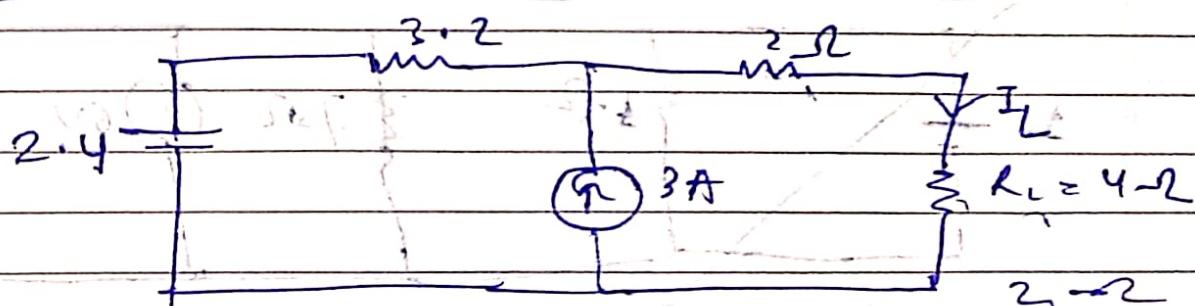
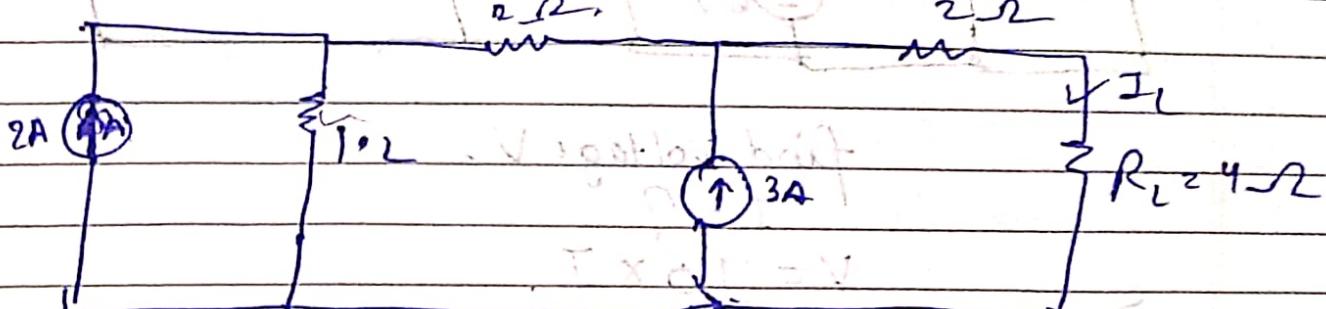
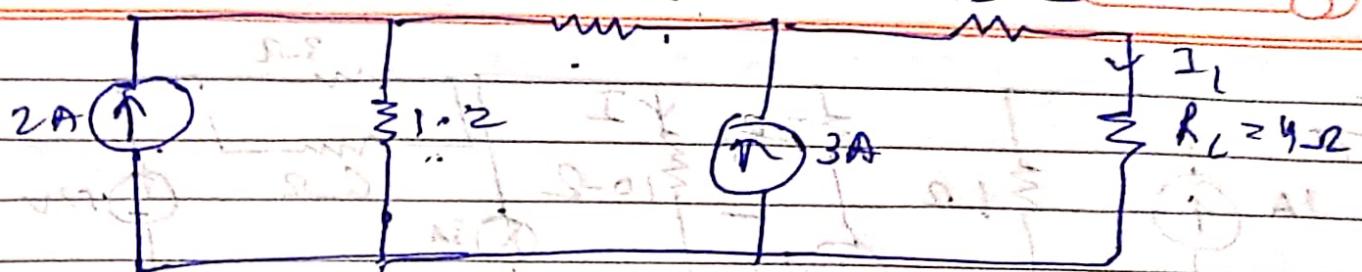


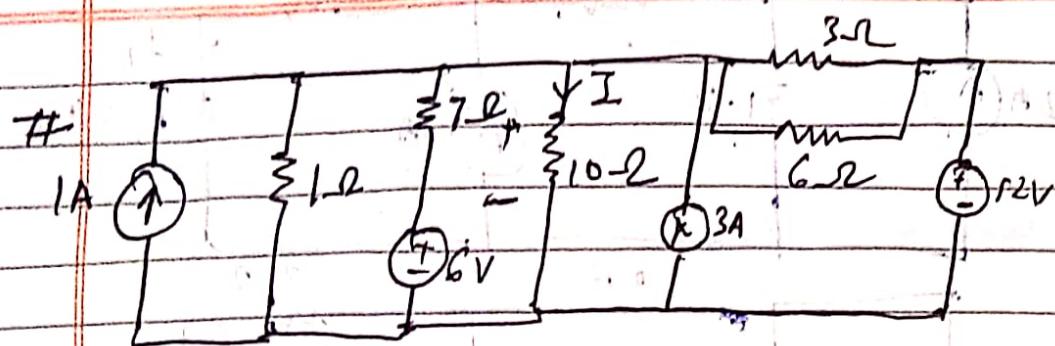

find voltage V .



$$I = ?$$

$$V = 10 \times I$$

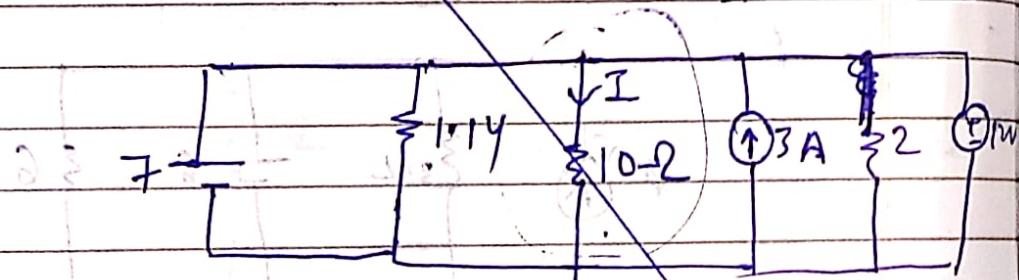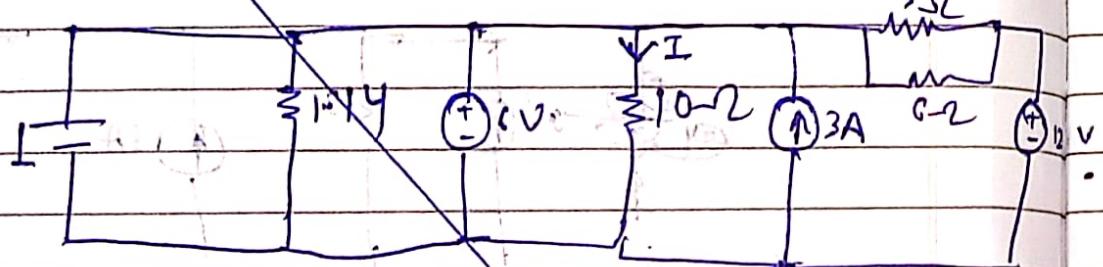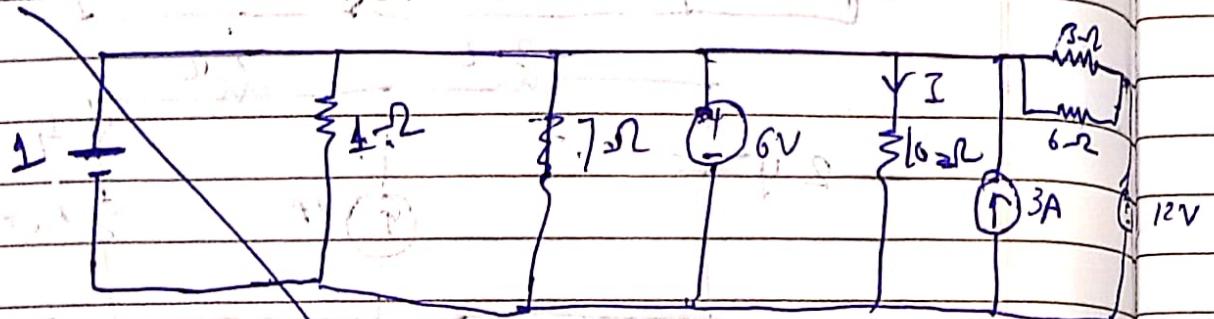

6.23V

12

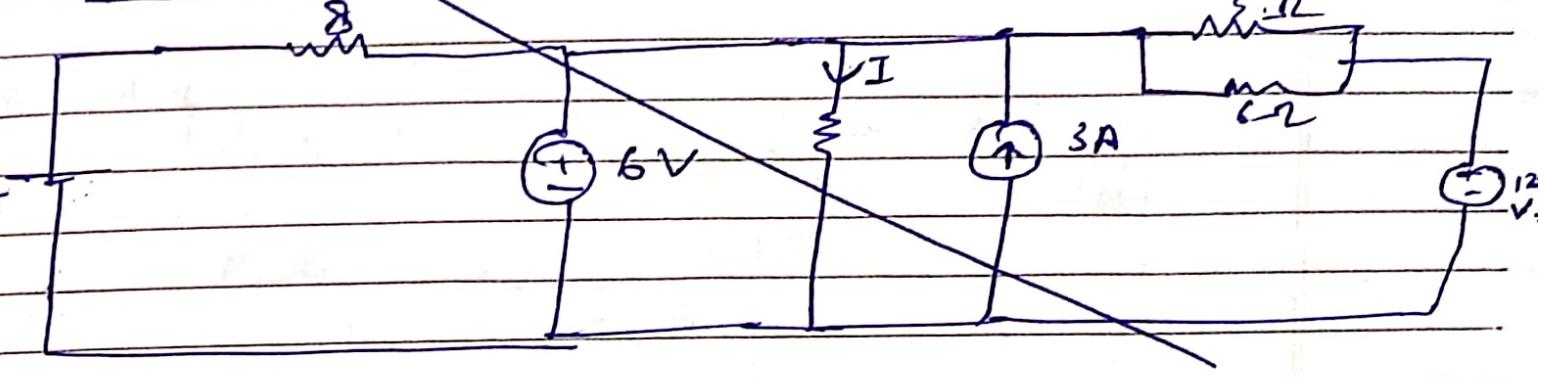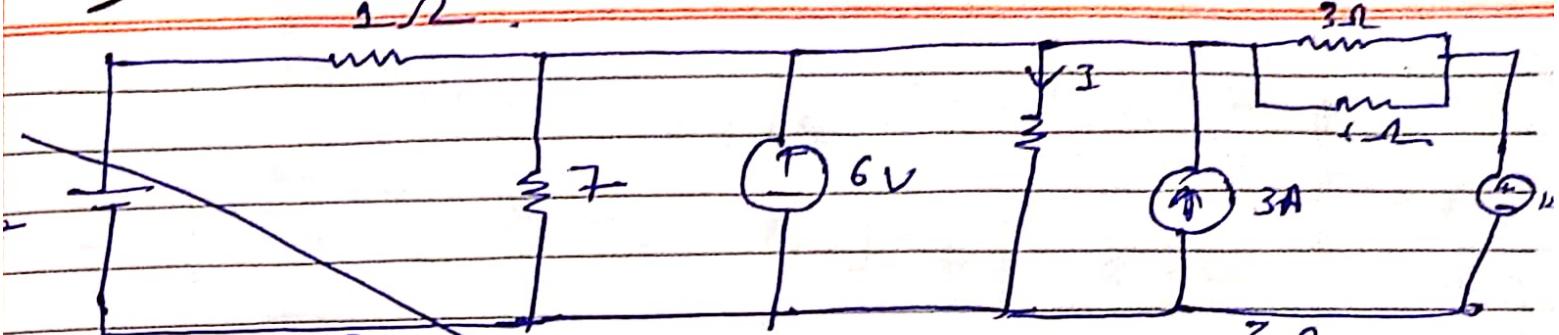

4

$$\begin{aligned} & \text{--- } \begin{array}{c} \text{mR} \\ \text{mB} \end{array} \quad Z = R + jX_L \quad E = a + jb \rightarrow ELO. \\ & \text{--- } \begin{array}{c} jX_C \\ + \end{array} \quad Z = R - jX_C \quad R \rightarrow p \\ & \text{--- } \begin{array}{c} \text{m} \\ \text{m} \end{array} \quad R \leftarrow E \cos \theta + jE \sin \theta \end{aligned}$$

final ans

J
has to be
in
polar
form.

$$\text{Ansatz: } \underline{\text{Rec}} \quad E_1 = 3 + j4 \rightarrow 5 \angle 53^\circ \text{ Polar.}$$

\downarrow Pal $\text{pal}(3,4)$

z 5

KCL

$$\tan(53^\circ - 13^\circ),$$

$$\text{Acc}(5, 53, 13) \rightarrow 3 \rightarrow \text{real}$$

RLC tank \rightarrow $3.99 \approx 4$ rings.

add, subtract \rightarrow Rec.
multiply + divide \rightarrow Poly.

$$2 + 5j + 6 + 1j = 8 + 6j$$


$$4 + 3j - (2 + 1j) = 2 + 2j$$

$$4(56) \times 2(10) = 860$$

$$\frac{4(50)}{910} = 2(46)$$

$$(2b-a^2)(a_1-a_2) = -48$$




$$(3173) + (365)$$

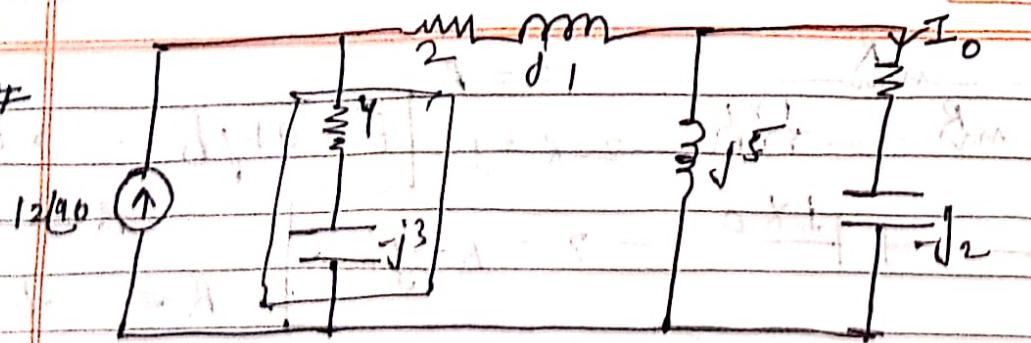

$$I_0 = ?$$

$$\text{Imp. } Z = 4 - j3$$

$$\text{Pol}(4,3) = 57 - 36.86^\circ$$

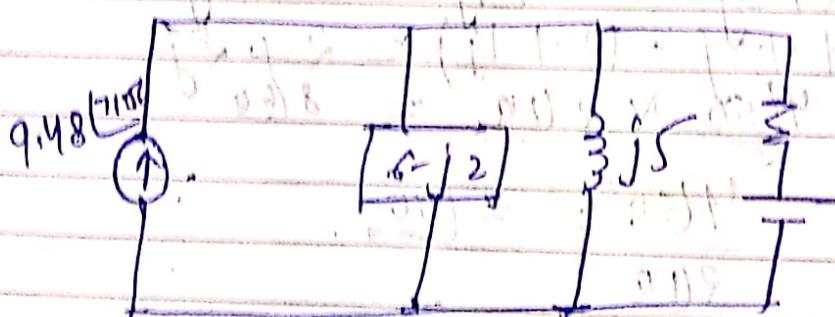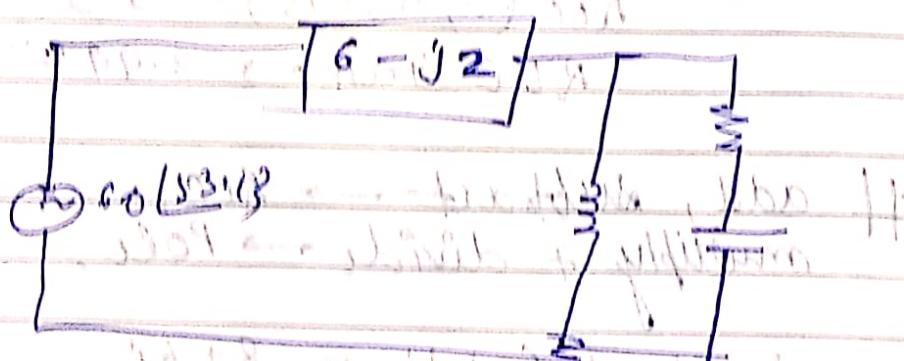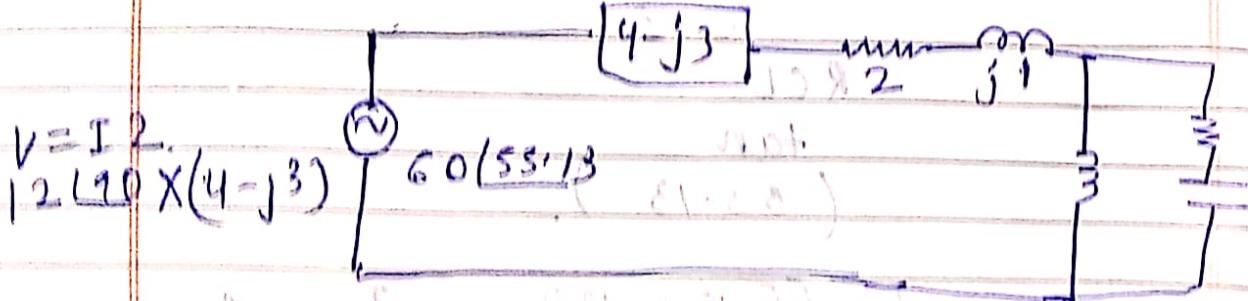

$$Z = \frac{2+j2}{2+j2} (6-j2) \parallel (0+j5)$$

$$\frac{(6-j2)(0+j5)}{(6-j2)+(0+j5)}$$

$$6.32 - 18.4$$

$$= 5$$

12 (90)

PAGE NO. 12
DATE: / / 201

$$\underline{6.32} - 18.4 \cdot 5 (90)$$

$$\underline{6.32} - 18.4 + 5 (90)$$

$$\underline{\underline{31.6}} - 71.6$$

$$\underline{\underline{11.32}} - 71.6$$


$$= (6 - j2) (0 + j5) \\ (6 + j3)$$

$$= \underline{6.32} - 18.4 \cdot 5 (90) \\ \underline{\underline{6.32}} \cdot 3 (90)$$

$$= \underline{\underline{31.6}} - 71.6 \\ 3 (90)$$

$$= 10.5 - 18.4.$$

$$= 21.1.$$

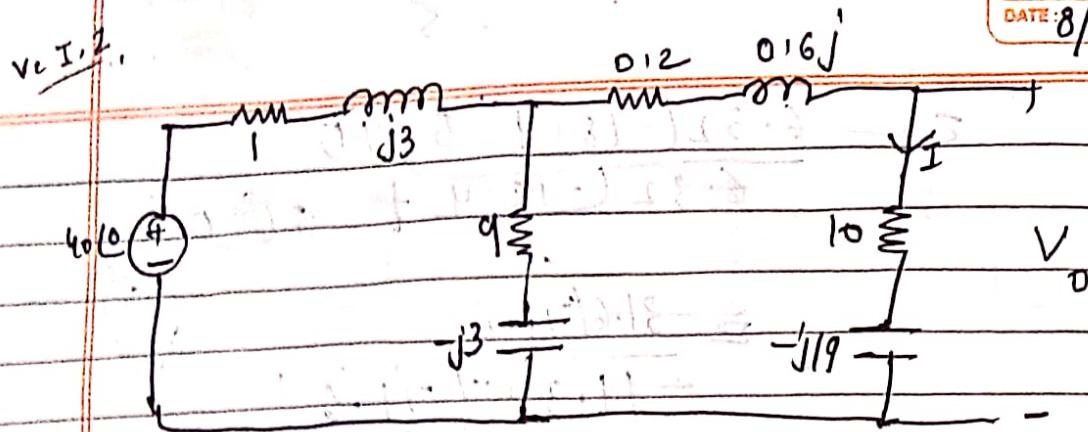

Find $V_0 = I(10, -j19)$.

Ans

$$(20 + j0) (10 - j2) = 14.74 \angle -27.0^\circ$$

$$10(10 - j2) - 20(1 + j0) =$$


$$20(1 + j0) - 20(1 + j2)$$

$$-j15 \text{ A} \times 10 =$$

$$-j150$$

$$P = 1(-j150) =$$

$$1.125$$

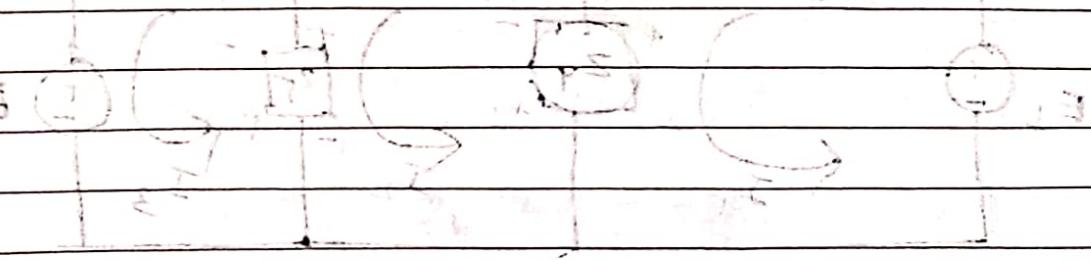

\rightarrow I, II, III strains have same max A

$$\textcircled{1} \rightarrow O = (I - F) p E + (F - I) p E -$$

$$\Rightarrow (I - F) p E - E_0 E + (F - I) p E -$$

$$O = p F - p E = (I - p F) p E -$$

$$\Rightarrow p F = p E \Rightarrow F = E$$

$$= p E$$

$$F = p E$$

$$I = p F$$

$$I = p^2 E$$

$$\therefore I = p^2 E \times p E = p^3 E = p E$$

$$\therefore I = p E \times p E = p^2 E$$

Contrafactual


$$I = p^2 E$$

$$[I] = [p^2 E]$$

- Cramer's rule, will use.

(Ref)

- Mesh Analysis - find branch currents.

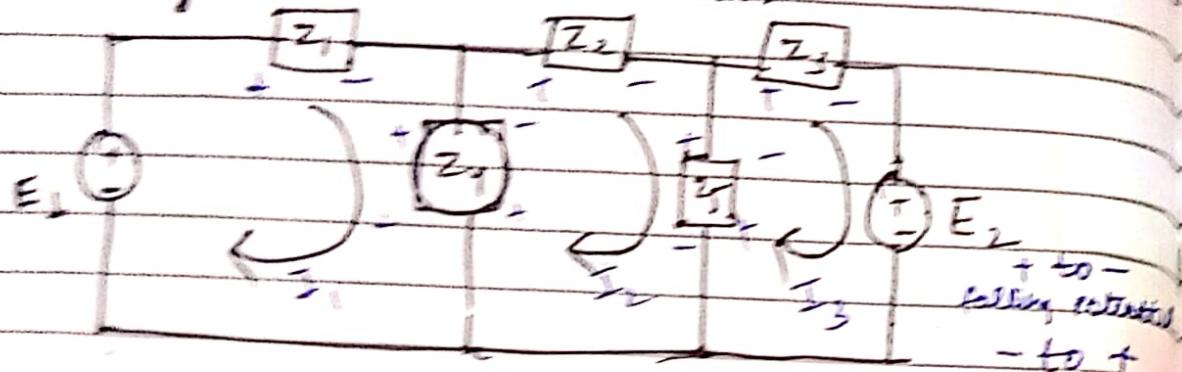

Leave tree mesh currents I_1, I_2, I_3 . positive potential

$$E_1 - I_1 Z_1 - Z_3 (I_1 - I_2) = 0, \quad \text{--- (1)}$$

Node 2,

$$-Z_1 (I_2 - I_1) - Z_2 I_2 - Z_3 (I_2 - I_3) = 0.$$

Node 3,

$$-Z_3 (I_3 - I_2) - Z_3 I_3 - E_3 = 0$$

$$I_1 =$$

$$I_2 =$$

$$I_3 =$$

$$I_{11} = I_1$$

$$I_{22} = I_2$$

$$I_{33} = I_3$$

$$I_{12} = I_1 - I_2 \text{ or } I_2 - I_1$$


$$I_{13} = I_1 - I_3 \text{ or } I_3 - I_1$$

(Main values)


$$IZ = E$$

$$[I][z] = [E]$$

\Rightarrow self & mutual inductances.

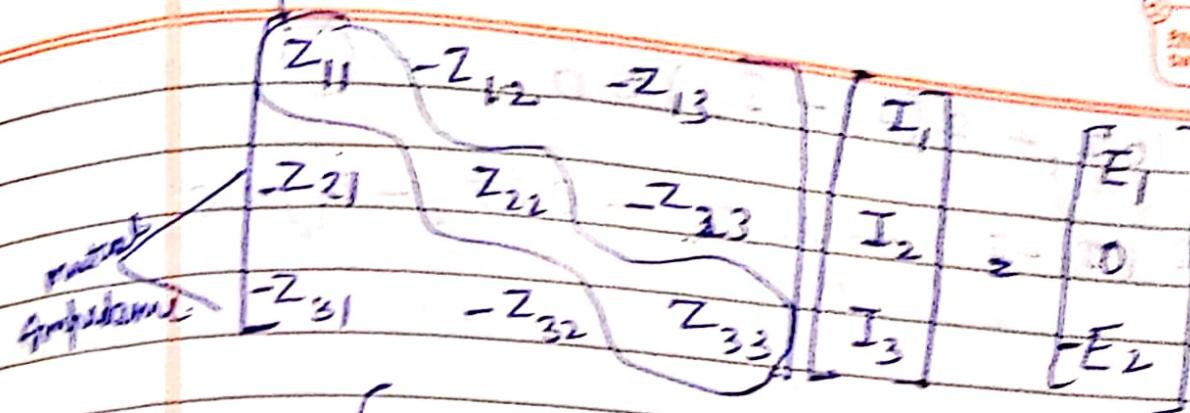

$$\begin{bmatrix} Z_{11} + Z_{24} & -Z_{24} & 0 \\ -Z_{24} & Z_{22} + Z_2 + Z_5 & -Z_5 \\ 0 & -Z_5 & Z_5 + Z_3 \end{bmatrix}$$

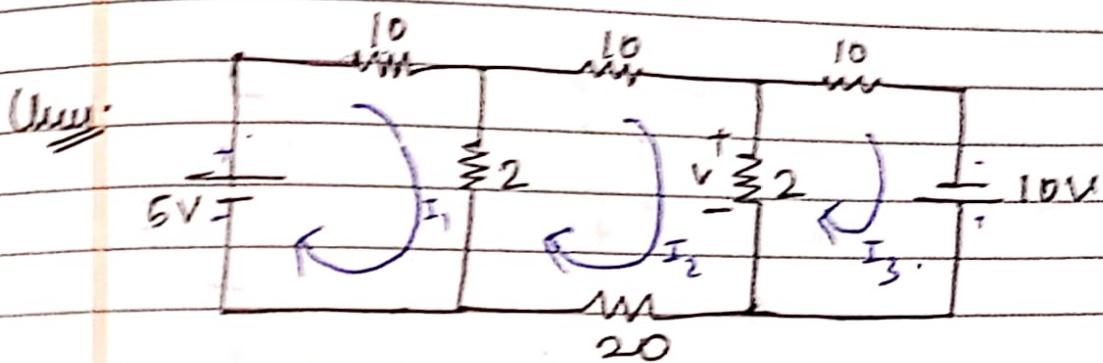

find V .

~~$$5 + 10I_1 + 2(I_1 - I_2) = 0 \quad \textcircled{1},$$~~

~~$$20I_2 + 3(I_2 - I_1) + 10I_2 - 2(I_2 - I_3) = 0 \quad \textcircled{ii}$$~~

~~$$2I_3 + 10I_3 + 10 = 0 \quad \textcircled{iii},$$~~

~~$$5 + 10I_1 + 2(I_1 - I_2) = 0$$~~


~~$$5 + 10I_1 + 2I_1 - 2I_2 = 0$$~~

~~$$5 + 12I_1 - 2I_2 = 0$$~~

$$5 - 10I_1 - 2(I_1 - I_2) = 0 \quad \text{--- (1)}$$

$$-2(I_2 - I_1) - 20I_2 - 2(I_2 - I_3) = 0$$

$$-2(I_3 - I_2) - 10I_3 + 10 = 0$$

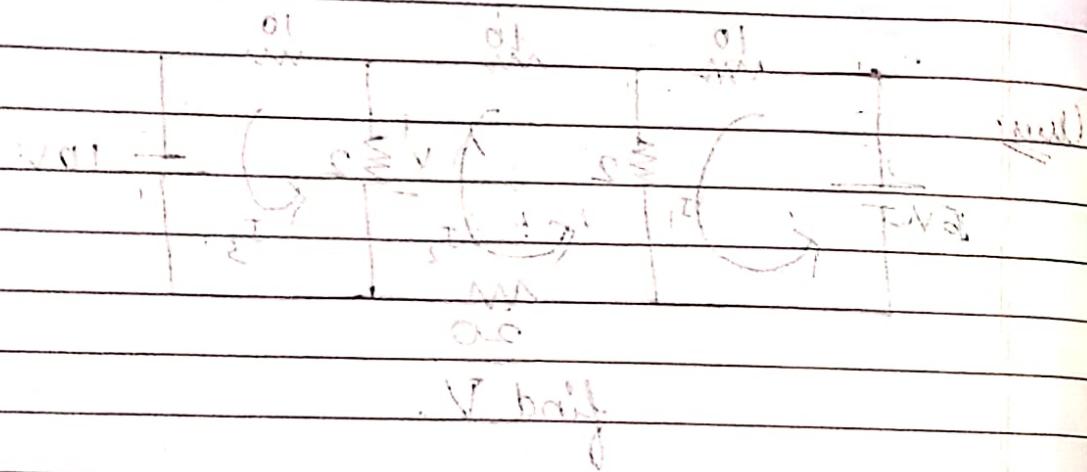

$$(1) \rightarrow 0 = (5 - 10I_1) - 10I_1$$

$$(2) \rightarrow 0 = (5 - 20I_2) - 20I_2$$

$$(3) \rightarrow 0 = 10I_3 - 10I_3$$

$$0 = (5 - 10I_1) - 10I_1$$

$$0 = 5 - 20I_2 - 20I_2$$

$$0 = 10I_3 - 10I_3$$


6.3 L5113

$(1+j2)$ $(3+j3)$

A_{21} $\frac{1}{j12}(1+j2)(3+j3)$

PAGE No. 1
DATE: 1/2021

#

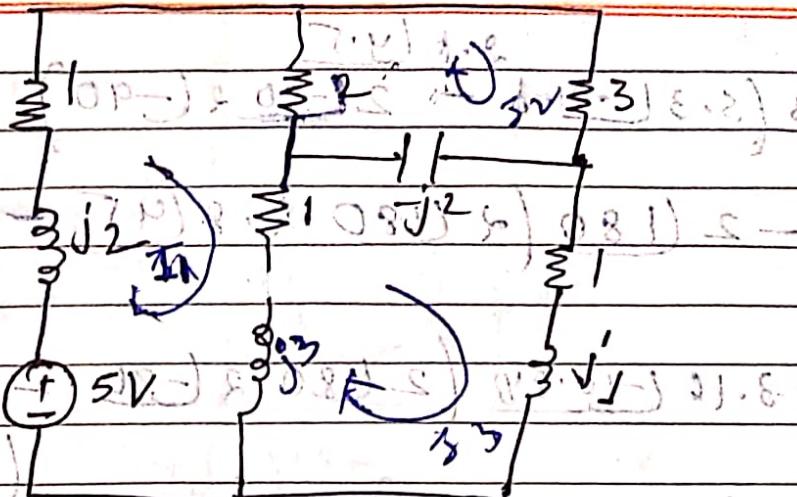

find Voltage across capacitor,

$$\begin{bmatrix} (1+j2)(3+j3) & -2(1-j2) \\ 0.81-j2 & 5-j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} -2 & -(-j2) \\ -(j_3+1) & -(-j2) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 4+j5 & -2 & -1-j3 \\ -2 & 5-j2 & -(-j2) \\ -(j_3+1) & -(-j2) & j_2+2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$= \left[4+j5 [(5-j2)(j_2+2) - (-j_2)] + 2 [-3(j_2+2) + ((j_2) + (j_3+1)) \right]$$

$$+ (-1-j3) [-2j2 + (5-j2)(j_3+1)] \right]$$

$$\begin{bmatrix} 6.3(5.113) & 2480 & 3.16 & 1.10843 \\ 2480 & 5.3(-21.8) & 2(-90) & 2.8(45) \\ -3.16 & 2(-90) & 2.8(45) & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{aligned}
 & \left[6.3 [51.3] (5.3 [21.8] - 2 [96.2] (-90)) \right. \\
 & \quad \left. - 2 [180] (2 [180] 2.8 [45] - 2 [90] \right. \\
 & \quad \left. + 3.16 [-10.84] (2 [180] 2 [-96] - 5.3 [21.8]) \right. \\
 & \quad \left. - [6.3 [51.3] (4 [92] - 1.96)] \right] \quad (-3.16 [18.4]) \\
 \Rightarrow & \left[6.3 [51.3] (14.84 [-17.3] - 4 [-180]) \right. \\
 & \quad \left. - 2 [180] (25.6 [225] - (6.32) (-7)) \right. \\
 & \quad \left. + 3.16 [-10.84] (4 [90] - 1.674 [40]) \right]
 \end{aligned}$$

$$\begin{aligned}
 2. \quad & \left[6.3 [51.3] (14.84 [-17.3] - 4 [-180]) \right. \\
 & \quad \left. - 2 [180] (25.6 [225] - (6.32) (-7)) \right. \\
 & \quad \left. + 3.16 [-10.84] (4 [90] - 1.674 [40]) \right]
 \end{aligned}$$

$$\frac{(a_1 - a_2)(b_1 - b_2)}{a_1 + a_2} = ? + \left[(a_1 - a_2) - (a_1 + a_2)(b_1 - b_2) \right] \quad (1)$$


$$\frac{(a_1 - a_2)(b_1 - b_2)}{a_1 + a_2} = ? + (b_1 - b_2)(a_1 - a_2) + \dots$$

$$\frac{(a_1 - a_2)(b_1 - b_2)}{a_1 + a_2} = ? + (b_1 - b_2)(a_1 - a_2) \quad (2)$$

$$\frac{(a_1 - a_2)(b_1 - b_2)}{a_1 + a_2} = ? + (b_1 - b_2)(a_1 - a_2) \quad (3)$$

$$\frac{(a_1 - a_2)(b_1 - b_2)}{a_1 + a_2} = ? + (b_1 - b_2)(a_1 - a_2) \quad (4)$$

3.32160
P04290199
DATE: 12/12/2018

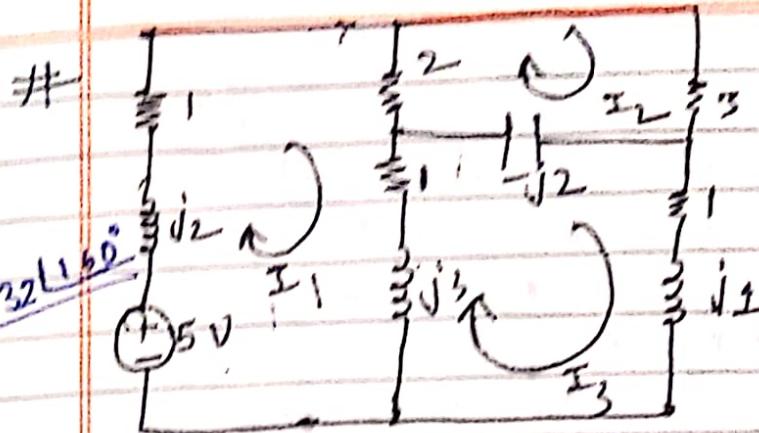


$$I_3 = \frac{\Delta_2}{\Delta} \quad \text{Ansatz}$$

$$\begin{bmatrix} (1+j2)(3+j3) & -2 & (-1-j3) \\ -2 & 5-j2 & -(j2) \\ -(j3+1) & -(j2) & j2+2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 4+j5 & -2 & -1-j3 \\ -2 & (5-j2) & -(j2) \\ -(j3+1) & -(j2) & j2+2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = [4+j5(5-j2)(j2+2) - (j2-j2)] + 2[-2(j2+2) - (j2+2) + j3+1] + (-1-j3)[-2(j2) - (5-j2)(-j3-1)]$$

=

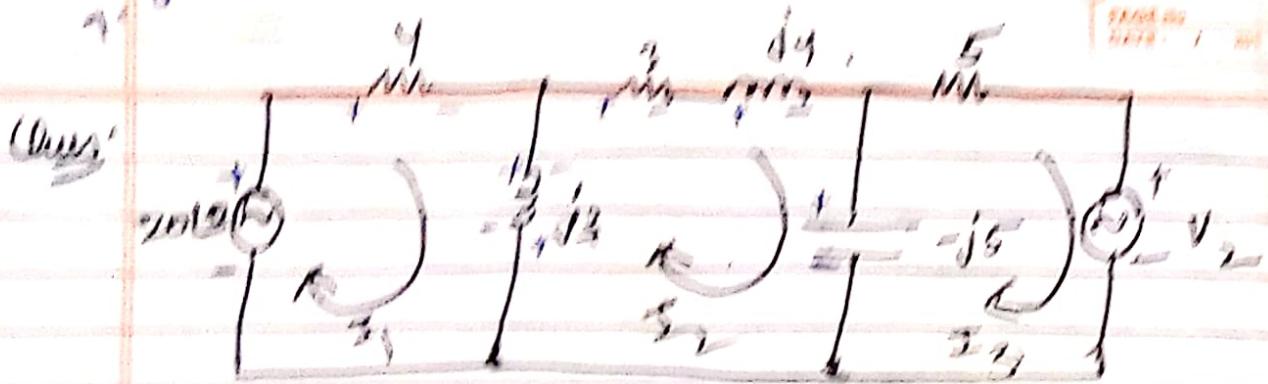

Determine value of V_2 such that current in $(3+j4)$ is zero using mesh analysis.

Mesh 1,

$$20I_0 - 4I_1 - j_3(I_1 - I_2) = 0 \quad \text{--- (1)}$$

Mesh 2,

$$-j_3(I_2 - I_1) - 3I_2 - j_4I_2 - (-j5)(I_2 - I_3) = 0 \quad \text{--- (2)}$$

$$-(j5)(I_3 - I_2) + 5I_3 - V_2 = 0 \quad \text{--- (3)}$$

OR

B_1

$$A_2 = \begin{bmatrix} 4+j3 & 20j & 0 \\ -j3 & 0 & j5 \\ 0 & -V_2 & 5-j5 \end{bmatrix}$$

$$= \begin{bmatrix} 4+j3 & 20 & 0 \\ -j3 & 0 & j5 \\ 0 & -V_2 & 5-j5 \end{bmatrix}$$

$$= [4+j3(0 + V_2 j5) - 20(-j3)(5-j5) - 0 + 0(-)]$$

$$= (4+j3)(V_2 j5) - 20(-j3)(5-j5)$$

$$= (1+3)(4+5) - 2 \cdot (-3 \cdot 3 + 15)$$

100
2010, 11

$$10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$


$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

$$= 10^2 + 2 \cdot 10 \cdot 3 + 3^2 = 100 + 60 + 9 = 169$$

707

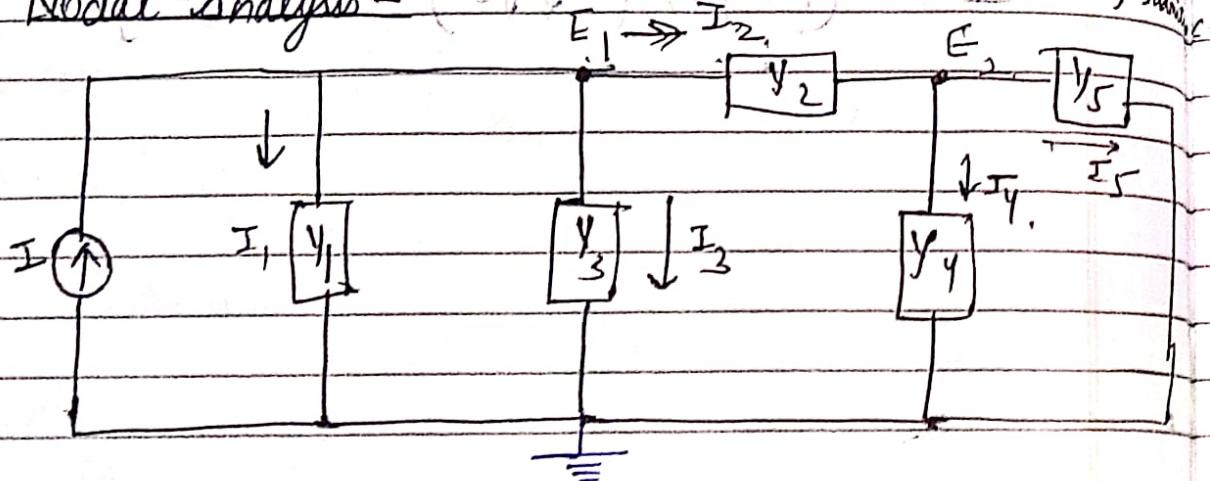2. 20 K.

Nodal Analysis = $(2) \cdot (Y) \cdot (I + V)$



$$\text{Node 1} \Rightarrow I = I_1 + I_2 + I_3 \text{ or } I_1 + I_2 + I_3 = I$$

$$E_1 Y_1 + (E_1 - E_2) Y_2 + E_1 Y_3 = I$$

$$\text{Node 2} - I_2 = I_4 + I_5 \text{ or } I_2 - I_4 - I_5 = 0$$

$$(E_1 - E_2) Y_2 - E_2 Y_4 - E_2 Y_5 = 0$$

$$(Y_1 + Y_2 + Y_3) E_1 + (-Y_2) E_2 = I \quad \textcircled{1}$$

$$(-Y_2) E_1 + (Y_2 + Y_4 + Y_5) E_2 = 0 \quad \textcircled{2}$$

$$\begin{bmatrix} Y_1 + Y_2 + Y_3 & -Y_2 \\ -Y_2 & Y_2 + Y_4 + Y_5 \end{bmatrix} \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} I \\ 0 \end{bmatrix}$$


$$[Y] [E] = [I]$$

$$\begin{bmatrix} Y_{11} & -Y_{12} \\ -Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$


\downarrow
Self admittance.
Mutual admittance.

6. $27^{\circ} 12' 3'' \rightarrow$ angle conversion ratio.

17/32

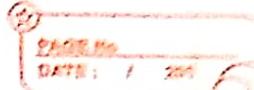

e. Ques.

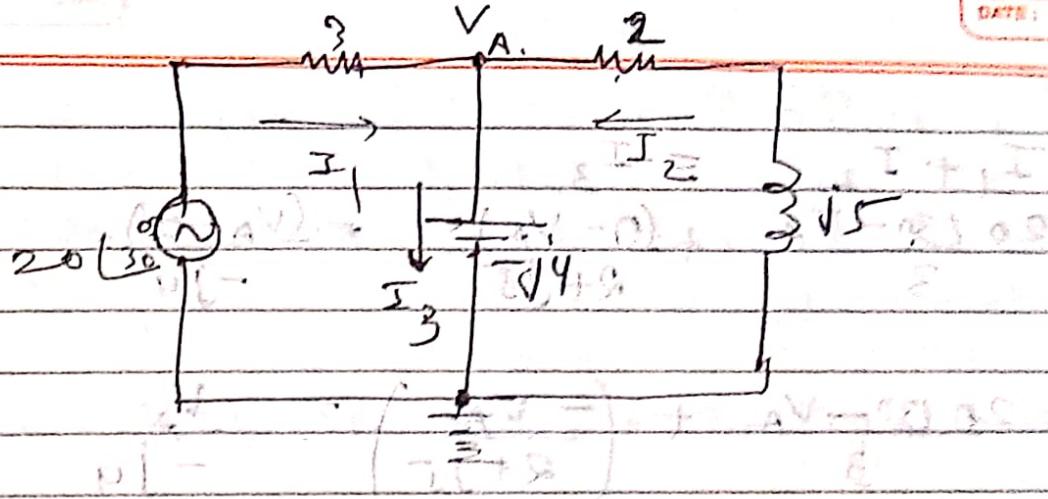

Find the power dissipated in each resistance.

$$(1) \Rightarrow I_1 + I_2 = I_3$$

$$\frac{20}{30} - V_A + \frac{(0 - V_A)}{2 + j5} = \frac{(V_A - 0)}{-j4}$$

$$I_1 = \frac{(17.32 + 10j - V_A)}{3} + \frac{(0 - V_A)}{2 + j5} = \frac{V_A - 0}{-j4}$$

$$P_{332} = I_1^2 \times 3 = (2 + j5)^2$$

$$P_{2-2} = I_2^2 \times 2 = \frac{(17.32 + 10j - V_A)(2 + j5) + (-3V_A)}{3 \cdot (2 + j5)} = \frac{V_A}{-j4}$$

$$(17.32 + 10j - V_A)(2 + j5) + (-3V_A)$$

$$= \frac{V_A}{-j4}$$

$$(17.32 + 10j - V_A)(2 + j5) + (-3V_A) = \frac{V_A}{-j4}$$

$$3 \cdot j4 \sqrt{(17.32 + 10j - V_A)(2 + j5)} = 3V_A + \frac{3V_A(2 + j5)}{3 \cdot (2 + j5)(-j4)} = 0$$

$$\Rightarrow \frac{(-j4) \sqrt{(19.99(30^\circ) - V_A)(5.3(68.1))} - 3V_A}{-1 + j(2 + j5)} = 0$$

$$\Rightarrow 19.99(30^\circ)(j4)$$

$$\frac{I_1 + I_2}{3} = \frac{I_3}{2+j5}$$

$$\frac{20(30 - V_A)}{3} + \frac{(0 - V_A)}{2+j5} = \frac{(V_A - 0)}{-j4}$$

$$\frac{20(30 - V_A)}{3} + \left(\frac{-V_A}{2+j5} \right) = \frac{V_A}{-j4}$$

$$\frac{20(30 - V_A)}{3} = \frac{V_A}{-j4} + \frac{V_A}{R+j5}$$

$$\frac{(0 - V_A)}{R+j5} = \frac{(V_A - 0)}{-j4} + \frac{(V_A - 0)}{2+j5}$$

$$\frac{V_A}{R+j5} = \frac{V_A}{-j4} + \frac{V_A}{2+j5}$$

$$\frac{V_A}{R+j5} = \frac{(V_A - 0) + (0 - V_A)}{-j4} + \frac{(V_A - 0)}{2+j5}$$

$$\frac{V_A}{R+j5} = \frac{V_A}{-3(j4)} + \frac{V_A}{3(2+j5)}$$

$$\frac{V_A}{R+j5} = \cancel{\frac{V_A}{-3(j4)}} + \cancel{\frac{V_A}{3(2+j5)}}$$

$$\frac{V_A}{R+j5} = \cancel{\frac{V_A}{-3(j4)}} + \cancel{\frac{V_A}{3(2+j5)}}$$

$$\frac{V_A}{R+j5} = \frac{V_A}{3(2+j5)}$$

$$\frac{V_A}{R+j5} = \frac{V_A}{(2+3)(2+j5)}$$

$$\frac{V_A}{R+j5} = \frac{V_A}{(2+3)(2+j5)}$$

$$\frac{V_A}{R+j5} = \frac{V_A}{(2+3)(2+j5)}$$

$$1279.2 + 184.32j$$

$$1279.2 + 184.32j = 142.2 + 337.0j$$

$$-16.19 - 17.50j = V_B$$

$$(142.2 + 337.0j) - (-16.19 - 17.50j)$$

$$I_1 + I_2 = I_3$$

currents in loop 1 and 2

$$\text{around } 20 \angle 30^\circ - V_A + (0 - V_A) = V_A - 0$$

$$\text{due to source } 3 \text{ at } 3 \angle 27.5^\circ \text{ and } -j4 \text{ at } 180^\circ$$


would add up to zero due to KCL at node A

$$\frac{17.32 + 10j}{3} - \frac{V_A}{3} + \frac{-V_A}{2+j5} = \frac{V_A}{-j4}$$

$$\frac{17.32 + 10j}{3} = -\frac{V_A}{j4} + \frac{V_A}{3} + \frac{V_A}{2+j5}$$

$$\frac{17.32 + 10j}{3} = (0.402 + 0.027j) V_A$$

$$15.38 + 5.34j = V_A$$

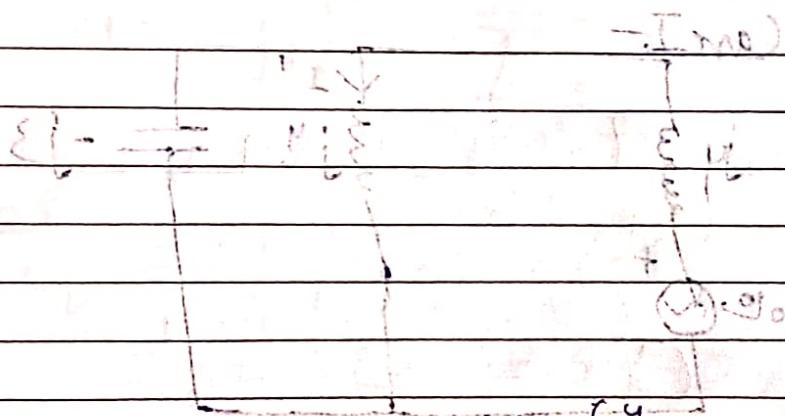



~~$$V_A = 17.32 - 15.38 - 30.6j$$~~

$$V_A = (17.32 - 15.38) + 4j$$

Superposition Theorem

In an active linear network containing several sources, the overall response in any branch is equal to the algebraic sum of the response of each source considered separately with all other sources replaced by their internal impedances.

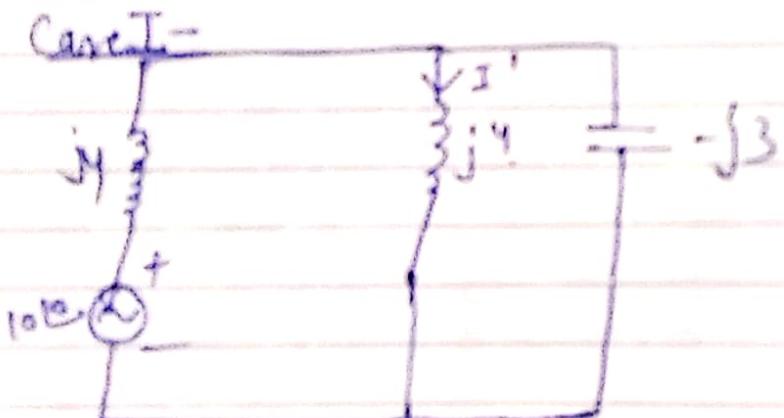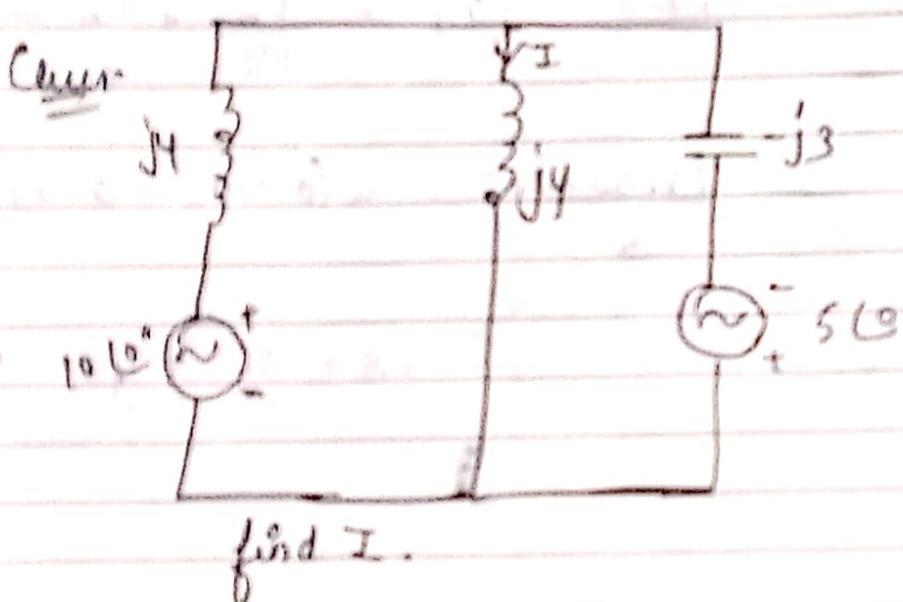- * Internal impedance of real voltage source
 ↓
 short circuit its internal impedance
 $= 0$.
- Internal impedance of real current source
 ↓
 open circuit its internal impedance
 $= \infty$.



$$\begin{aligned}
 Z_{eq} &= [j4 || -j3] + j4 \\
 &= \frac{j4(-j3)}{j4 + (-j3)} + j4 \\
 &= -j8.
 \end{aligned}$$

(2)

$$I_{AB} = \frac{V}{Z}$$

$$= \frac{10\angle 0^\circ}{0-j8} = \frac{10\angle 0^\circ}{8\angle -90^\circ} \\ = 1.25\angle 90^\circ$$


$$I' = 1.25\angle 90^\circ \times \frac{-j3}{j4 + (-j3)}.$$

$$I' = 1.25\angle 90^\circ \times \frac{3\angle -90^\circ}{j4\angle 90^\circ + (-j3)\angle -90^\circ}$$

$$= 1.25\angle 90^\circ \times \frac{3\angle -90^\circ}{1\angle 90^\circ}.$$

$$I' = 3.75\angle -90^\circ.$$

Case 2 -

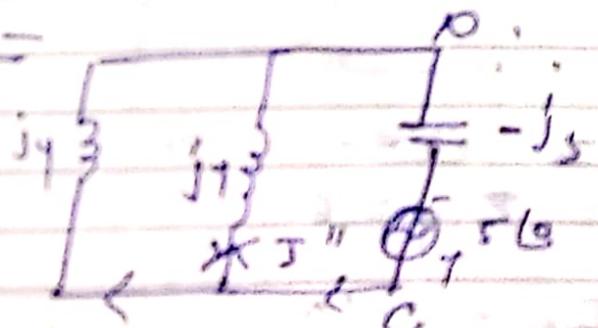

$$I_{CQ} = (j4/1/j4) + (-j3) = -j.$$

$$I_{CD} = \frac{5\angle 0^\circ}{0-j} = 5(90^\circ \text{ or } j5).$$

$$I'' = j5 \times \frac{j4}{j4 + j3}$$


$$j^2 = -1$$

$$I = I + (-I)''$$

$$I = (-j3 \cdot 75 + -j2 \cdot 5) = -j6.25 \\ = 6.25\angle 90^\circ$$



Find current in capacitor.

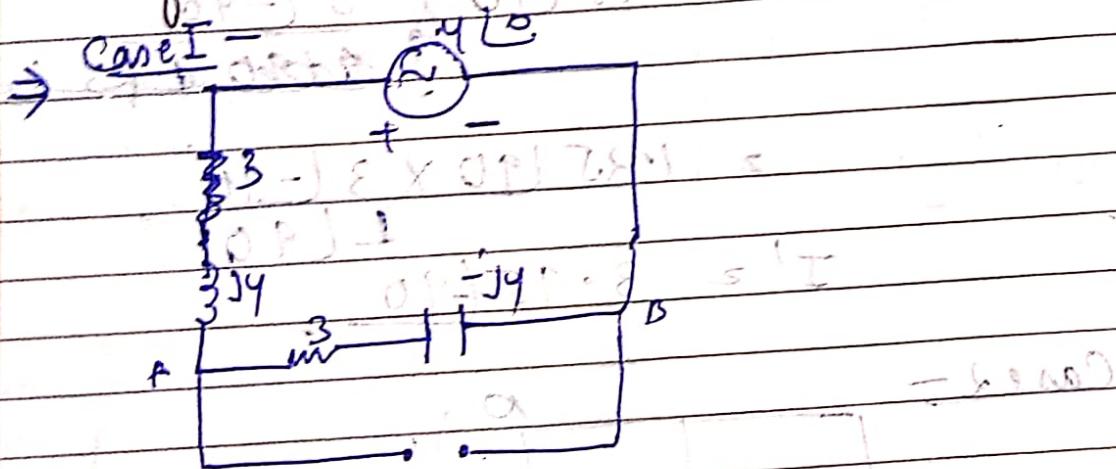


$$Z_C = -j25$$

$$Z_{eq} = 6$$

$$I_{AB} = \frac{410}{6} = 68.33 A$$

$$I = (143 + j43) \times \frac{1}{68.33} = 2.066 A$$

$$\text{Case II } I_C = 2.066 A$$

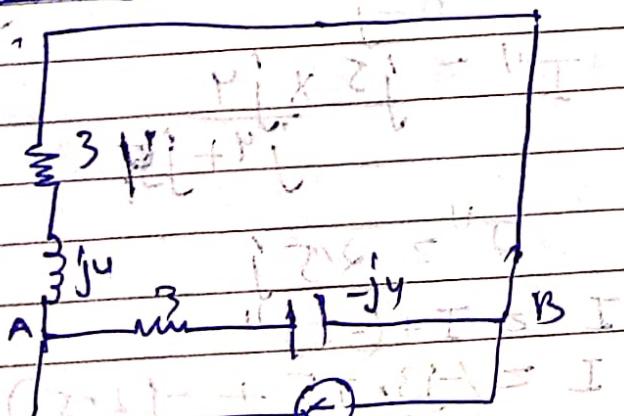

$\sqrt{2} I_2$

4°

$Z_{eq} = 0$

R_{eq}

$$Z_{eq} = 2(90) \times \frac{3+j4}{3+j4+3-j4}$$

$$= 2(90) \times \frac{3+j4}{6}$$

$$= 2(90) \times \frac{5}{53.13} \quad 6$$

$$= 2(90) \times 0.83 \quad 6$$

$$= 1.66 (13.13)$$

$$G_P S = I_1 S$$

$$= Z_{eq} + Z_{eq}$$

$$= 0.66 \quad 6 + 1.66 \quad 13.13$$

$$= 0.66 + 0j + (-1.32 + 0.99j)$$

$$2j\omega = 7$$


$$= -0.66 + j - 1.32$$

$$G_P S$$

$$OP) 2 = T \quad j = 7.19 (123.4)$$

15/09/22


Ques.

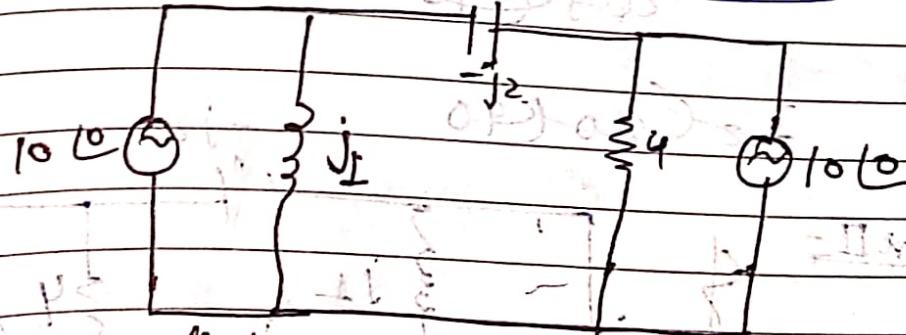

find current through inductor as well as capacitor.

resultant will be zero

Case I-

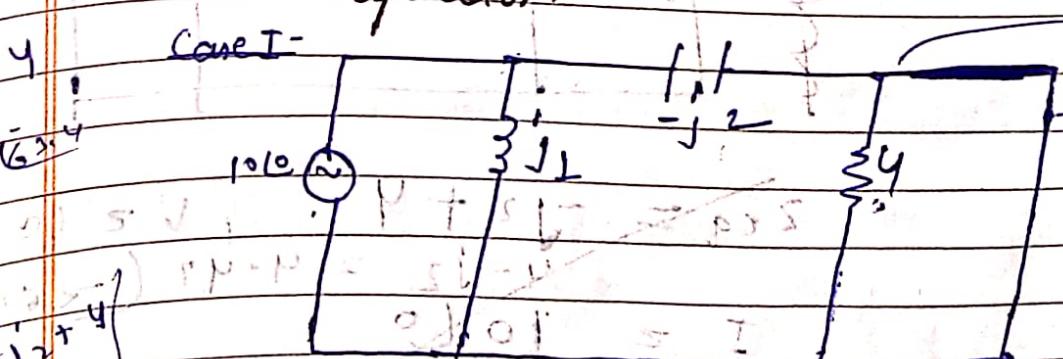

$$Z_{eq} = j_1 // j_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{j_1} + \frac{1}{-j_2} \Rightarrow -j_2 + j_1$$

$$(V_L + V_O) S = \frac{V_1}{-j_2 j_1} \cdot \frac{V_2}{-j_2 j_1}$$

$$(V_L + V_O) S = \frac{-j_1}{-j_2 j_1}$$

$$\begin{aligned} (V_L + V_O) S &= \frac{1}{2} (-90) \\ (V_L + V_O) S &= \frac{1}{2} (-90) \cdot 1 (90) \\ (V_L + V_O) S &= \frac{1}{2} (-90) \end{aligned}$$


$$Z_{eq} = 200 \Omega \quad (Z_{eq} = 2 \text{ } \angle -90^\circ)$$

$$\text{Case I: } I = \frac{V}{Z_{ca}} = \frac{10}{2 \text{ } \angle -90^\circ} \text{ A}$$

$$I = 5 \text{ } \angle 90^\circ \text{ A}$$

$$I = 5 \text{ } \angle 90^\circ$$

Case II:

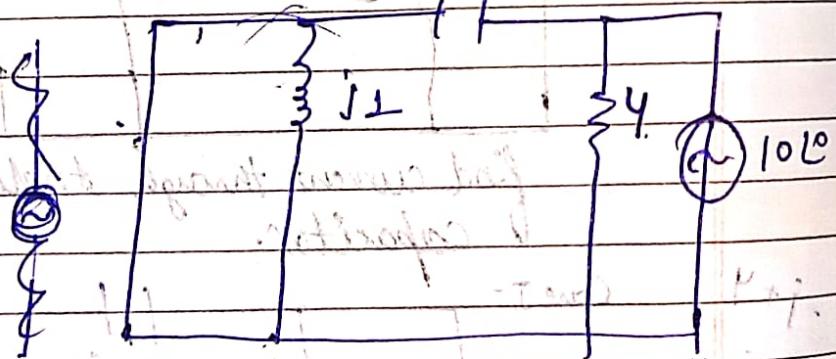

$$Z_{eq} = -j_2 + j_1, \quad V = 10 \text{ } \angle 0^\circ$$

$$-j_2 = 4 \cdot 47 \text{ } \angle -26.5^\circ$$

$$I = 10 \text{ } \angle 0^\circ$$

~~$$I = 4.47 \text{ } \angle -26.5^\circ$$~~

~~$$I = 2.23 \text{ } \angle -26.5^\circ$$~~


Q1, P. 11, Q1.1

$$Z_Q = \frac{1}{-j2} + \frac{1}{4+j2}$$

(as capacitor) $\frac{1}{-j2} \rightarrow 0.5 - j0.5$

$$= \frac{4+j2 - j2}{4+j2}$$

Ans:

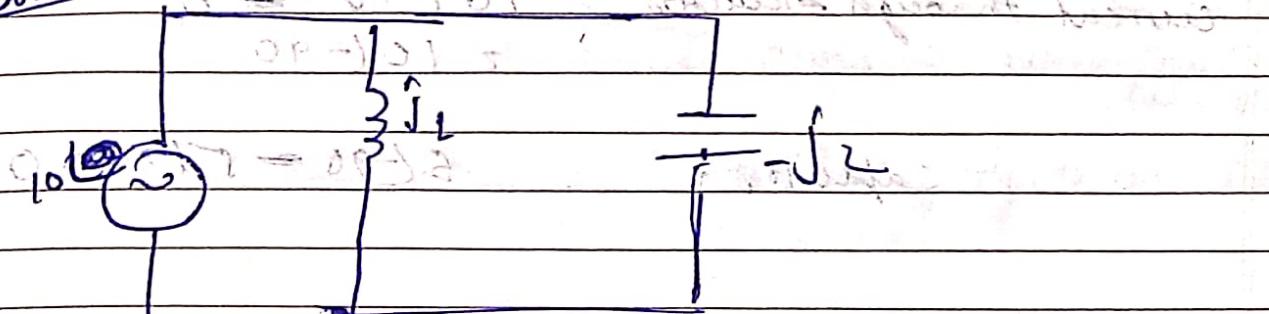

- current will flow clockwise so resistance

$$I \text{ through } j_1 = 10 \text{ A}$$

(inductor), now at node 0, j_1 flows upwards, $-j_2$ flows downwards, and $j_1 - j_2 = 10 \text{ A}$ since $j_1 = 10 \text{ A}$ and j_2 is to switch out 10 A

$$\text{Required } Z = 10 - 9.0 \text{ ohm}$$

so I through $-j_2 = 10 - 9.0 = 1.0 \text{ A}$

Now V_{-j_2} (Capacitor) \rightarrow $10 - 9.0 = 1.0 \text{ A}$


now with $-j_2$ up $\rightarrow 10 \text{ A}$

$$= 10 - 9.0 = 1.0 \text{ A}$$

$$= 5.90$$

$$= 10 - 9.0 + 5.90 = 6.90$$

Ans: $Z = 6.90 \text{ ohm}$

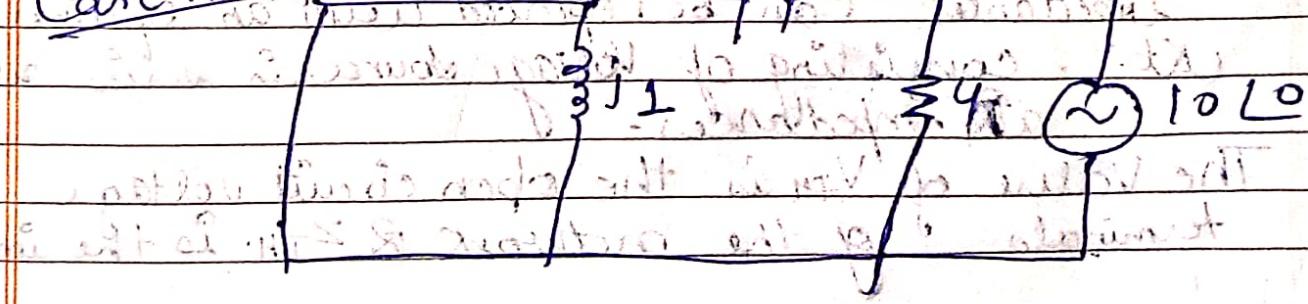





measured upto the terminals of the network with all
circuit sources replaced by their standard
impedances.

Limitations of Thevenin's theorem:-

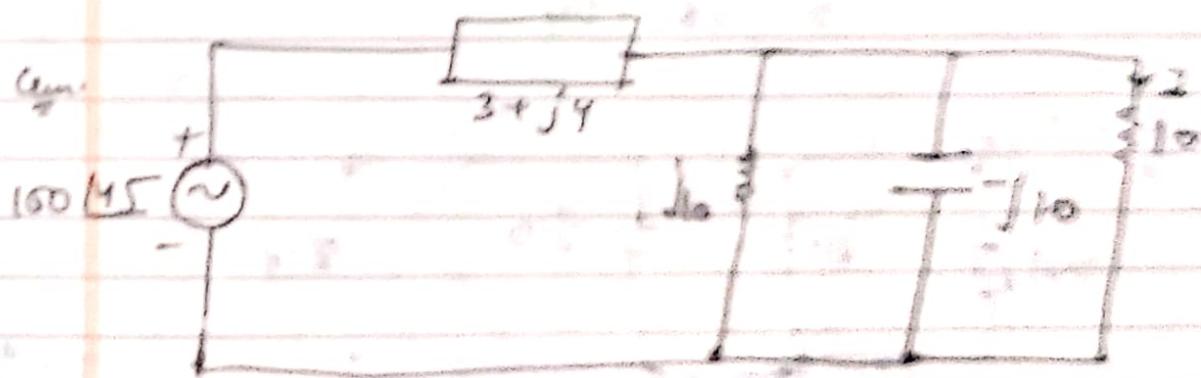- ① Not applicable to circuits consisting unilateral elements like diode.
- ② Not applicable to circuits consisting of non-linear elements like diode, transistor.
- ③ Not applicable to circuits consisting of controlled or dependent sources.
- ④ Not applicable to circuits consisting of mutual coupling between load & any other CT or CTs.



find V_M or V_{CE} .

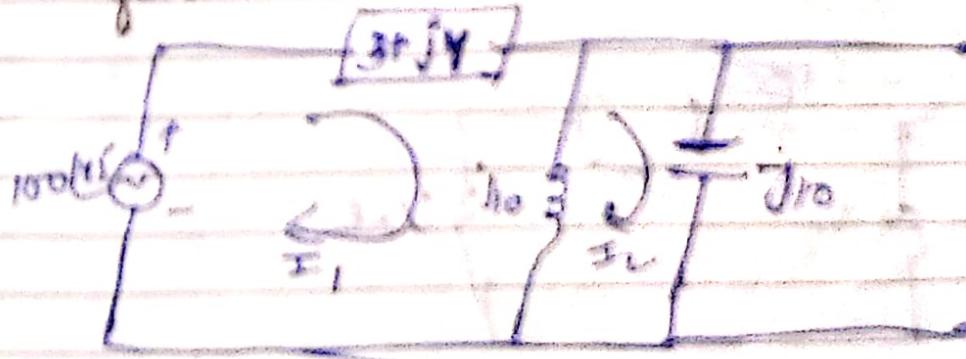

j, ||/f¹ < || 109

$$\text{Capacitor} = \frac{10}{10\pi}, \text{ Inductor} = 0$$

$$Z = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} =$$

$$= 5(1.40)$$

$$\text{current through inductor } Z = 10^{-90} \rightarrow 0$$
$$Z = 10^{-90}$$

Capítulo: 5790 = 5,120,20


Limitation of superposition theorem -

1. Applicable only to linear ckt., not applicable to circuits consisting non-linear elements like diode, transistor etc.
 2. Not valid for power Relationships.
 3. Not applicable to ckt consisting of only dependent sources, not useful to CKTs consisting of less than two independent sources.

Thevenin's Theorem

Any two terminals containing energy sources & impedances can be replaced with an equivalent Kt . consisting of voltage source in series with all impedances.

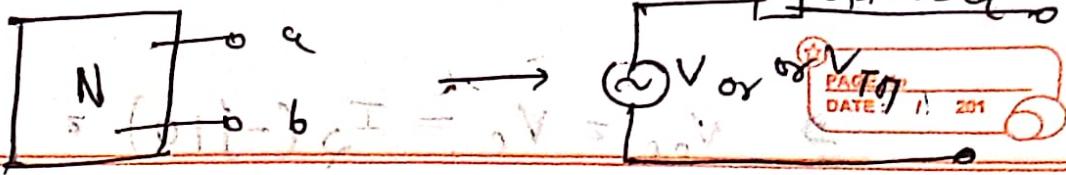
The value of V_{TH} is the open circuit voltage ^{lecture} terminals of the network & Z_{TH} is the input impedance.




measured b/w the terminals of the network with all energy sources replaced by their internal impedances.

Limitations of Thvenin's theorem:-

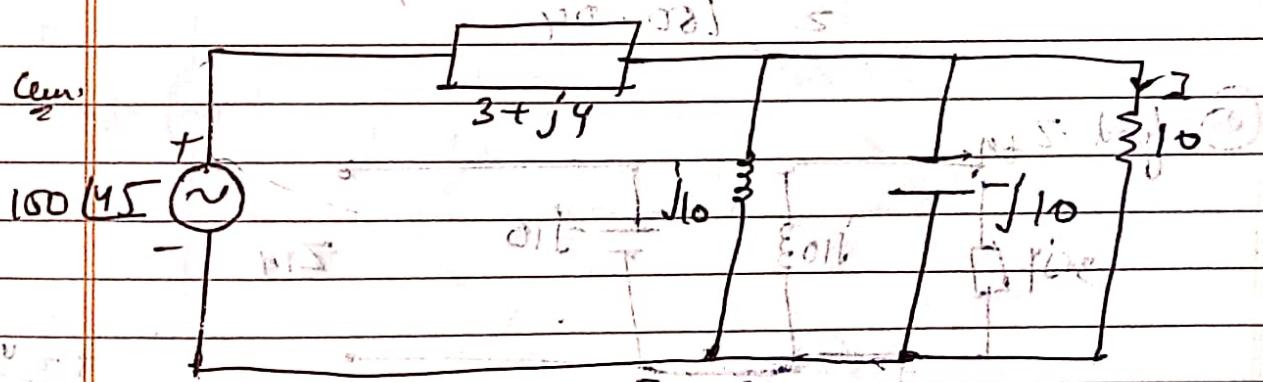- (1) Not applicable to circuits consisting unilateral elements like diode,
- (2) Not applicable to circuits consisting of non-linear elements like diode, transistor.
- (3) Not applicable to circuits consisting of controlled or dependent sources.
- (4) Not applicable to circuits consisting of magnetic coupling between load & any other ckt element.



find V_{TH} or V_{oc}

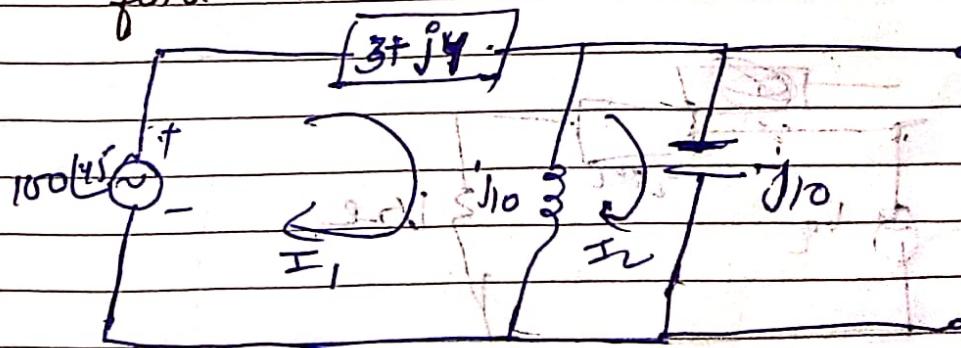

$$\Rightarrow V_{oc} = V_c = I_2 (-j10) \frac{1}{z}$$

$$\begin{bmatrix} 3 + j1 & -j10 \\ -j10 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 100 \angle 45^\circ \\ 0 \end{bmatrix}$$

$$\Delta = 100 \angle 0^\circ$$

$$\Delta_1 = 0, \Delta_2 = 100 \angle 135^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{100 \angle 135^\circ}{100 \angle 0^\circ}$$


$$= 10 \angle 135^\circ$$

$$V_{oc} = V_c = 10 \angle 135^\circ (-j10)$$


$$= 10 \angle 135^\circ 10 \angle 0^\circ j (-84.2^\circ)$$


$$= 160.04$$


⑤ find Z_{th}

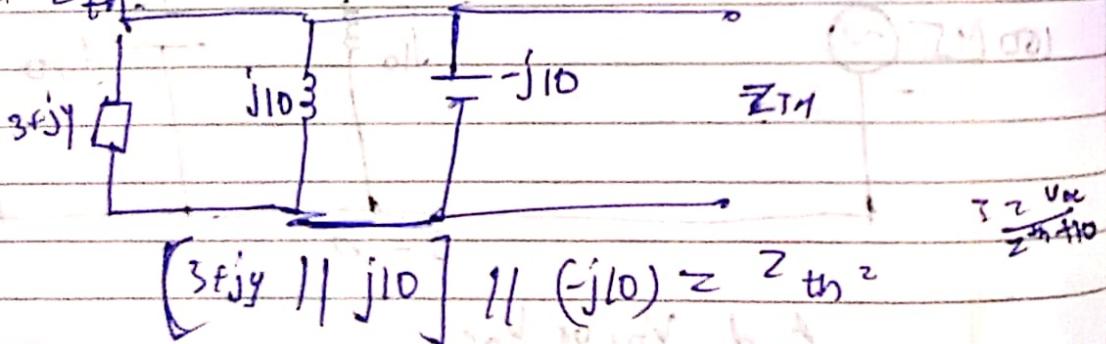


⑥

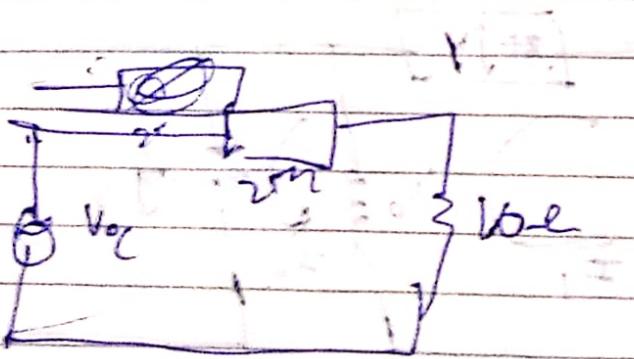

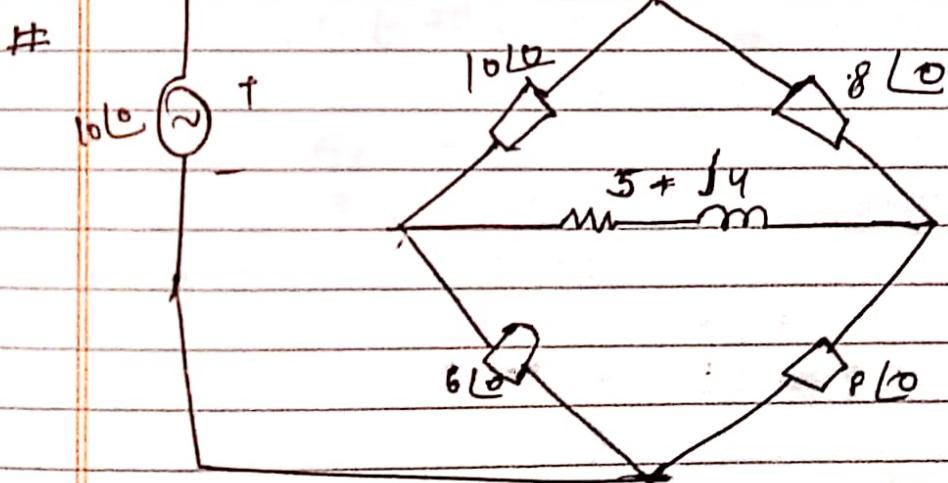

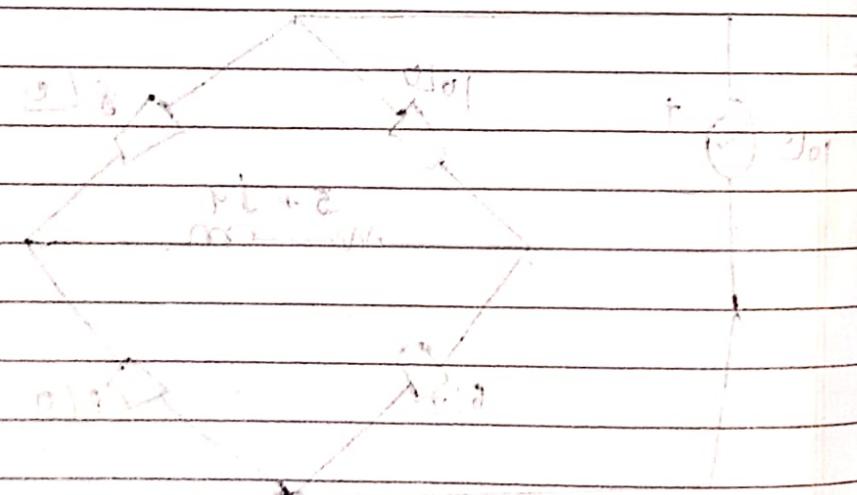

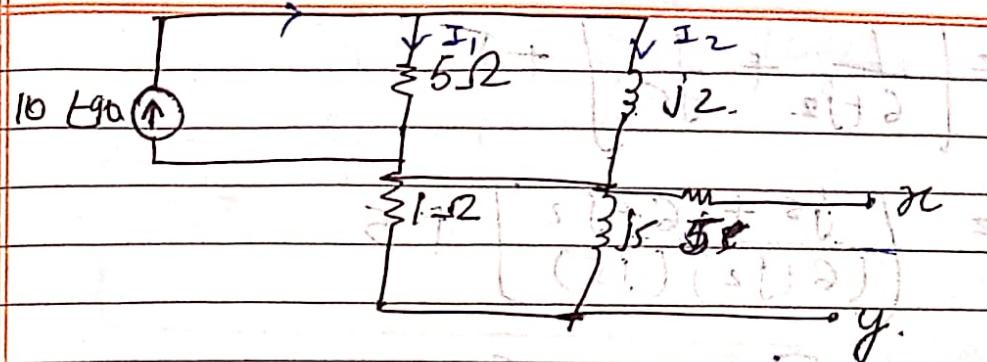CircuitFind V_{oc} + Z_{th} at terminals $x-y$.

$$\Rightarrow \text{V}_{oc} = V_{j5} = I_2(j5) = \frac{10 L - 90 \times 5}{5 + (j2 + j5 + 1)}$$

$$= 10 L - 90 \times \frac{5}{5 + j7 + 1}$$

$$= 10 L - 90 \times \frac{5}{6 + j7}$$

$$= 10 L - 90 \times \frac{5}{9.2 L 49.3}$$

$$= 50 L - 90$$

$$9.2 L 49.3$$

$$= 5.43 L - 139.3$$

$$\begin{aligned} & -50 L - 90 \\ & -5.43 L 0.73 \\ & \hline 208.90 L 70.78 \end{aligned}$$

$$V_{oc} = I_2 \times j5$$

$$= 27.15 L - 90.73 X$$

$$= 5.43 L - 139.3 X j5$$

$$= 5.43 L - 139.3 X 5 L 90$$

$$V_{oc} = 27.15 L - 49.3 V$$

$$Z_{th} = \left[(5 + 1 + j2) || j5 \right] + 5$$

$$= (6 + j2) || j5 + 5$$

$$= \left[\frac{1}{6+j2} + \frac{1}{j5} \right] + j5$$

$$= \left[\frac{j5 + 6+j2}{(6+j2)(j5)} \right] + j5$$

$$\left[\frac{j7 + 6}{(6+j2)(j5)} \right] + j5$$

$$= \frac{j7 + 6 + (6+j2)(j5)}{(6+j2)(j5)}$$

$$= 6.32 (18.4 - 5j90)$$

V_{TH}
= 16V

$$21 \times 0.32 = 6.72$$


$$21 \times 0.32 - 16 = 0.32$$

$$0.32 \times 0.32 - 16 = -15.84$$

$$0.32 \times 0.32 - 16 = -15.84$$


$$21 \times 0.32 - 16 = 0.32$$

$$21 \times 0.32 - 16 = 0.32$$

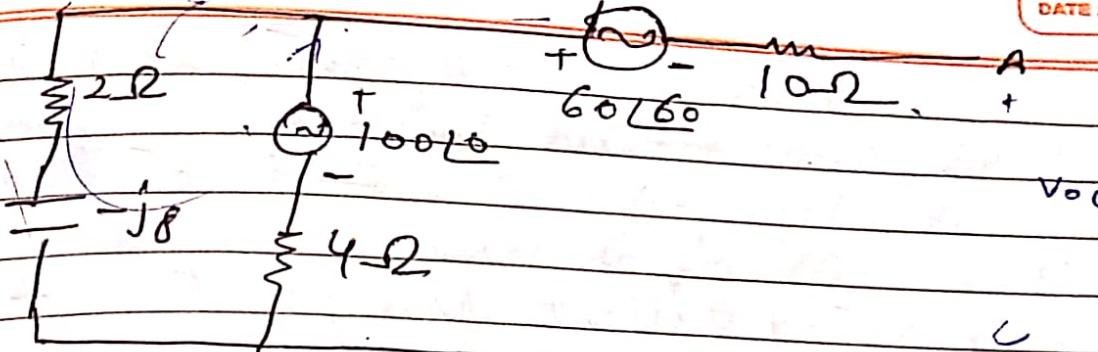

find Thevenin eq. Circuit

B.

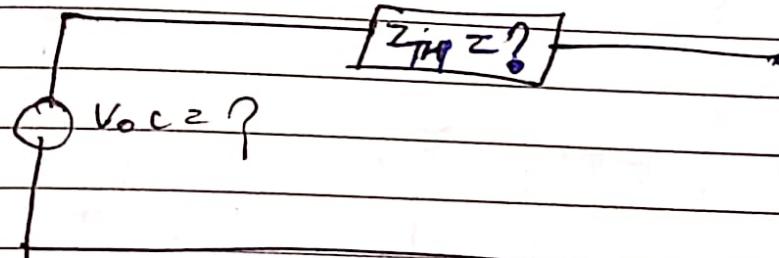

~~R_{TH} = 2 - j8 + 4~~

$$R_{TH} = 2 - j8 + 4 \\ = 6 - j8.$$

$$I_T = 100 \angle 0^\circ \times 6 - j8 \\ = 100 \angle 0^\circ \times 10 \angle -53.13^\circ \\ = 100 \angle 53.13^\circ$$

$$I = \frac{100 \angle 0^\circ}{10 \angle -53.13^\circ} \\ = 10 \angle 53.13^\circ$$

$$\text{Voltage across } 4\Omega \text{ drop} = 10 \angle 53.13^\circ \times 4 \\ = 40 \angle 53.13^\circ = 24 + j32.$$

By applying KVL,

$$-40 \angle 53.13^\circ + 100 \angle 0^\circ - 60 \angle 60^\circ \\ - 40 \angle 53.13^\circ + 100 \angle 0^\circ - 60 \angle 60^\circ = V_{OC}$$

23
23

with 1st distinct half

$\{ \} = P$

Second

$\{ \} = Q$

$P + Q = S = P + Q$

$P - Q = T$

(Ans)

$S = P + Q$ or $S = T$

$S = P + Q$ or $S = T$

$P + Q = S$

$P + Q = T$

$S = P + Q$

$S = P + Q$

$S = P + Q$ or $S = T$

$S = P + Q$ or $S = T$

$T = P + Q$


$S = P + Q$ or $S = T$

$S = P + Q$


$S = P + Q$ or $S = T$

Norton's Theorem

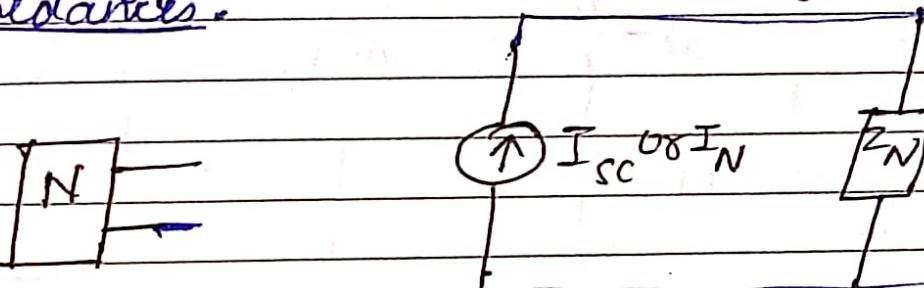Any two terminal network containing energy sources and impedances can be replaced by an equivalent source in parallel with an impedance. The value of current source is thus, short circuit current between the terminals with all energy sources replaced by their internal impedances.



Norton's eqⁿ Circuit.

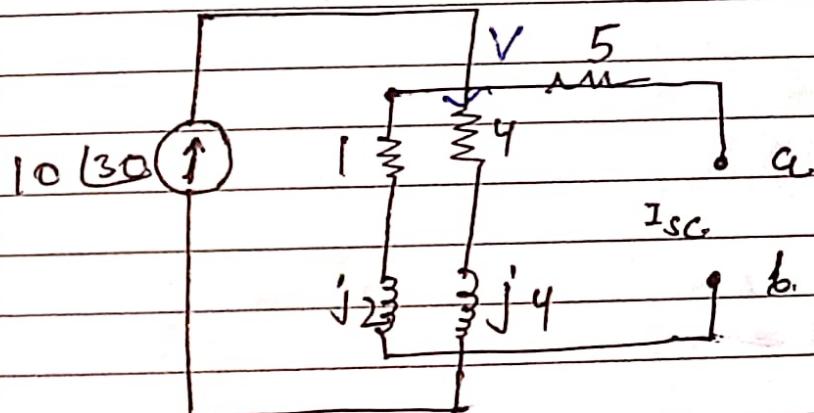

Draw norton's eq. circuit

By nodal,

apply KCL eqⁿ -

$$10/30 = \frac{V_1}{1+j_2} + \frac{V_2}{4+j_4} + \frac{V_3}{5}$$

$$10/30 = \frac{(4+j_4)(5) + 5(1+j_2) + (1+j_2)(4+j_4)}{(1+j_2)(4+j_4)(5)}$$


$$10/30 = \frac{5.65 - 45 \cdot 5/10 + 5[3 \cdot 23(3.4) + 2 \cdot 23(6.3 \cdot 4)] - 2 \cdot 23[6.3 \cdot 4] \cdot 5.65 / 510}{(5.65 \cdot 45)}$$

$$V = 42 \times 64^4, \quad Z_k = 109 \text{ N/mm}^2 \quad \underline{Z_{02}} [((j_2) 11 + (j_4) 2)] + 5$$


$$10 [30 \times 2.23] 63.4 \times 5.65 / 45 \times 510$$

$$\approx \sqrt{5.65 / 45 \times 510} + 5 / (2.23)$$


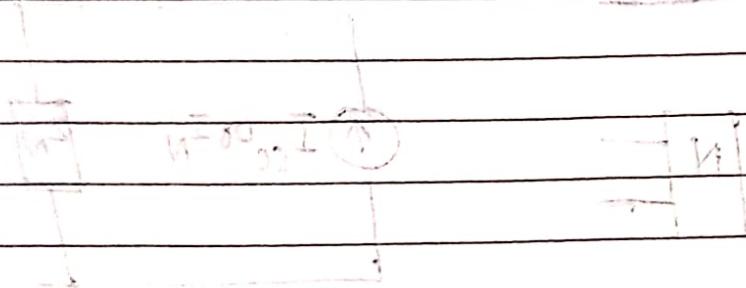
$$\Rightarrow 629.975 / 138.4 = \sqrt{28.35 / 45 + 11.15 / 6} + 12$$



Method of Sections

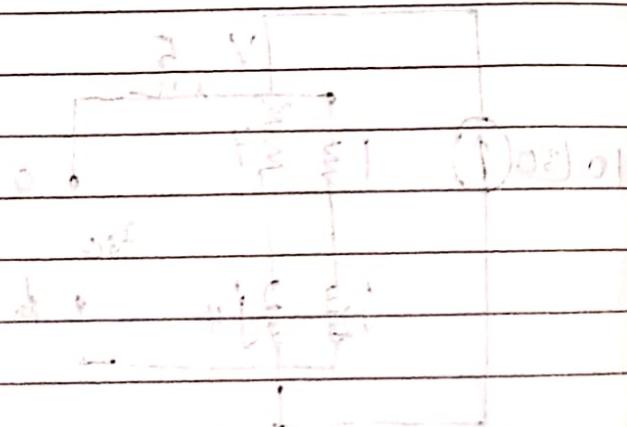

Method of Sections

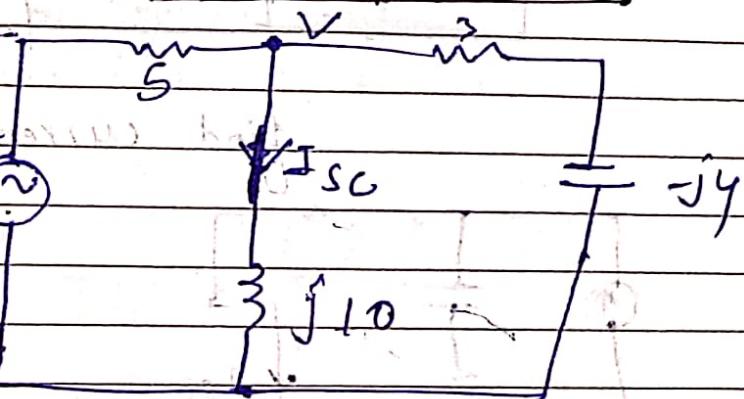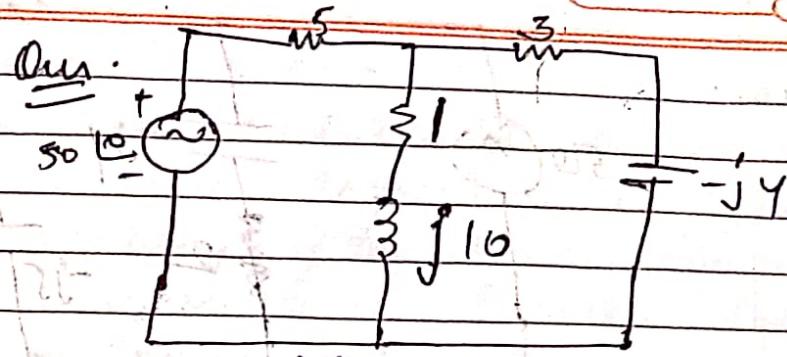

$$V - 50\angle 0^\circ + \frac{V}{3-j10} + \frac{V}{3-j4} = 0$$


$$V = 30.7 \angle (-100^\circ)$$

$$V = 30.7 \angle (-10^\circ)$$

$$\frac{V}{j10} = I_{sc} = \frac{30.7 \angle (-10^\circ)}{j10 \angle 90^\circ} = 3.07 \angle (-100^\circ)$$

$$Z_N = j10 + \frac{5(3-j4)}{5+3-j4}$$


$$= 9.1 \angle 74.05^\circ$$

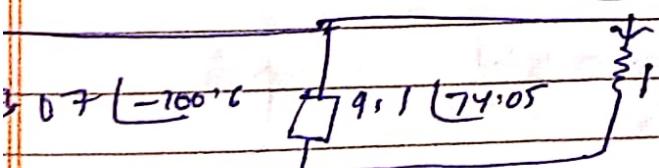


$$I = 3.07 \angle (-100^\circ) \times \frac{-9.1 \angle 74.05^\circ}{9.1 \angle 74.05^\circ + 1}$$

=

Ans.

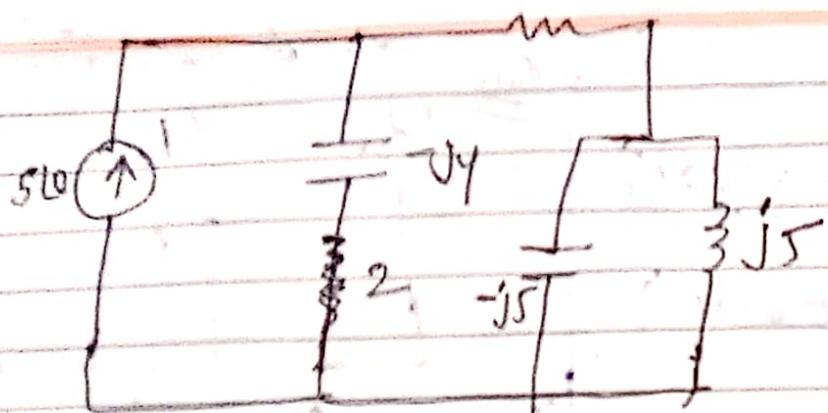


find current through $-j5$.

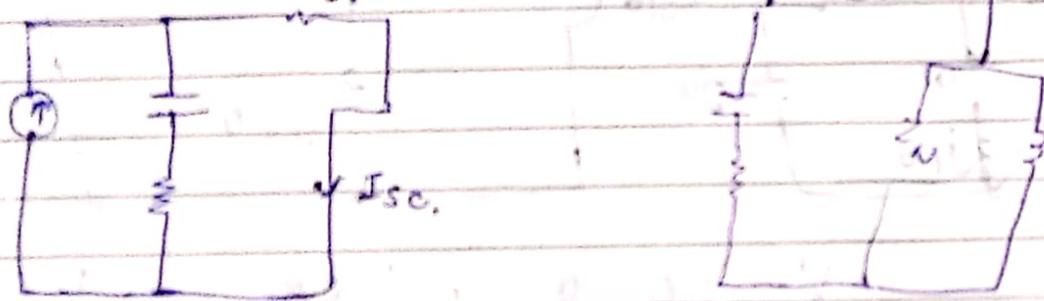

~~J. J. J.~~

Maximum Power Triangle Theorem -

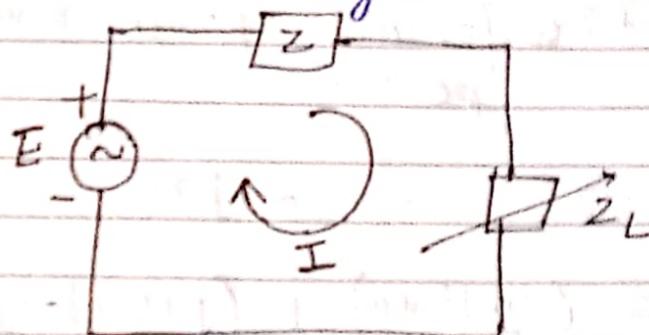Maximum power will be delivered by the network when the load reactance is equal to the complex conjugate of the internal impedance of the network, measured looking back into the terminals of the network.



$$I = \frac{E}{Z + Z_L}$$

$$P = I^2 R_L$$

$X_L \rightarrow$ Reactance

$Z_L \rightarrow$ Impedance

$$\text{where } Z = R + jX$$

$$Z_L = R_L + jX_L$$

$$P = \left(\frac{E}{Z + Z_L} \right)^2 R_L = \frac{E^2}{(R + R_L)^2 + (X + X_L)^2} R_L \quad \text{--- (1)}$$

for maximum power $\frac{\partial P}{\partial X}$ must be zero,

$$\frac{\partial P}{\partial X} = 0 \Rightarrow [X_L Z - X]$$

Again, for maximum power $\frac{\partial P}{\partial R}$ must be zero.


$$\frac{\partial P}{\partial R} = 0 \Rightarrow [X_L^2 - R]$$

$$[X_L^2 = R]$$

$$P_{\max} = \frac{E^2}{4R_L}$$

$$\left(\frac{1}{10} + \frac{1}{40} \right) + \left(\frac{1}{10} - \frac{1}{20} \right)$$
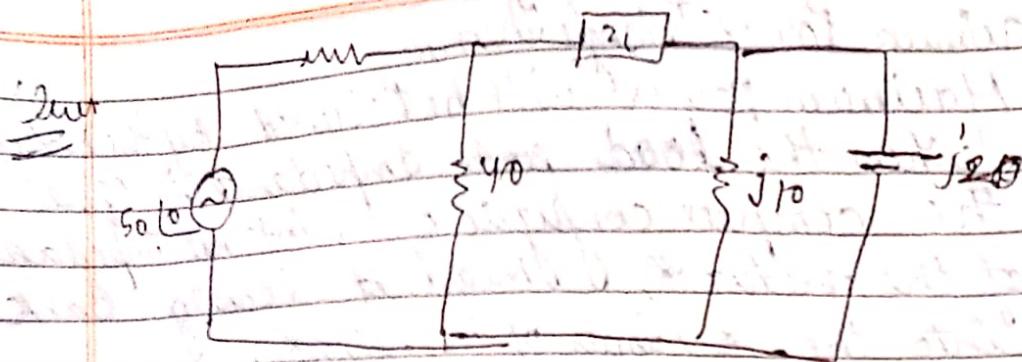
$$0.125 + \left(\frac{1}{10} j - \frac{1}{20} j \right)$$



Find Z_b for max power & value of max power.

$$Z_L = Z^* = 8 - j20,$$


$$Z = (10 \parallel 40) + (j10 \parallel -j20),$$

$$Z = \frac{10 \times 40}{10 + 40} + \frac{10j \times -20j}{10j - 20j}$$

$$Z = \frac{400}{50} + \left(\frac{-200j^2}{-10j} \right)$$

$$Z = 8 + \left(\frac{200}{-10j} \times \frac{10j}{10j} \right)$$

$$Z = 8 + 20j,$$

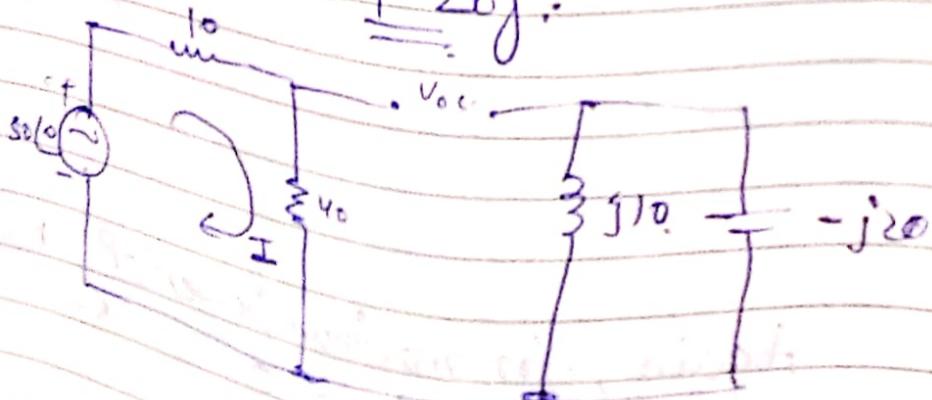

$$I = \frac{50\angle 0^\circ}{50} = 1$$

$$P_{max} \geq \frac{V_{oc}}{50} \times 40 \times 1 = 40$$

$$P_{max} = \frac{(V_{oc})^2}{4R_L}$$

$$= (40 \angle 0)^2$$

$$4(8 + 20j)$$

$$= (40 \angle 0)^2$$

$$(32 + 80j)$$


$$= (40 \angle 0)^2$$

$$8 \cdot 6 \cdot 16 / 68 \cdot 19$$

$$= 1600 / -68 \cdot 19$$


$$8 \cdot 6 \cdot 16$$

28 | 9 | 22

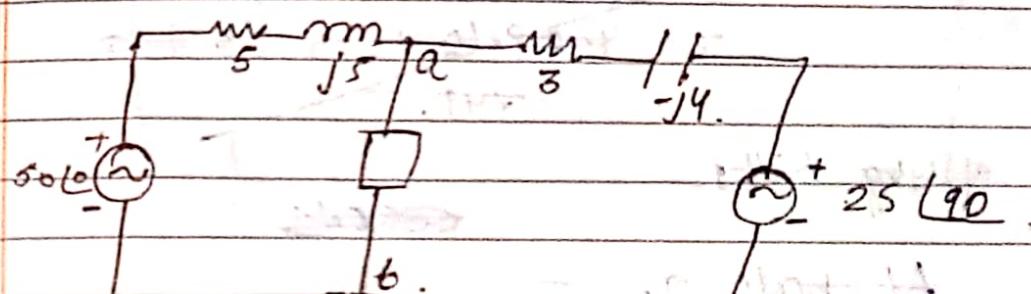

$$Z_L = ? \quad Z_1^* \text{ or } Z_m^*$$

$$P_L(\max) = ?$$

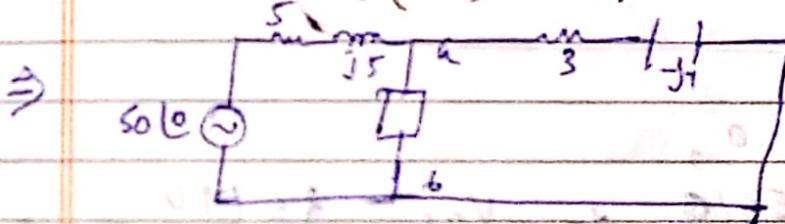

$$Z_m = 5 + j5 \parallel 11 \perp j4$$

$$= 5 + j5 \times 3 - j4$$

$$5 + j5 + 3 - j4$$

$$= (5 + j5)(3 - j4)$$

$$(5 + j5) + (3 - j4)$$

$$= 7.07 \angle 45^\circ \times 5 \perp (-53.1)$$

$$8 + j$$

$$= 35.35 \perp 8.1$$

$$8 + j$$

$$= 35.35 \perp 8.1$$


$$8.06 \perp 7.12$$

$$= 4.38 \perp 15.22$$

$$= 4.22 + 1.14j$$

$$R_L = 4.22 \Omega$$

$$\Rightarrow V_{oc}$$

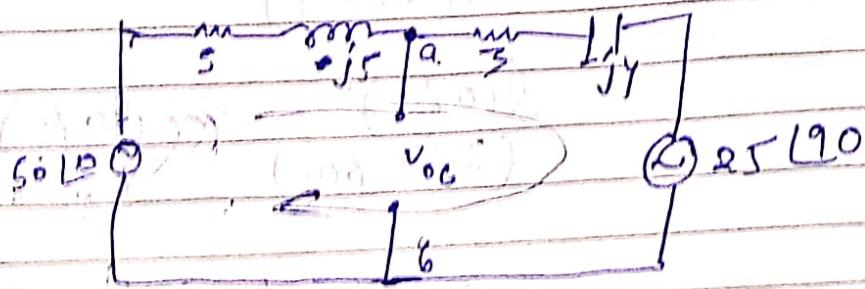

At node a,

$$\frac{V_{oc}}{5+j5} + \frac{(5+j5)}{4+4.8+10+4.3} \times 50 \text{ V} = 0$$

applying KVL;

at node b:

At node a,

$$5+j5 = 50 \text{ V}$$

applying KVL;

$$-50 \text{ V} -$$

at node a,

$$\frac{V_{oc} - 50}{5+j5} + \frac{V_{oc} - 25}{3+j4} = 0$$

$$\frac{3V_{oc} - 150}{(5+j5)} - \frac{4jV_{oc} + 5V_{oc} - 125}{3+j4} = 0$$

$$+ 5jV_{oc}$$

$$8V_{oc} - 150 - 125j + jV_{oc} + 200j - 125 = 0$$


$$V_{oc}(8+j) = 180 + 125j - 200j - 125$$

$$V_{oc} = \frac{125 - 75j}{8+j} = 9.8 \angle 75.5^\circ$$


$$P_{L\max} = \frac{(9.8)^2}{4 \times 4.22} =$$

6.21 (30°)

PAGE NO. : / DATE : / 201

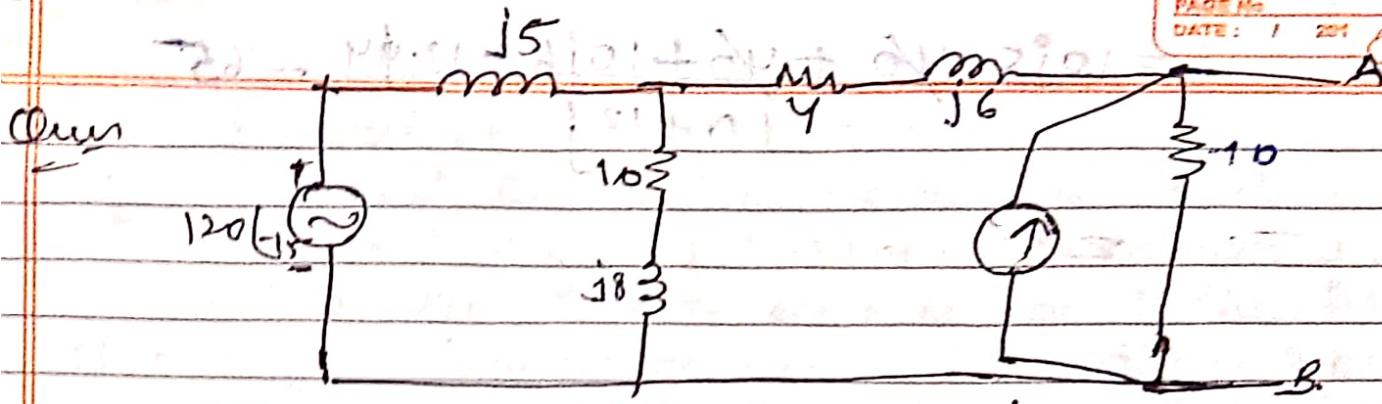

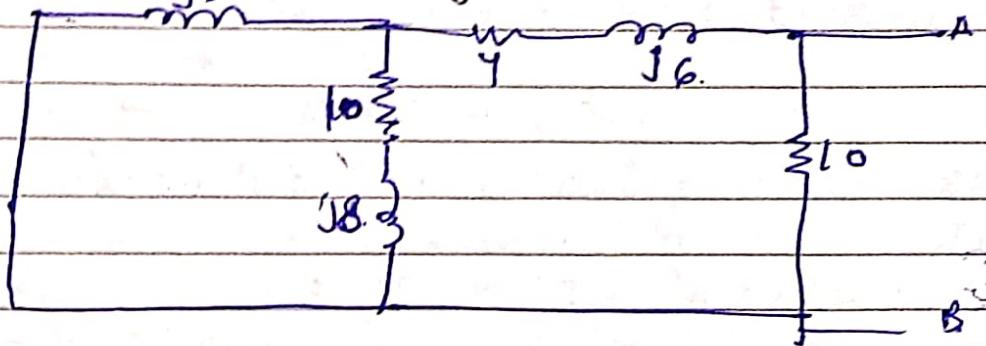
Find Z_{AB} across A-B for max power transfer.



$$\Rightarrow \text{Req } Z = 10 + j8$$

$$Z_{AB} = \frac{j5}{j5 + 10 + j8}$$

$$= \frac{j5(10 + j8)}{10 + 13j}$$

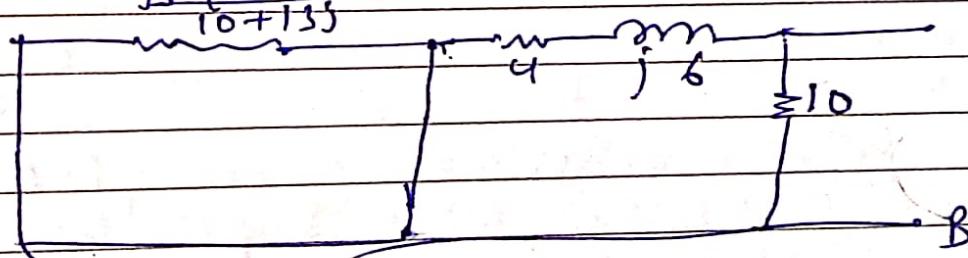

$$Z_{AB} = \frac{j5(10 + j8) + 4 + j6}{10 + 13j}$$


$$= \frac{j5(10 + j8) + (10 + 13j)(4 + j6)}{10 + 13j}$$

$$= \frac{10j5 + 40 + 40 + 40 \times j6 + 13 \times 4j}{10 + 13j} = G5$$


Compensation Theorem -

If a circuit circuit has certain distribution of voltages & currents across through various branches and due to some reason if the impedance of one of the branch changes, the voltage & current in other branches are affected. To nullify this effect the voltage source should be changed accordingly.


In a linear network N , having voltage source V (actually V_{oc}) with internal impedance Z_m , it delivers current I to the impedance Z . If the impedance changes from Z to $Z + \Delta Z$, then the change in current ΔI can be obtained by replacing Voltage source with its internal Impedance & placing a compensation voltage source of magnitude $V_c = I \Delta Z$ in series with impedance $(Z + \Delta Z)$ & its polarity is opposite to the flow of current I .

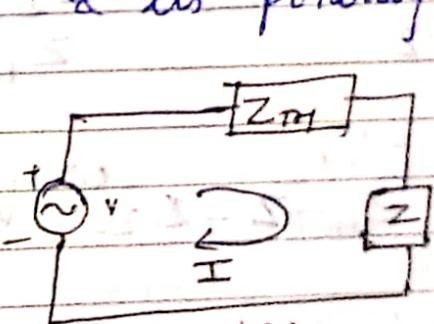

(a).

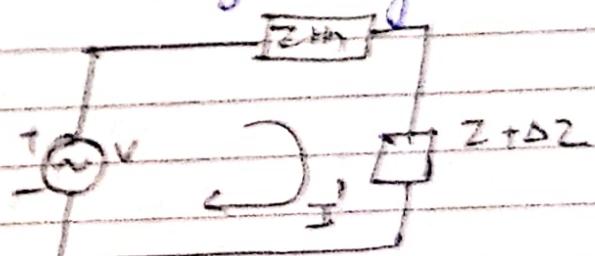

(b).

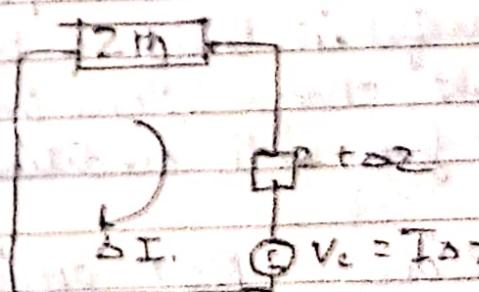

(c).

The current in fig (a) is $I = \frac{V}{Z_m + Z}$ — (1)

$$= 10j5 - y_6 + y_6 + 10j6 + 13 \cdot j4 - 65 \\ 10 + 13j$$

z

10+13j

and now we have the same chain

0.1m


10
13j

0.1m


Compensation Theorem -

If a circuit circuit has certain distribution of voltages & currents across & through various branches and due to some reason if the impedance of one of the branch changes, the voltage & current in other branches are affected. To nullify this effect the voltage source should be changed accordingly.

In a linear network N , having voltage source V (actually V_{oc}) with internal impedance Z_m , it delivers current I to the impedance Z . If the impedance changes from Z to $Z + \Delta Z$, then the change in current ΔI can be obtained by replacing voltage source with its internal impedance Z & placing a compensation voltage source of magnitude $V_c = I \cdot \Delta Z$ in series with impedance $(Z + \Delta Z)$ & its polarity is opposite to the flow of current I .

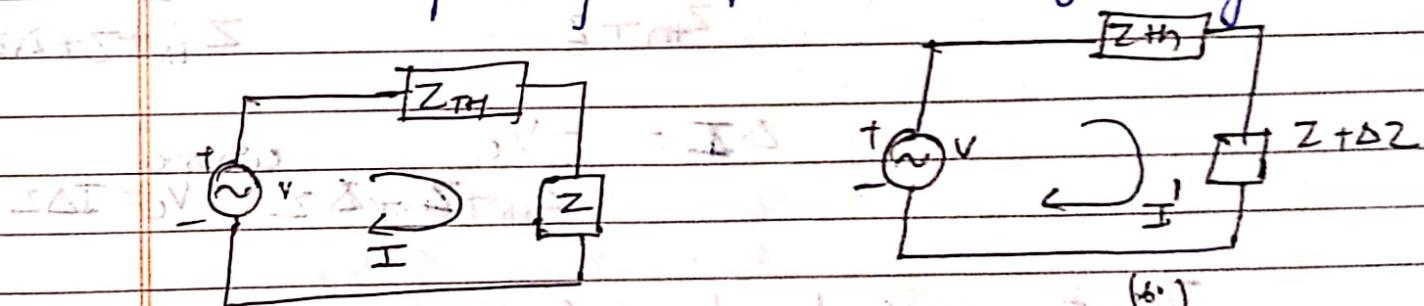

(a). Finding no load current

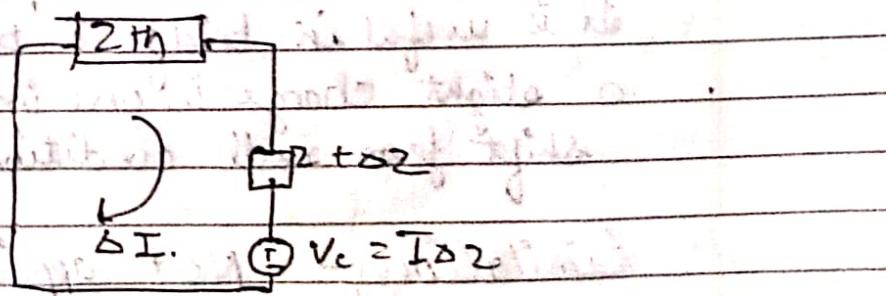

(b).

The current in fig. (a) is $I = \frac{V}{Z_m + Z}$

\Rightarrow If I_1 & I_2 are currents in the bridge then if impedance changed from Z to $Z + \Delta Z$

$$\therefore \text{Current } I = \frac{V}{Z_{th} + (Z + \Delta Z)} \quad \text{Eqn ②}$$

from Eqn ① & ②

$$\Delta I = I' - I = \frac{V}{Z_{th} + Z} - \frac{V}{Z_{th} + (Z + \Delta Z)}$$

$$\Delta I = \frac{V(Z_{th} + Z) - V(Z_{th} + Z + \Delta Z)}{(Z_{th} + Z + \Delta Z) \cdot (Z_{th} + Z)}$$

$$= \frac{V[Z_{th} + Z - Z_{th} - Z - \Delta Z]}{(Z_{th} + Z + \Delta Z) \cdot (Z_{th} + Z)}$$

$$= \frac{-\Delta Z}{(Z_{th} + Z + \Delta Z) \cdot (Z_{th} + Z)},$$


Since, $I \propto \frac{V}{Z_{th} + Z} \Rightarrow \Delta I = -I \Delta Z$

$$\Delta I = -\frac{V_c}{Z_{th} + Z + \Delta Z} \text{ where } V_c = I \Delta Z.$$

This theorem is based on principle of superposition.
It is useful in bridge & potentiometer circuit when
a slight change in one impedance result, in a
shift from null conditions.

Limitations - Not applicable to ckt, consisting
of only dependent sources, not applicable
to non-linear ckt's.

STAR DELTA TRANSFORMATION

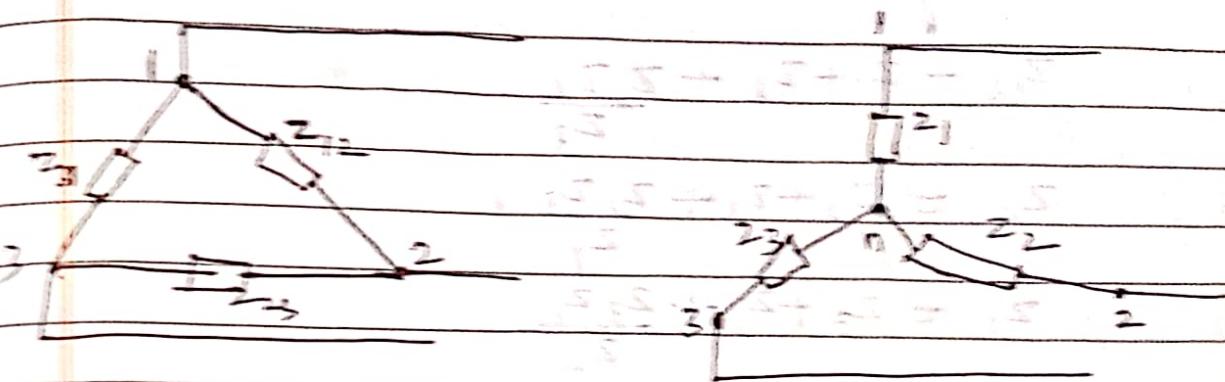

For star connection: The impedance between terminal 1 & 2 is $Z_1 + Z_2$.

For delta connection: Two parallel paths,
 \therefore impedance between 1 & 2 is $Z_{12} \parallel Z_{23} + Z_{31}$

Impedance between terminal 1 & 2 is

$$Z_1 + Z_2 = \frac{Z_{12}(Z_{23} + Z_{31})}{Z_{12} + (Z_{23} + Z_{31})} \quad \text{--- (1)}$$

Similarly impedance between 2 & 3

$$Z_2 + Z_3 = \frac{Z_{23} \cdot (Z_{12} + Z_{31})}{Z_{23} + (Z_{12} + Z_{31})} \quad \text{--- (2)}$$

Similarly impedance between 3 & 1.

~~$$Z_1 + Z_3 = \frac{Z_{31} (Z_{12} + Z_{23})}{Z_{31} + (Z_{12} + Z_{23})} \quad \text{--- (3)}$$~~

Subtracting eq (2) from (1) & adding result to eq (3)

$$Z_1 = \frac{Z_{12} \cdot Z_{31}}{Z_{12} + Z_{23} + Z_{31}}$$

$$Z_2 = \frac{Z_{23} \cdot Z_{12}}{Z_{12} + Z_{23} + Z_{31}}, \quad Z_3 = \frac{Z_{31} \cdot Z_{23}}{Z_{12} + Z_{23} + Z_{31}}$$

similarly we can obtain,

$$Z_{12} = Z_1 + Z_2 + \frac{Z_1 Z_2}{Z_3}$$

$$Z_{23} = Z_2 + Z_3 + \frac{Z_2 Z_3}{Z_1}$$

$$Z_{31} = Z_3 + Z_1 + \frac{Z_3 Z_1}{Z_2}$$

In fact we can verify the result with the help of

$5 + j5 \parallel 5 - j5$


Let's follow next a different method.

Let's consider a circuit with two resistors.

A C.R. is connected across the two resistors.

30 | 9 | 22.

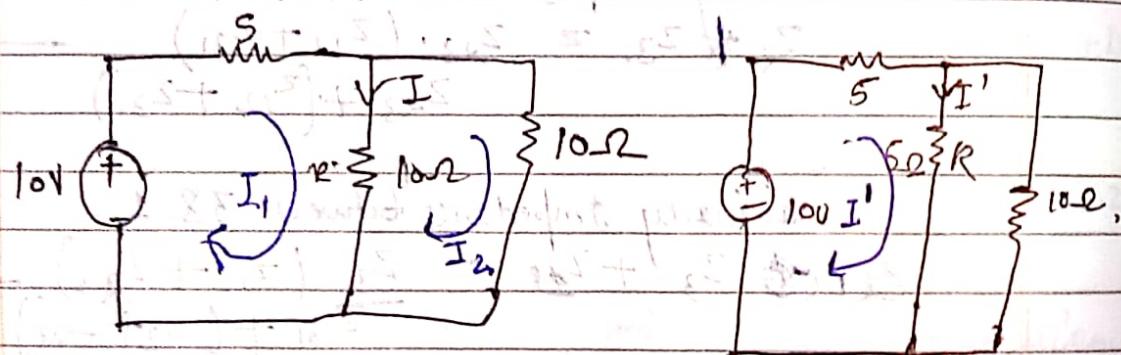Ques: The resistance R is changed from 10Ω to 5Ω . Verify Compensation Theorem.




$$-5I_1 - 10I_2 = 10 \quad (1)$$

$$-5(I_1 - I_2) - 10(I_2 - I_1) = 10.$$

93

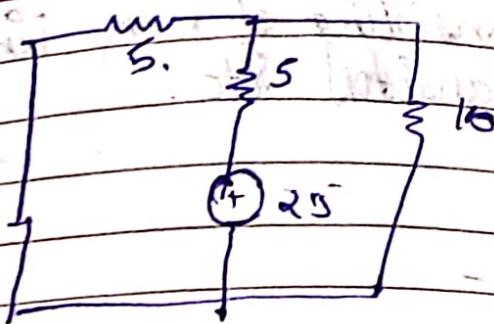1. Using compensating theorem,

$$V_C = I \cdot \Delta Z = 0.5 (-5) \\ = -2.5 V$$



$$\Delta I = 2.5$$


$$5 + 10 \\ \frac{5}{3}$$

$$2. 0.30 A.$$

Reciprocity Theorem → voltage

The ratio of excitation to response remains invariant in current

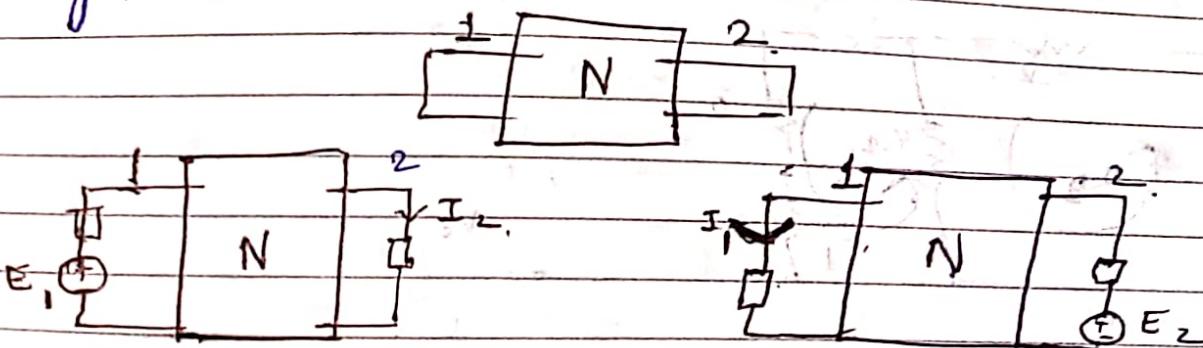a reciprocal network w.r.t interchange between the points of application of excitation and measurement of response.



E_1 in branch 1 produces current

I_2 in branch 2

E_2 is moved to branch 2

and response I_1 measured

The reciprocity theorem asserts that

$$E_1 = E_2$$

Reciprocity theorem indicates that V/I are mutually interchangeable. V/I is called transfer resistance (impedance).



Limitations-

Not applicable to networks consisting of any dependent source even if it is linear.

2. Not applicable to network consisting of any time varying element.

3. Not applicable to network consisting of non-linear elements like diode, transistor etc.

Ques Verify Reciprocity Theorem -

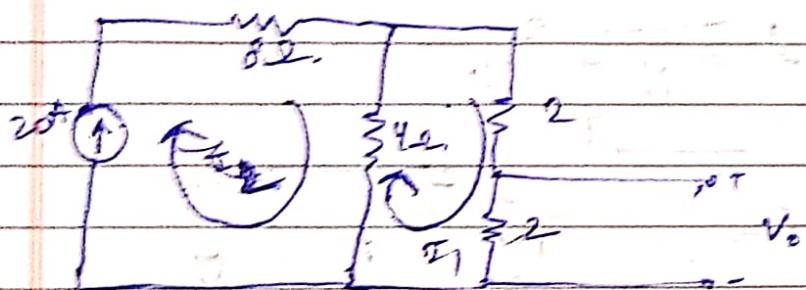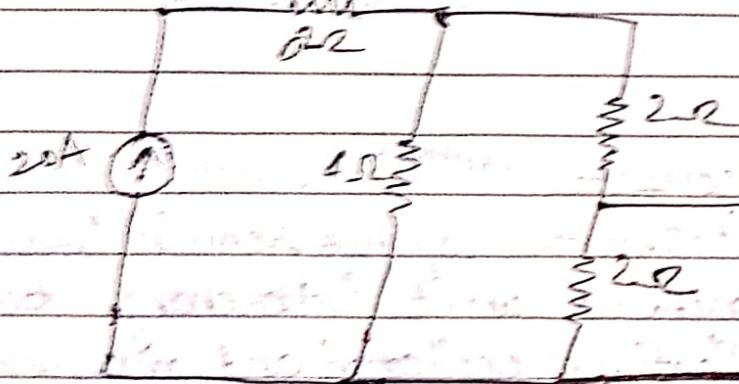

$$I_2 = 20 \text{ A}$$

$$-2I_1 - 4I_1 - 2I_1 =$$

$$-2I_1 - 4(I_1 - I_2) - 2I_1 = 0$$


$$-2I_1 - 4(20 - 2I_1) - 2I_1 = 0$$

$$-2I_1 - 4I_1 + 80 - 2I_1 = 0$$

$$-8I_1 = -80$$

$$I_1 = 10$$

$$V_0 = I_1 R \\ = 20V,$$

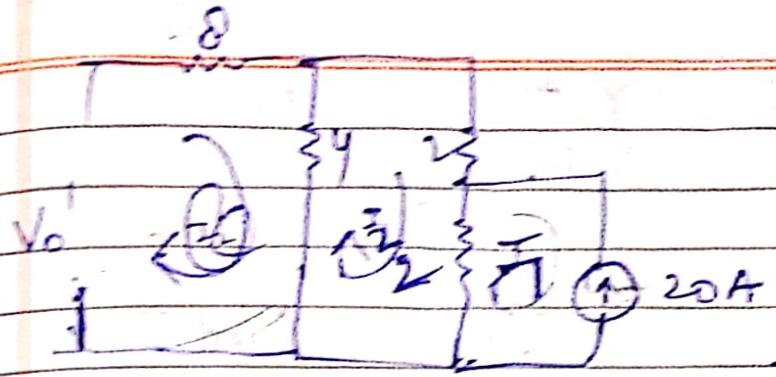

$$I_1 = 20$$

$$-4(I_2 - I_1) - 8 = 0$$

$$-4I_2 + 80 - 8 = 0$$

$$\Rightarrow -4I_2 + 72 = 0$$

$$\cancel{-4I_2} = \cancel{72}$$

$$\underline{\underline{I_2 = 18}}$$

$$\underline{\underline{I_2 = 18}}$$

~~$$-2I_2 - 6(I_2 - I_1) - 4I_2 = 0$$~~

~~$$-2I_2 - 2I_2 + 2I_1 - 4I_2 = 0$$~~

~~$$-2 \times 20 - 2I_2 + 2 \times 20 = 4I_2 = 0$$~~

~~$$-40 - 2I_2 + 40 = 4I_2 = 0$$~~

$$-2I_2 - 2(I_2 - I_1) - 4I_2 = 0$$

$$-2I_2 - 2I_2 + 40 - 4I_2 = 0$$

$$-8I_2 + 40 = 0$$

$$\underline{\underline{I_2 = 5}}$$



$$I_2 = 5$$

$$V_o = 4 \times 5$$

$$\boxed{V_o = 20 V}$$

$$\boxed{V_o = V_o'}$$

∴ Reciprocity theorem verified.

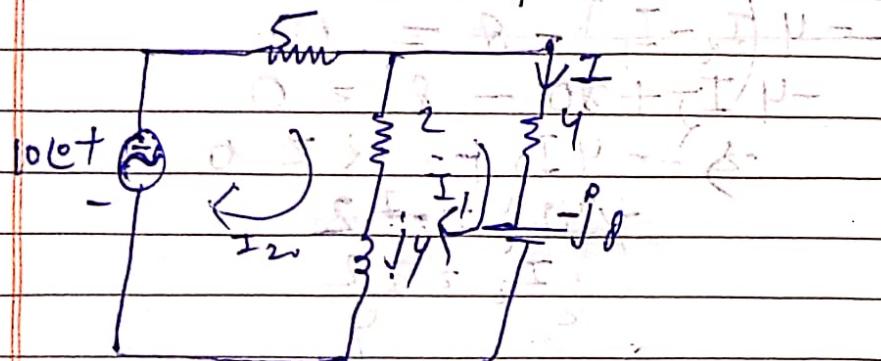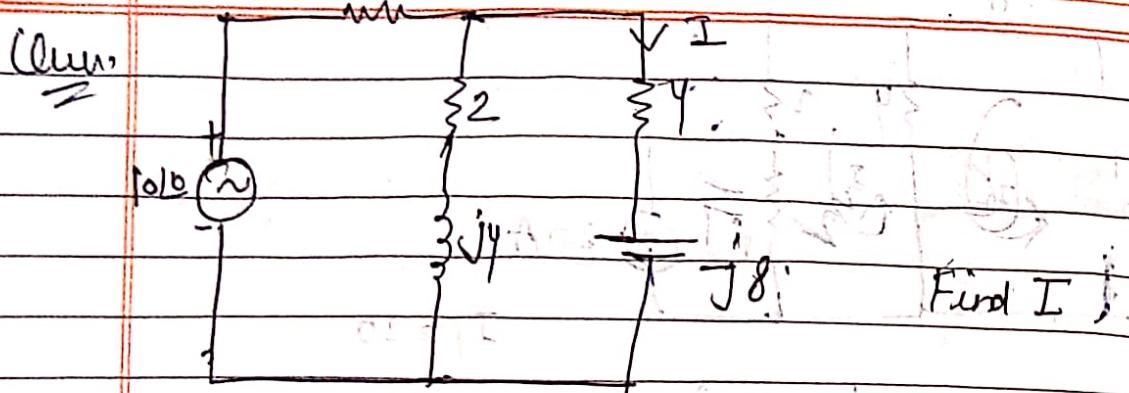

$$-j_1 I - 4I_1 - j_4(I_1 - I_2) - 2(I_1 - I_2) = 0$$

$$-4I_1 - j_8 I_1 - j_4 I_1 + j_4 I_2 - 2I_1 + 2I_2 = 0$$

$$-10I_1 + 5I_2 - 2(I_2 - I_1) - j_4(I_2 - I_1) = 0 \quad \textcircled{1}$$

$$-10 + 0j - 5I_2 - 2I_2 + 2I_1 - j_4I_2 + j_4I_1 = 0 \quad \textcircled{11}$$

from Eq $\textcircled{1}$ & $\textcircled{11}$

$$-4I_1 - j_8 I_2$$

$$-6I_1 - 12jI_1 + j_4I_2 + 2I_2 = 0$$

$$+ 2I_1 + j_4I_1 - j_4I_2 - 7I_2 = 0$$

$$-4I_1 - 8jI_1 - 5I_2 = -10$$

Current divided Rule -

$$Z_{eff} = (4-j8)(2+j4)$$

$$= (4-j8) + (2+j4)$$

$$= (4-j8)(2+j4)$$

$$(6-j4)$$

$$= V$$

$$\Rightarrow 8 \cdot 9 \cdot 4 | -63 \cdot 4 \times 4 \cdot 4 | 7 | 63 \cdot 4$$

$$Z_{eff} = 7 | 1 | 3 \cdot 9 \cdot 9 \cdot 6 | 6 | 7 | 1 | 3 \cdot 9 \cdot 9 \cdot 6$$

$$= 5.54 (33.6)$$

$$= 2 \text{ and } 0 =$$

$$I_s = \frac{V}{Z_{eff}}$$



Final answer is 5.54 A
and 0 A

TELLIGEN'S THEOREM

The summation of instantaneous power or summation of complex power of sinusoidal source in a network is zero. Mathematically,

$$\sum_{k=1}^b V_k I_k = 0$$


where b is the no. of branches in a network
while for complex power,

$$\sum_{k=1}^b V_k I_k^* = \sum_{k=1}^b S_k = 0 \text{ where } S = V_k I_k^* \\ = P + jQ,$$


Telligen's theorem is independent of circuit elements i.e., circuit having elements which are linear or non-linear, active or passive, time varying or time invariant. It is based on KVL & KCL.



PAGE NO.
DATE: / /

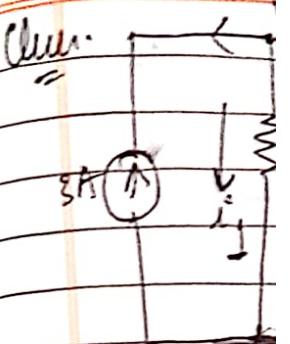

Ans.

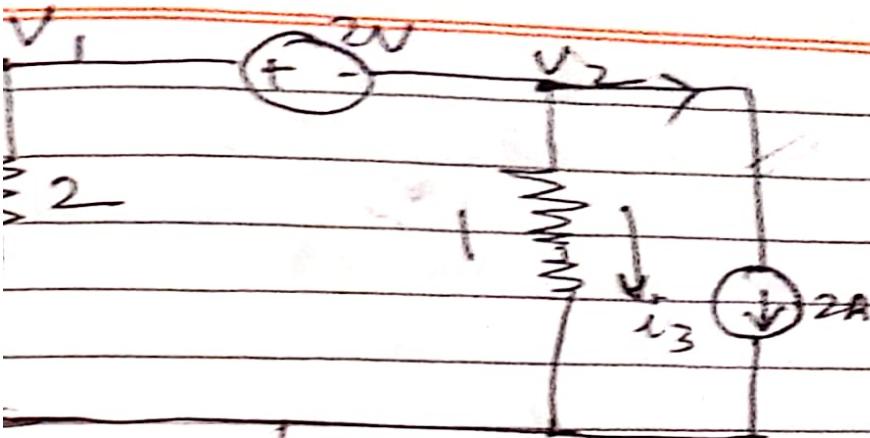

$$\frac{1}{2} i_1, i_3 = ?$$

node 1 & 2 are collectively called Super node.

$$\frac{V_1}{2} - 3 + \frac{V_2}{1} + 2 = 0 \quad \text{or}$$

$$\begin{aligned} V_1/2 + 2V_2 &= 2 \quad \text{--- (I)} \\ V_1 - V_2 &= 2 \quad \text{--- (II)} \\ V_1 + V_2 &= - \\ 3V_2 &= 0 \\ V_2 &= 0 \end{aligned}$$

Put $V_2 = 0$ in eq (I)


$$V_1 + 2(0) = 2$$

$$V_1 = 2$$

$$i_1 = \frac{V_1}{2}$$

$$i_3 = 0$$

$$i_1 = \pm 1$$

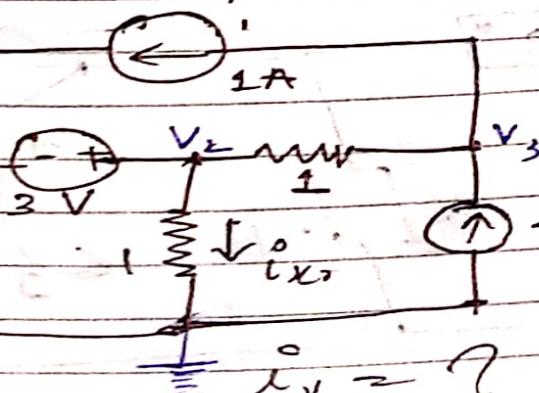

$$i_{12} = 2.5$$


$$i_{13} = 2.5$$

$$\frac{V_1}{1} - 1 + \frac{V_2}{1} + \frac{V_3 - V_1}{1} = 0$$

$$\frac{V_2 - V_3 + 2}{1} = 1 \rightarrow (\text{node 2})$$

$$V_2 - V_1 = 3 \rightarrow (\text{node 1})$$

\hookrightarrow (Ans)

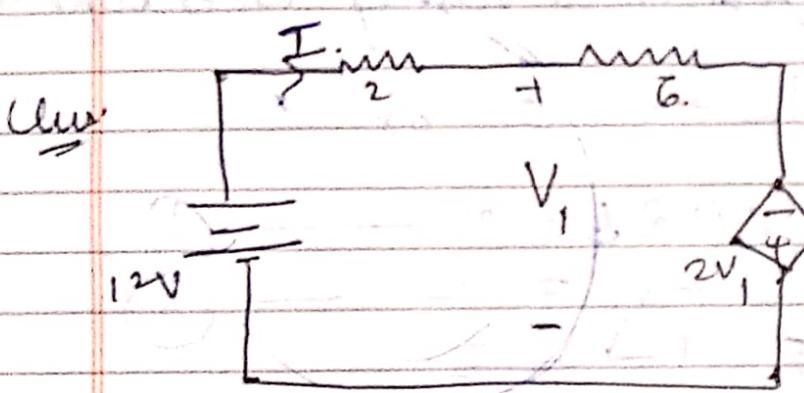


$$12 = 2I$$

$$-2I - V_1 + 12 = 0 \quad \text{--- (1)}$$

~~$$12 - 8I + 2V_1 = 0 \quad \text{--- (2)}$$~~

$$-8I + 2V_1 + 12 = 0 \quad \text{--- (1)}$$

$$III = -3 \quad I = 3A$$

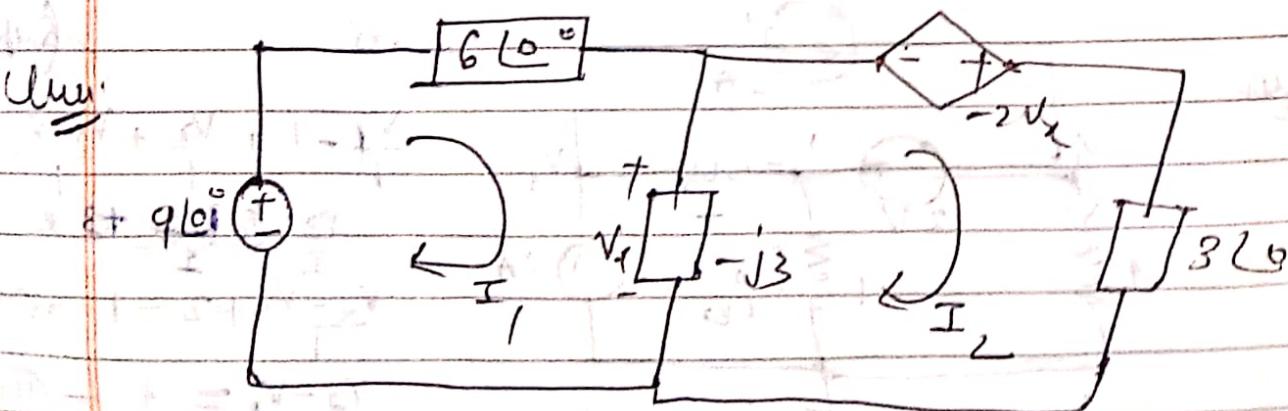

$$I_1 = 5 + 6j$$

$$I_2 = 1 + 2j \quad L = 16$$

$$I_1 + I_2 > ?$$


$$V_3 = -j_3(I_2 - I_1) \quad \text{--- (1)}$$

Mesh 1,

$$\begin{aligned} 10 - 6(0 + j_3(I_2 - I_1)) &= 0 + 0 \\ 9 - 6 + j_3(I_2 - I_1) &= 0 \\ 3 + j_3(I_2 - I_1) &= 0 \quad \text{--- (2)} \end{aligned}$$

Mesh 2,
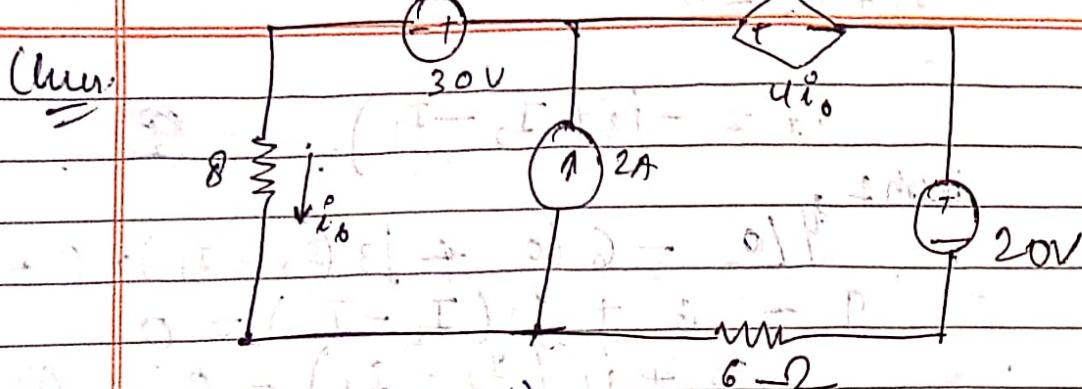
$$2(-j_3)(I_2 - I_1) - 3(0) - (j_3)(I_2 - I_1) = 0 \quad \text{--- (3)}$$




$$\begin{aligned}
 & (2 - i_0') \\
 & 8 \downarrow i_0' \quad 1 \uparrow 2A \quad -4i_0' \\
 & -4i_0' - 6(2 - i_0') + 8i_0'' = 0 \\
 & -4i_0' - 12 + 6i_0' + 8i_0'' = 0 \\
 & -12 + 2i_0' + 8i_0'' = 0 \\
 & 10i_0' = 12 \\
 & i_0' = 1.2A
 \end{aligned}$$

$$\begin{aligned}
 & 8 \downarrow i_0'' \quad 30V \quad 4i_0''' \\
 & +6 - \\
 & 30 - 4i_0'' + 6i_0''' + 8i_0'''' = 0 \\
 & 10i_0'''' = -30 \\
 & i_0'''' = -3A
 \end{aligned}$$

$$\begin{aligned}
 & 8 \downarrow i_0''' \quad 4i_0''' \\
 & +6 - \\
 & -4i_0''' - 20 + 6i_0''' \\
 & + 8i_0''' = 0 \\
 & 10i_0''' = 20 \\
 & i_0''' = 2A
 \end{aligned}$$

$$(I = 0.2)$$

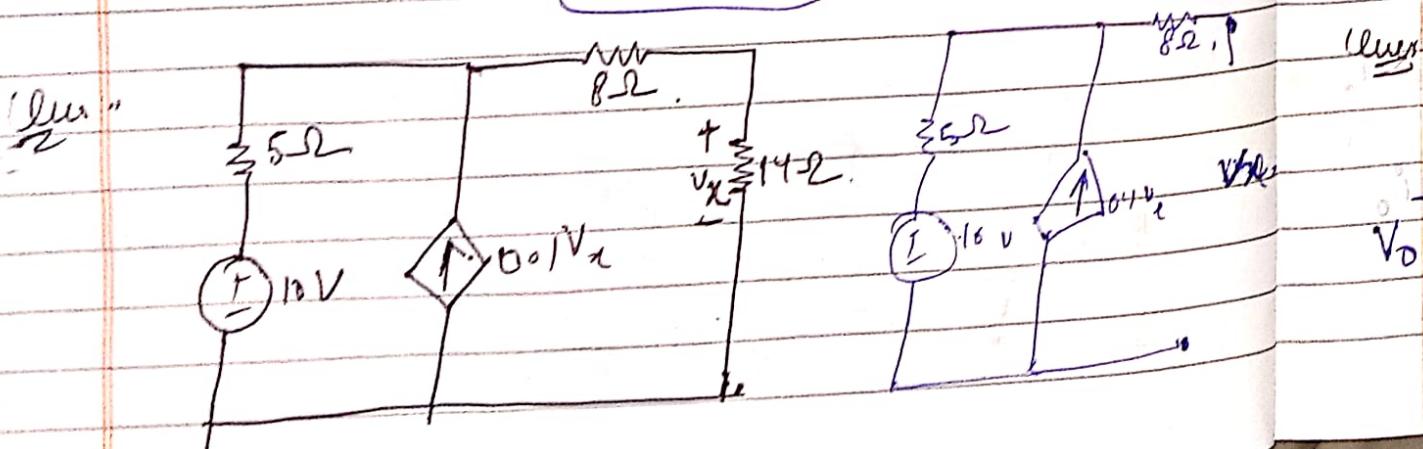

$$10 + 2 \cdot 5 V_x - V_x \geq 0$$

$$2 \cdot 5 V_x - V_x \geq -10.$$

$$10 \leq V_x \geq -10$$

$$R_N = \frac{V}{I_{SC}}$$

PAGE No. / DATE: / / 201

$$10 + 5(0.1 \cdot V_x) - V_x \geq 0$$


$$10 + 0.5 V_x - V_x \geq 0; \quad V_x > V_{TH} = V_{OC}$$

$$10 - 0.5 V_x \geq 0$$


$$0.5 V_x \geq 10$$

$$V_x = 20$$


$$\boxed{V_x = 20V}$$

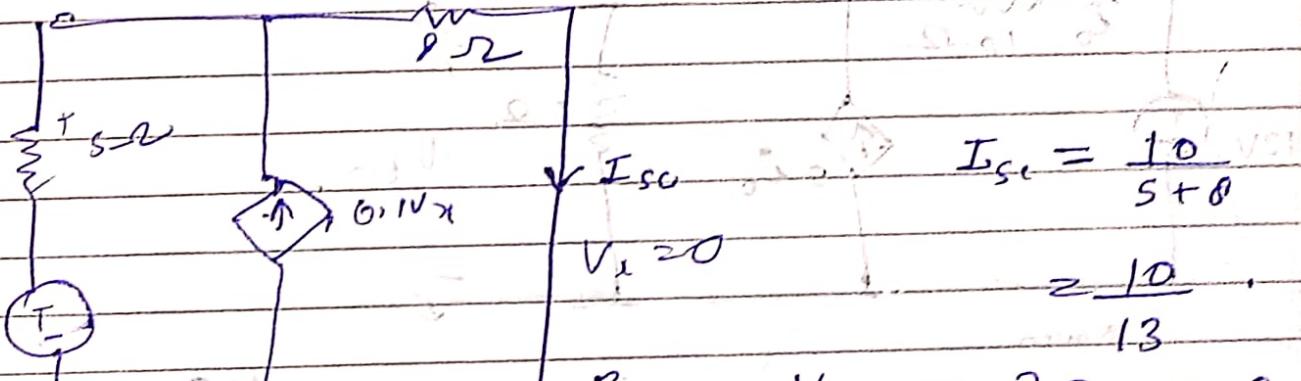
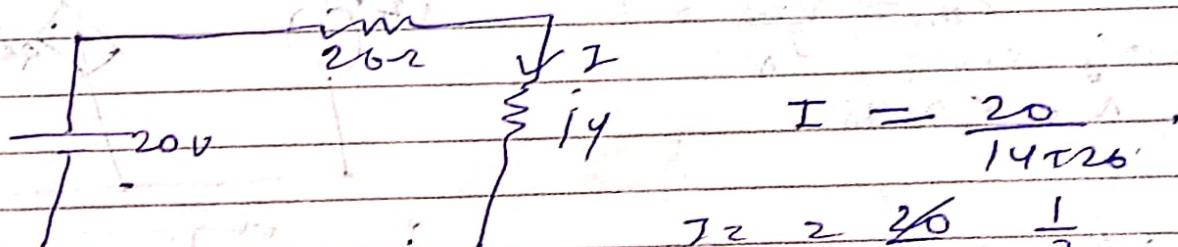
$$R_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{20}{10/13} = 26$$



$$(I = 0.5A)$$

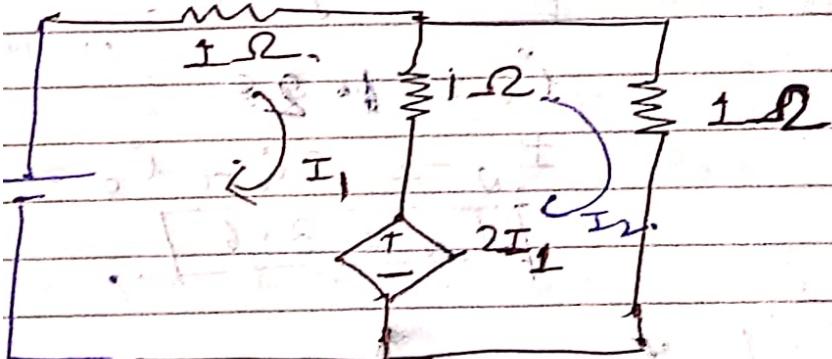

Thevenin
eq.
ckt.

when no independent source
is there then

$$\boxed{V_{TH} = 0}$$

R_{TH} :


$$V_o = i_1 - \frac{1}{2}(i_1 - i_2) - 2(i_1) = 0 \Rightarrow V_o = 4i_1 - 3i_2$$

$$\frac{1}{2}i_1 - \frac{1}{2}(i_2 - i_1) - i_2 = 0 \Rightarrow 3i_1 - 2i_2$$

$$\therefore V_o = 4i_1 - 3i_2$$

$$V_o = \frac{5}{2}i_1$$
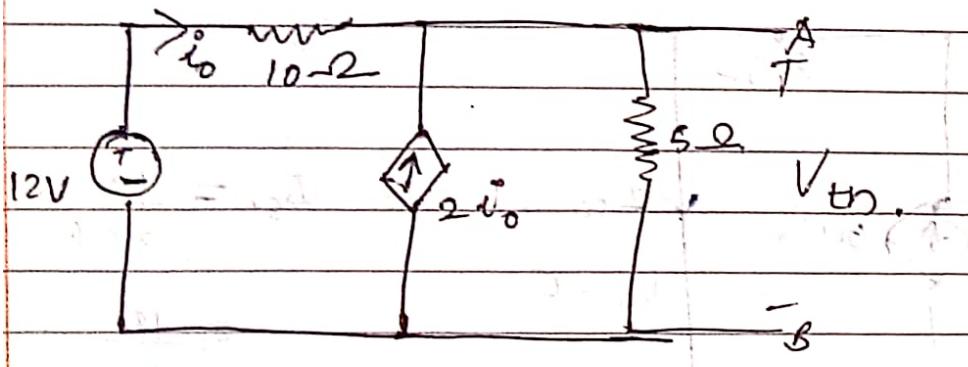
$$\boxed{\frac{V_o}{i_1} = \frac{5}{2} = R_{TH}}$$




Norton

$$I_N = 0$$

$$Z_N = \frac{V_{TH}}{I_N} = ?$$

$$2 - 10i_0 - 5i_0 = ?$$

$$i_0 = 0.48$$

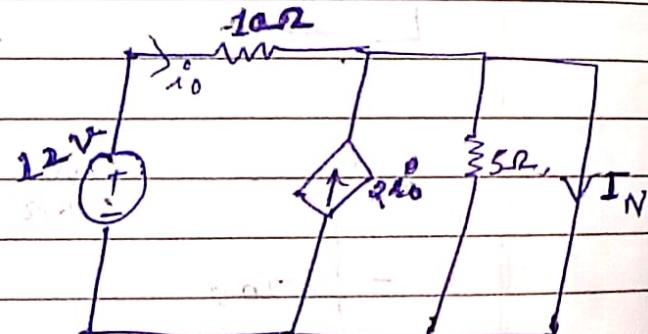


$$V_{TH} = V_{ss} = 5 \times 3i_0$$

$$= 8.66 \text{ V}$$

$$= 15 \times 0.41$$

$$= 7.2$$

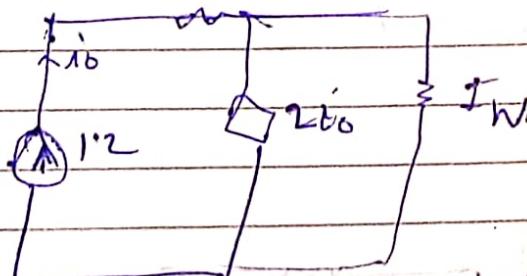

(1)

$$i_0 = 0.28$$

$$I_N = 2i_0 + i_0 = 3i_0$$

$$\boxed{I_N = 3.6}$$


$$\boxed{Z_{TH} = 2}$$

Unit-3

Fourier Series = Trigonometric & exponential

Any arbitrary periodic function can be represented as by an infinite series of sinusoidal at harmonic related frequencies. Periodic $f(x)$ can be represented as Fourier series and a periodic wave form of Fourier transform.

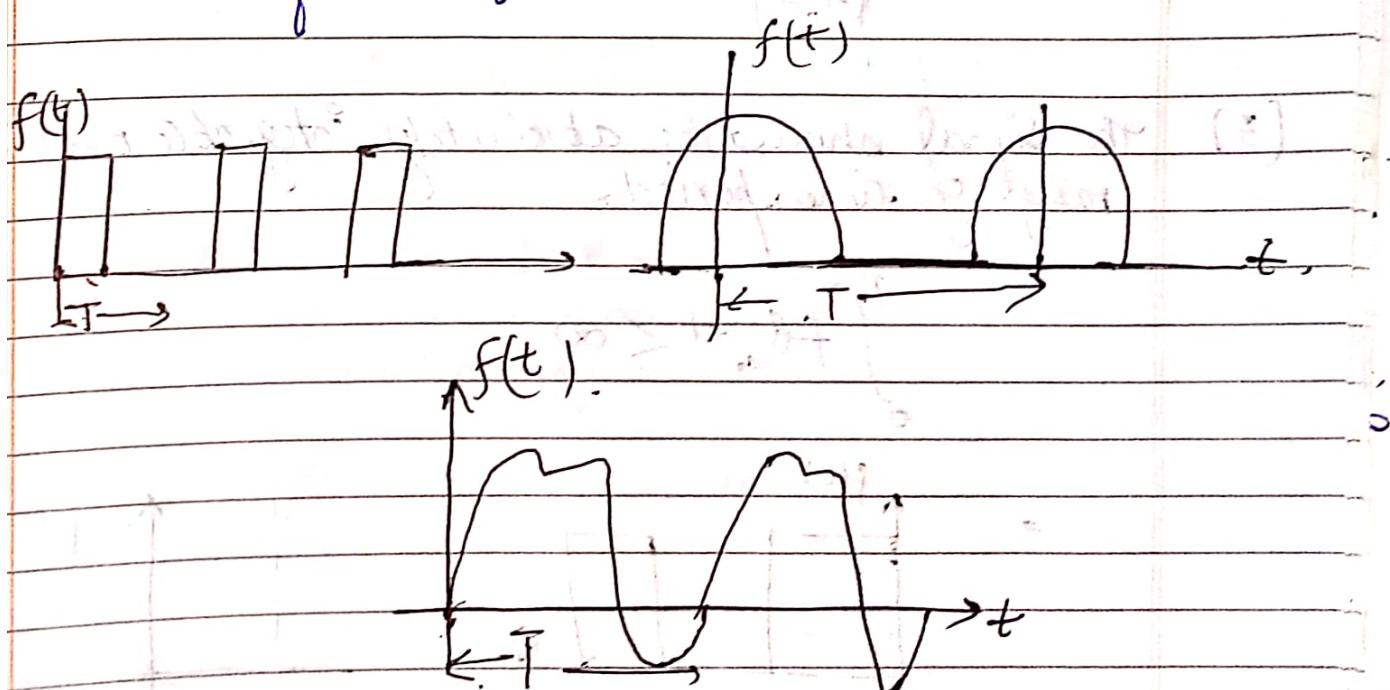A signal $f(t)$ is said to be periodic of period T if $f(t) = f(t + T)$.



Condition for existence of Fourier series \rightarrow Dirichlet's Condition.

A signal should have finite no. of discontinuities over the range of time period


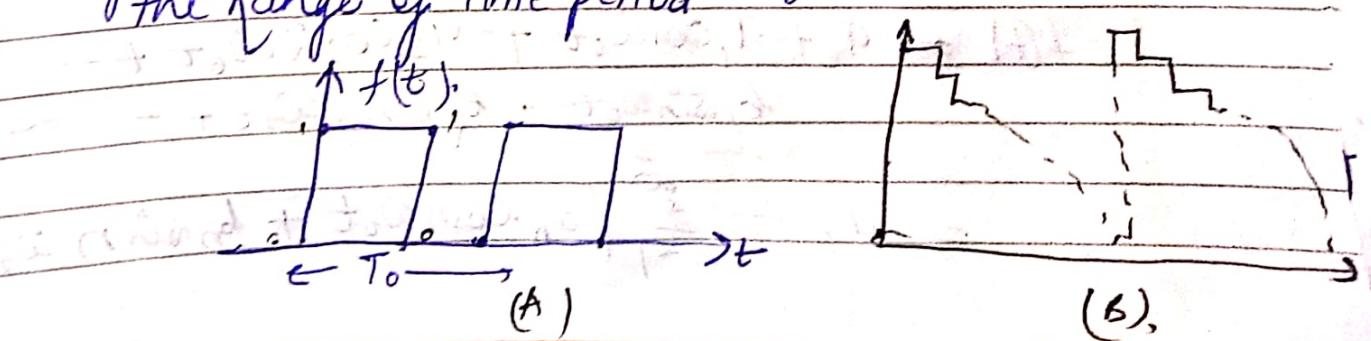



fig (A) can be determined by fourier series as discontinuous are finite in it. But fig (B) cannot be determined as infinite discontinuities are there.

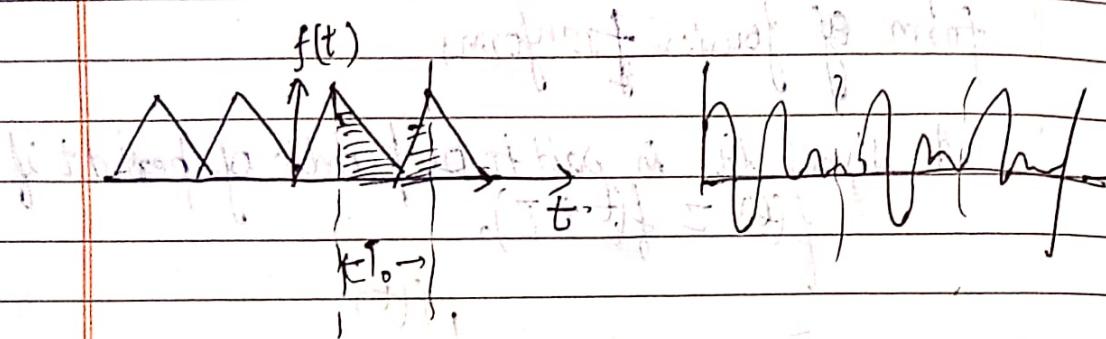- (2) The signal should have finite no. of maxima and minima over the range of time period



- (3) The signal should be absolutely integrable over the range of time period.

$$\int_{-\infty}^{\infty} |f(t)| dt < \infty$$

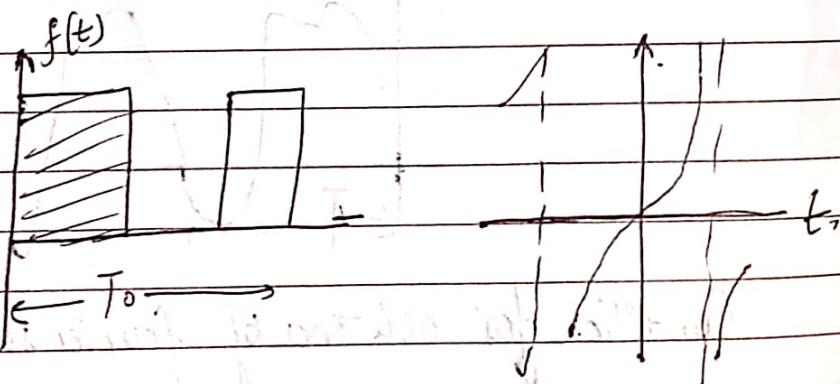

Trigonometric Fourier Series -

$$f(t) = a_0 + a_1 \cos \omega_0 t + a_2 \cos 2\omega_0 t + \dots + a_n \cos n\omega_0 t + b_1 \sin \omega_0 t + b_2 \sin 2\omega_0 t + \dots + b_n \sin n\omega_0 t$$


$$= a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

where, $a_0 = \frac{1}{T} \int_0^T f(t) dt$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt$$

$f(t)$

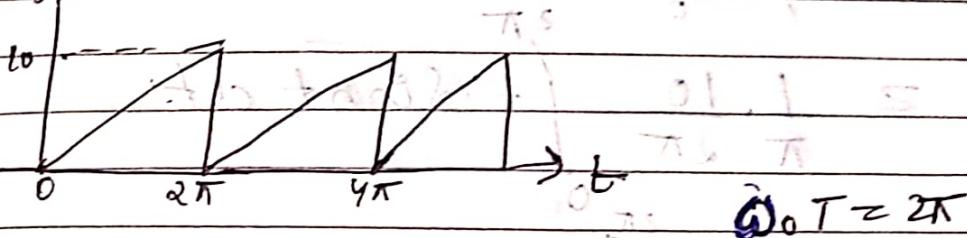

$$\omega_0 T = 2\pi$$

Time period = 2π

$$y = mx + c$$

$$f(t) = \frac{10}{2\pi} t + 0$$

$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} \frac{10}{2\pi} t dt$$

$$= \frac{1}{2\pi} \times \frac{10}{2\pi} \left[\frac{t^2}{2} \right]_0^{2\pi}$$

$$= \frac{10}{4\pi^2} \cdot \frac{4\pi^2}{2} = 5,$$

$$a_n = \frac{2}{2\pi} \int_0^{2\pi} \frac{10}{2\pi} t \cos nt dt$$

$$= \frac{2}{2\pi} \times \frac{10}{2\pi} \int_0^{2\pi} t \cos nt dt$$

$$= \frac{5}{\pi^2} \left[\frac{t(-\sin t)}{n} - \frac{1}{n^2} (\cos nt) \right]_0^{2\pi}$$

$$= \frac{5}{\pi^2} \left[-\text{const} t \right]_0^{2\pi}$$

$$= \frac{5}{\pi^2} \left[-\eta_2 + \frac{\eta_1}{n^2} \right]$$

$$= \frac{5}{\pi^2} [0] = 0,$$

$$\therefore b_n = \frac{1}{\pi} \int_0^{2\pi} (10 + 5 \sin nt) dt$$

$$= \frac{1}{\pi} \cdot \frac{10}{2\pi} \int_0^{2\pi} t dt$$

$$= \frac{5}{\pi^2} \int_0^{2\pi} t dt$$

$$= \frac{5}{\pi^2} \left[\frac{t^2}{2} \right]_0^{2\pi}$$


$$= \frac{5}{\pi^2} \left[\frac{(2\pi)^2}{2} \right] = 10\pi^2$$

$$= 10\pi^2$$

$$= 10 \cdot 3.14^2 = 98.6$$

$$= 314$$

$$= 314 \text{ units}^2$$

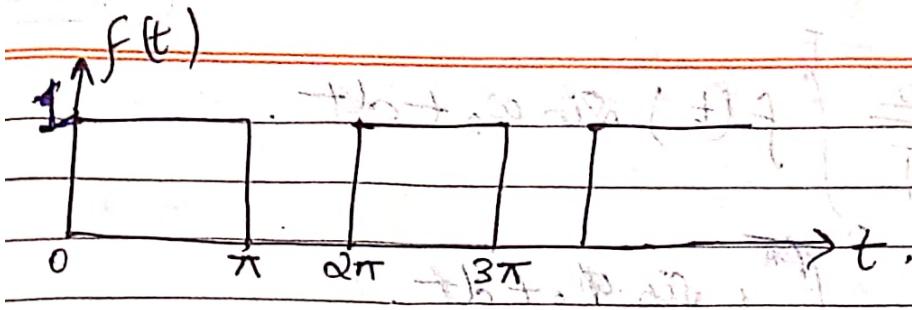

$$f(t) = \boxed{1} ; \quad f(t) = 1 \text{ for } 0 \text{ to } \pi.$$

$$a_0 = \frac{1}{T} \int_0^T f(t) dt, \quad \omega_0 = 1,$$

$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} 1 dt.$$

$$= \left[\frac{1}{2\pi} t \right]_0^{2\pi} = \frac{1}{2\pi} [2\pi] = 1$$

$$= \frac{1}{2\pi} \left[-t \right]_0^{2\pi} = \frac{1}{2\pi} [-2\pi] = \frac{1}{2}$$

$$a_n = \frac{2}{2\pi} \int_0^{2\pi} 1 \cos n(\frac{\pi}{2}) t dt.$$

$$a_n = \frac{1}{\pi} \int_0^{2\pi} \cos nt dt.$$

$$a_n = \frac{1}{\pi} \left[\frac{-\sin nt}{n} \right]_0^{2\pi}$$

$$= \frac{1}{\pi} \left[\frac{-\sin 2\pi}{2\pi} \right]_0^{2\pi}$$

$$= \frac{1}{\pi} \left[0 \right] = \boxed{a_n = 0}$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin \omega_0 t dt.$$

$$= \frac{2}{2\pi} \int_0^{\pi} \sin \omega_0 t dt,$$

$$= \frac{1}{\pi} \int_0^{\pi} \cos \omega_0 t dt$$

$$= \frac{1}{\pi} \int_0^{\pi} \cos n t dt$$

$$= \frac{1}{\pi} \left[\frac{\cos nt}{n} \right]_0^{\pi}$$

$$= -\frac{1}{n\pi} [\cos n\pi - \cos 0].$$

$b_n = 0$ when n is even

$n = 1$


$$f(t) = a_0 + a_1 \cos \omega_0 t + a_2 \cos 2\omega_0 t + \dots$$

with $t = \pi/2$)

$$= a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t)$$

$$= a_0 + \frac{1}{2} +$$

$f(t)$.

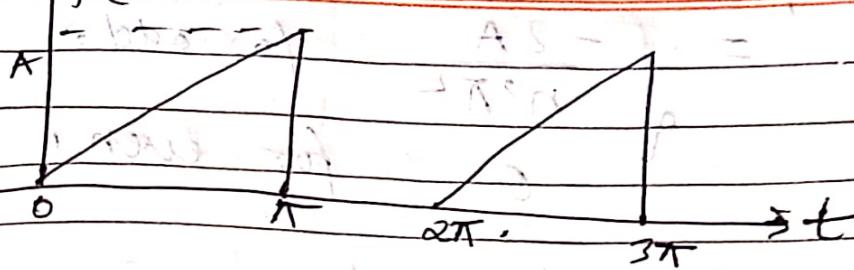

$$f(t) = \frac{A}{\pi}t \quad \text{for } 0 \leq t < \pi$$

$$0 \quad \text{for } \pi \leq t < 2\pi.$$

$$a_0 = \frac{1}{T} \int_0^T f(t) dt, \quad T = 2\pi$$

$$= \frac{1}{2\pi} \int_0^\pi \frac{A}{\pi} t dt$$

$$= \frac{1}{2\pi} \times \frac{A}{\pi} \left[\frac{t^2}{2} \right]_0^\pi$$

$$= \frac{1}{2\pi} \times \frac{A}{\pi} \times \frac{\pi^2}{2}$$

$$= \frac{A \pi^2}{4 \pi^2} = \frac{A}{4}$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt, \quad \omega_0 = \frac{\pi}{T}$$

$$= \frac{2}{2\pi} \int_0^\pi \frac{A}{\pi} t \cos nt dt$$

$$= \frac{1}{\pi} \times \frac{A}{\pi} \int_0^\pi t \cos nt dt$$

$$= \frac{1}{\pi} \times \frac{A}{\pi} \left[t \cdot \frac{-\sin nt}{n} \right]_0^\pi - \left[\frac{1}{n^2} \cos nt \right]_0^\pi$$

$$= \frac{A}{n^2 \pi^2} \left[(-1)^n - 1 \right]$$

~~odd~~

$$= \begin{cases} -\frac{2A}{n^2\pi^2} & \text{for odd,} \\ 0 & \text{for even.} \end{cases}$$

$$b_n = \frac{2}{T} \int_0^T f(t) \sin n\omega_0 t dt,$$

$$= \frac{2}{2\pi} \int_0^\pi A \cdot t \sin nt dt$$

$$= \frac{1}{\pi} \cdot \frac{A}{n} \int_0^\pi t \cdot \sin nt dt$$

$$= \frac{1}{\pi} \cdot \frac{A}{n} \left[t \cdot \left(\frac{\text{Const}}{n} \right) - \left(\frac{-\sin t}{n^2} \right) \right]_0^\pi$$

$$= \frac{A}{\pi n^2} \left[-it \cdot (-i)^n \right]$$

$$= -A(-i)^n$$

$$= -\frac{A}{n} \cdot \text{for even}$$


$$\frac{A}{n\pi} \text{ for odd}$$

$$\begin{aligned} b_n &= -\frac{A}{n} & A &= \frac{1}{\pi} \\ &= -\frac{C(1)}{n} & C &= \frac{1}{\pi} \end{aligned}$$

a_0 - giving the average value

PAGE No.

DATE: / /

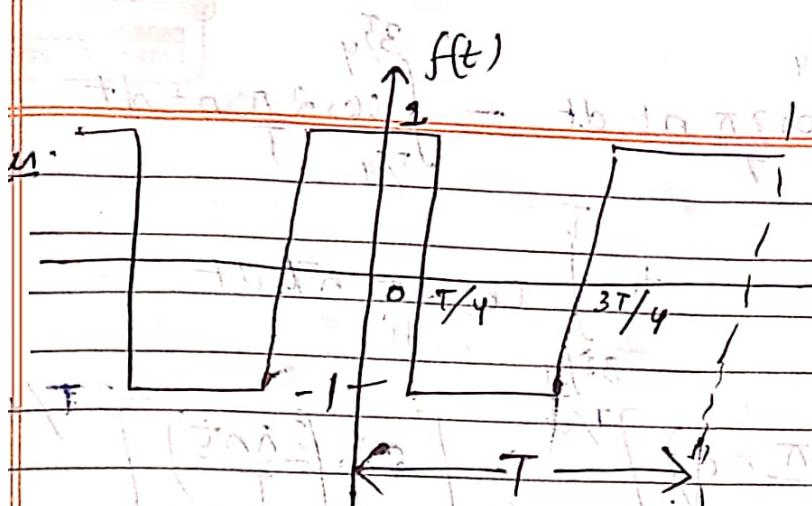

$$\omega_0 t = 2\pi$$

$$\omega_0 = \frac{2\pi}{T}$$

$$f(t) = 1 \quad \text{for } 0 \text{ to } T/4,$$

$$f(t) = -1 \quad \text{for } T/4 \text{ to } 3T/4$$

$$f(t) = 1 \quad \text{for } 3T/4 \text{ to } T,$$

$$a_0 = 0$$

↳ as the waveform is symmetric.

$$a_n = \frac{2}{T} \int_0^T f(t) \cos n\omega_0 t dt.$$

$$(A) \text{ and } a_n = \frac{2}{T} \left[\int_0^{T/4} \frac{1}{2} \cos n \frac{2\pi}{T} dt + \int_{T/4}^{3T/4} -1 \cos n \frac{2\pi}{T} dt \right]$$

$$+ \int_{3T/4}^T \frac{1}{2} \cos n \frac{2\pi}{T} dt.$$

$$a_n = \frac{2}{T} \left[\cancel{\frac{1}{n} \sin n \frac{2\pi}{T}} \Big|_0^{T/4} + \cancel{\frac{1}{n} \sin n \frac{2\pi}{T}} \Big|_{T/4}^{3T/4} \right] + \cancel{\frac{1}{n} \sin n \frac{2\pi}{T}} \Big|_{3T/4}^T + \cancel{\frac{1}{n} \sin n \frac{2\pi}{T}} \Big|_T^T$$

$$a_n \Rightarrow \frac{2}{T} \left[\frac{\sin(n \omega_0 \frac{T}{4})}{n} + \frac{\sin(n \omega_0 \frac{3T}{4})}{n} \right]$$

$$a_n = \frac{2}{T} \left[\int_0^{T/4} \cos \frac{2\pi}{T} nt dt - \int_{T/4}^{3T/4} \cos \frac{2\pi}{T} nt dt \right]$$

$$= \int_0^{T/4} \cos \frac{2\pi}{T} nt dt$$

$$= \frac{2}{T} \left[\left[\frac{\sin \left(\frac{2\pi}{T} nt \right)}{\frac{2\pi}{T} n} \right]_0^{T/4} - \left[\frac{\sin \left(\frac{2\pi}{T} nt \right)}{\frac{2\pi}{T} n} \right]_{T/4}^{3T/4} \right]$$

$$= \frac{2}{T} \left[\frac{\sin \left(\frac{2\pi}{T} n \cdot \frac{T}{4} \right)}{\frac{2\pi}{T} n} - \frac{\sin \left(\frac{2\pi}{T} n \cdot \frac{3T}{4} \right)}{\frac{2\pi}{T} n} \right]$$

$$= \frac{2}{T} \left[\frac{\sin \frac{2\pi n}{2}}{\frac{2\pi n}{T}} - \left[\frac{\sin \frac{3\pi n}{2}}{\frac{2\pi n}{T}} - \frac{\sin \frac{5\pi n}{2}}{\frac{2\pi n}{T}} \right] \right]$$

$$+ \left[\frac{\sin \frac{2\pi n}{2}}{\frac{2\pi n}{T}} - \frac{\sin \frac{3\pi n}{2}}{\frac{2\pi n}{T}} \right]$$

$$= T \left[\frac{1}{\pi n} \left[\sin \frac{\pi n}{2} - \sin \frac{3\pi n}{2} + \sin \frac{\pi n}{2} + \sin \frac{2\pi n}{2} + \sin \frac{3\pi n}{2} \right] \right]$$


$$= \frac{1}{\pi n} \left[2 \sin \frac{\pi n}{2} - 2 \sin \frac{3\pi n}{2} \right]$$

$$a_n = \frac{2}{\pi n} \left[\sin \frac{\pi n}{2} - \sin \frac{3\pi n}{2} \right]$$

$$n=1, a_1 = 4/\pi$$

$$n=2, a_2 = 0$$

$$n=3, a_3 = -4/3\pi$$

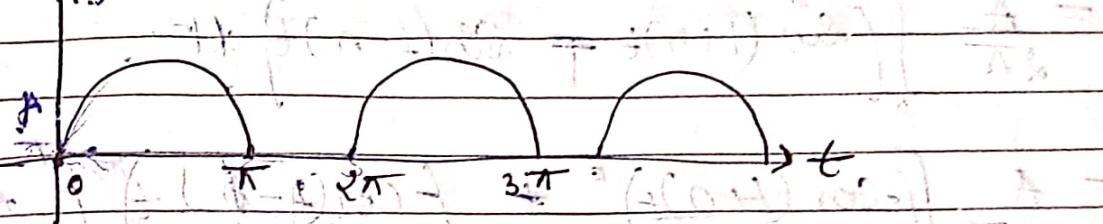$f(t)$ (time) period = 2π

$$\omega_0 T = 2\pi$$

$$(1+i\omega_0) \omega_0 = (1+i\omega_0)(\omega_0 -)$$

$$(1+i\omega_0) f(t) = A \sin t \text{ for } t \geq 0 \text{ on}$$

$$\begin{aligned} \sin A \cos B &= \frac{1}{2} [\sin(A+B) + \sin(A-B)] \\ (1+i\omega_0) (1+i\omega_0) (1+i\omega_0) &\quad \int dt \end{aligned}$$

$$a_0 = \frac{1}{T} \int_0^T f(t) dt$$

$$(1+i\omega_0) \frac{1}{2\pi} \int_0^{2\pi} A \sin t dt.$$

$$(1+i\omega_0) = \frac{1}{2\pi} A [-\cos t] \Big|_0^{2\pi}$$

$$= \frac{A}{2\pi} [(-1) - (-1)]$$

$$= \frac{A}{2\pi} [0] = \frac{A}{2\pi} f^2$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cos nt dt$$

$$= \frac{2}{2\pi} \int_0^{2\pi} A \sin t \cos nt dt$$

$$= \frac{A}{\pi} \int_0^{2\pi} \frac{1}{2} [\sin(1+n)t + \sin(1-n)t] dt$$

$$= \frac{A}{2\pi} \int_0^{\pi} (\sin((1+n)t) + \sin((1-n)t)) dt.$$

$$= \frac{A}{2\pi} \left[\left(-\cos((1+n)t) \right) \Big|_0^{\pi} + \left(\cos((1-n)t) \right) \Big|_0^{\pi} \right],$$

$$= \frac{A}{2\pi} \left[-\cos((n+1)\pi) - \cos((n-1)\pi) \right]$$

$$= \frac{A}{2\pi} \left[\frac{-(-1)^{n+1}}{(n+1)} + \frac{(-1)^{n-1}}{(n-1)} + \frac{1}{(n+1)} - \frac{1}{(n-1)} \right].$$

if $n = 2, 4, 6, \dots$ (even).

$$a_n = \frac{A}{2\pi} \left[\frac{-(-1)}{n+1} + \frac{(-1)}{n-1} + \frac{1}{(n+1)} - \frac{1}{(n-1)} \right].$$

$$= \frac{A}{2\pi} \left[\frac{1}{(n+1)} - \frac{1}{(n-1)} + \frac{1}{(n+1)} - \frac{1}{(n-1)} \right]$$

$$= \frac{A}{2\pi} \left[\frac{2}{(n+1)(n-1)} \right] = \frac{A}{2\pi} \times 2 \left[\frac{2}{n^2-1} \right]$$

$$a_n = \frac{A}{\pi} \left[\frac{-2}{n^2-1} \right]$$

$$\boxed{a_n = \frac{-2A}{\pi(n^2-1)}}$$

if $n = 1, 3, 5, \dots$ (odd)

$$= \frac{A}{2\pi} \left[-\frac{1}{(n+1)} + \frac{1}{(n-1)} + \frac{1}{(n+1)} - \frac{1}{(n-1)} \right]$$

$$\Rightarrow |a_n| = 0$$

$a_n = 0$, n is odd

$$= \frac{-2A}{\pi(n^2-1)}, n \text{ is even}$$

$$= (n-1) \sin t + (-1)^n$$

~~b_n~~

$$b_n = \frac{2}{\pi} \int_0^\pi f(t) \sin n\omega_0 t dt$$

$$= \frac{2}{\pi} \int_0^\pi A \sin t \sin nt dt$$

$$= \frac{A}{\pi} \int_0^\pi \sin nt \cdot \sin t dt$$

$$= \frac{A}{\pi} \int_0^\pi (\cos(n-1)t - \cos(n+1)t) dt$$

$$= \frac{A}{\pi} \left[\frac{\sin(n-1)t}{(n-1)} - \frac{\sin(n+1)t}{(n+1)} \right]_0^\pi$$

$$= \frac{A}{\pi} \left[\frac{\sin(n-1)\pi}{(n-1)} - \frac{\sin(n+1)\pi}{(n+1)} \right]_0^\pi$$

$$= |b_n| = 0$$

$$f(t) = \frac{A}{\pi} - \frac{2A}{\pi} \left[\frac{\cos \omega t + \cos 4\omega t + \cos 6\omega t}{(2^2 - 1)(4^2 - 1)(6^2 - 1)} \right]$$



Even Signal

- Remains identical under folding operation/time reversal

$$x(t) \xrightarrow{T.R} x(-t) = x(t)$$

e.g. $x(t) = \cos \omega t$.
 $t \rightarrow -t$.
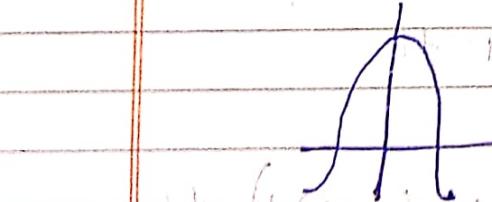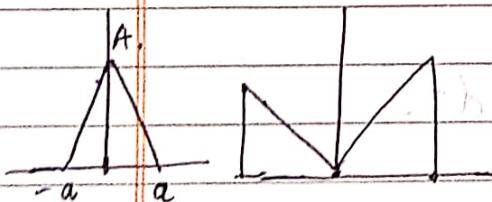
$$x(-t) = \cos(-\omega t) = \cos \omega t = x(t)$$



$$b_n = 0, \quad T/2$$

$$a_0 = \frac{2}{T} \int_0^{T/2} f(t) dt.$$

$$a_n = \frac{4}{T} \int_0^{T/2} f(t) \cos n\omega_0 t dt.$$

- Does not remain identical under folding $x(-t) = -x(t)$


$$x(t) = \sin(\omega t) +$$

$$x(-t) = \sin(-\omega t) = -\sin(\omega t) = -x(t).$$

Note -

- 1) Odd signal must be zero at $t = 0$.

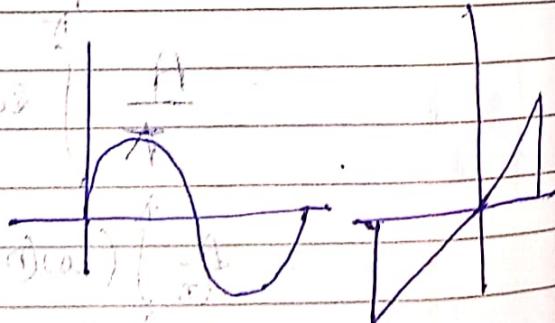- 2) Avg. or mean value of odd signal is zero.



$$a_0 = 0$$


$$a_n = 0,$$

$$b_n = \frac{4}{T} \int_0^{T/2} f(t) \sin n\omega_0 t dt.$$

$\sin(f+)$

$$\cos n\pi = (-1)^n$$

PAGE No. / DATE: / 201

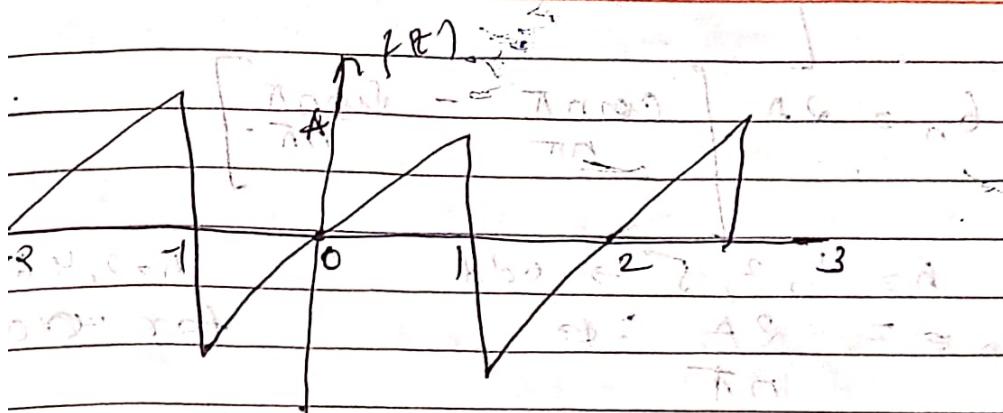

$$T = 2$$

$$\omega_0 T = 2\pi \quad ; \quad \omega_0 2 = 2\pi$$

is it is odd signal, $\int f(t) dt = A[t]$ $(\omega_0 = \pi)$
then, the value of a_0 & a_n is zero.

$$b_n = \frac{1}{2} \int_0^T A t \sin n\omega_0 t dt$$

$$= 2A \int_0^{\pi} t \cdot \sin n\pi t dt$$

$$= 2A \left[t \cdot \frac{\sin n\pi t}{n\pi} - \frac{1}{n\pi} \cdot \frac{\sin n\pi t}{n\pi} \right]_0^\pi$$

$$= 2A \left[t \cdot \frac{\cos n\pi t}{n\pi} - \frac{\sin n\pi t}{n\pi} \right]_0^\pi$$

$$= 2A \left[\frac{\cos n\pi}{n\pi} - \frac{\sin n\pi}{n\pi} \right] - 0 - 0$$

$$n\pi = 0 \Rightarrow$$

$$b_n = 2A \left[\frac{\cos n\pi}{n\pi} - \frac{\sin n\pi}{n\pi} \right]$$

$\omega \text{ Bn}$

$$b_n = 2A \left[\frac{\cos n\pi}{n\pi} - \frac{\sin n\pi}{n\pi} \right]$$

$n = 1, 3, 5 \rightarrow \text{odd}$

$$b_n = 2 \frac{2A}{n\pi} \quad \text{for odd,}$$


$n = 2, 4, 6 \rightarrow \text{even}$

for even,

$$b_n = -\frac{2A}{n\pi}$$

$$f(t) = A + \frac{2A}{\pi} \left[\sin \pi t - \frac{1}{3} \sin 3\pi t + \frac{1}{5} \sin 5\pi t - \dots \right]$$

Class

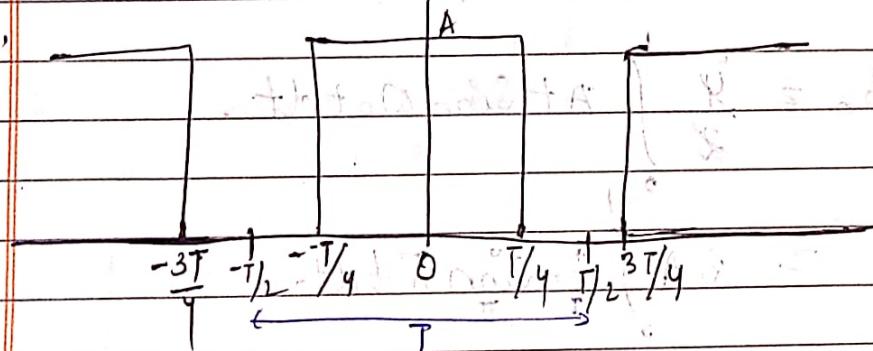

$$f(t) = A \quad T = T, \quad b_n = 0$$

Here, as this is an even function.

$$\therefore A_0 = \frac{1}{T} \int_0^T A dt = A$$

$$= 0 \quad \boxed{A_0 = A}$$

$$\frac{1}{2} \cdot 2A \times T = A$$

a_n

$$\boxed{a_0 = A}$$

$$\omega_0 T = 2\pi \quad -\sin \cos$$

$$\omega_0 = \frac{2\pi}{T}, \quad 1 \quad 201$$

$$a_n = \frac{4}{T} \int_0^{T/4} A \cos \omega_0 t dt$$

$$= \frac{4A}{T} \left[\cos \omega_0 t \right]_0^{T/4}$$

$$= \frac{4A}{T} \int_0^{T/4} \cos \omega_0 t dt$$

$$T = \frac{\pi}{\omega_0} \quad \Rightarrow \quad \frac{4A}{T} \int_0^{\pi/4} -\sin \frac{\pi}{n} t dt$$

$$= \frac{4A}{T} \int_0^{\pi/4} \cos \frac{\pi}{n} t dt$$

$$= \frac{4A}{T} \left[\frac{-\sin \frac{\pi}{n} t}{\frac{\pi}{n}} \right]_0^{\pi/4}$$

$$= \frac{4A}{T} \left[\frac{-\sin \frac{\pi}{n} t}{\frac{\pi}{n}} \right]_0^{\pi/4}$$

$$= \frac{4A}{T} \left[\frac{-\sin \frac{\pi}{n} t}{\frac{\pi}{n}} \right]_0^{\pi/4}$$


$$= \frac{4A}{T} \left[\frac{\sin \pi n}{\frac{\pi}{n}} \right]$$

$$= \frac{4A}{T} \left[\frac{\sin \pi n}{\frac{\pi}{n}} \right]$$

$$= 2A \sin \pi n \quad \Rightarrow \quad = \frac{2A \sin \pi n}{\frac{\pi}{n}}$$

$$a_1 = 2A, \quad a_2 = 0, \quad a_3 = -2A$$

Ans.

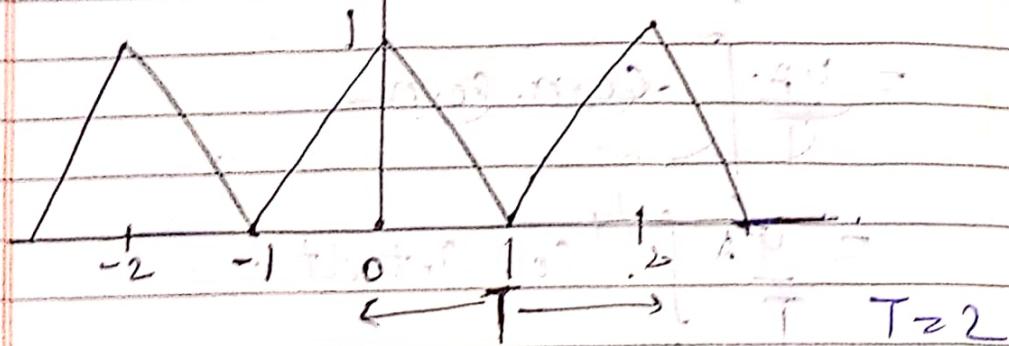

$$\omega_0 T = 2\pi$$

$f(t) = 1-t$. $\omega_0 = \pi$
as it is even signal, then, the
value of b_n is zero.

$$a_0 = \frac{3}{2} \int (1-t) dt$$

$$a_0 = \frac{3}{2} \int (1-t) dt$$

$$a_0 = \left[t - \frac{t^2}{2} \right] \Big|_0^1$$

$$a_0 = \left[1 - \frac{1}{2} \right] = \frac{1}{2}$$

$$a_0 = 1 - \frac{1}{2} \Rightarrow a_0 = \frac{1}{2}$$

$$a_n = \frac{4}{2} \int (1-t) \cos n\pi t dt$$

$$= 2 \int (1-t) \cos n\pi t dt$$

$$= 2 \int_0^1 \cos n\pi t - t \cos n\pi t dt$$

$$= 2 \int_0^1 \cos n\pi t - t \cos n\pi t dt$$

$$= 2 \int_0^1 \cos n\pi t - t \cos n\pi t dt$$

$$= 2 \left[\frac{\sin n\pi t}{n\pi} - t \cdot \frac{\sin n\pi t}{n\pi} + \frac{1}{n\pi} \cos n\pi t \right]_0^1$$

$$= 2 \left[\frac{\sin n\pi}{n\pi} - \frac{\sin n\pi}{n\pi} + \frac{\cos n\pi}{n\pi} - \frac{1}{n\pi^2} \right]$$

$$= 2 \left[\frac{\cos n\pi - 1}{(n\pi)^2} \right]$$

for even,

Half wave Symmetry \Leftrightarrow (only odd harmonic present)

$$f(t) = -f(t \pm T/2).$$


1) Perform time shifting:

$$f(t) \rightarrow f(t + T/2)$$

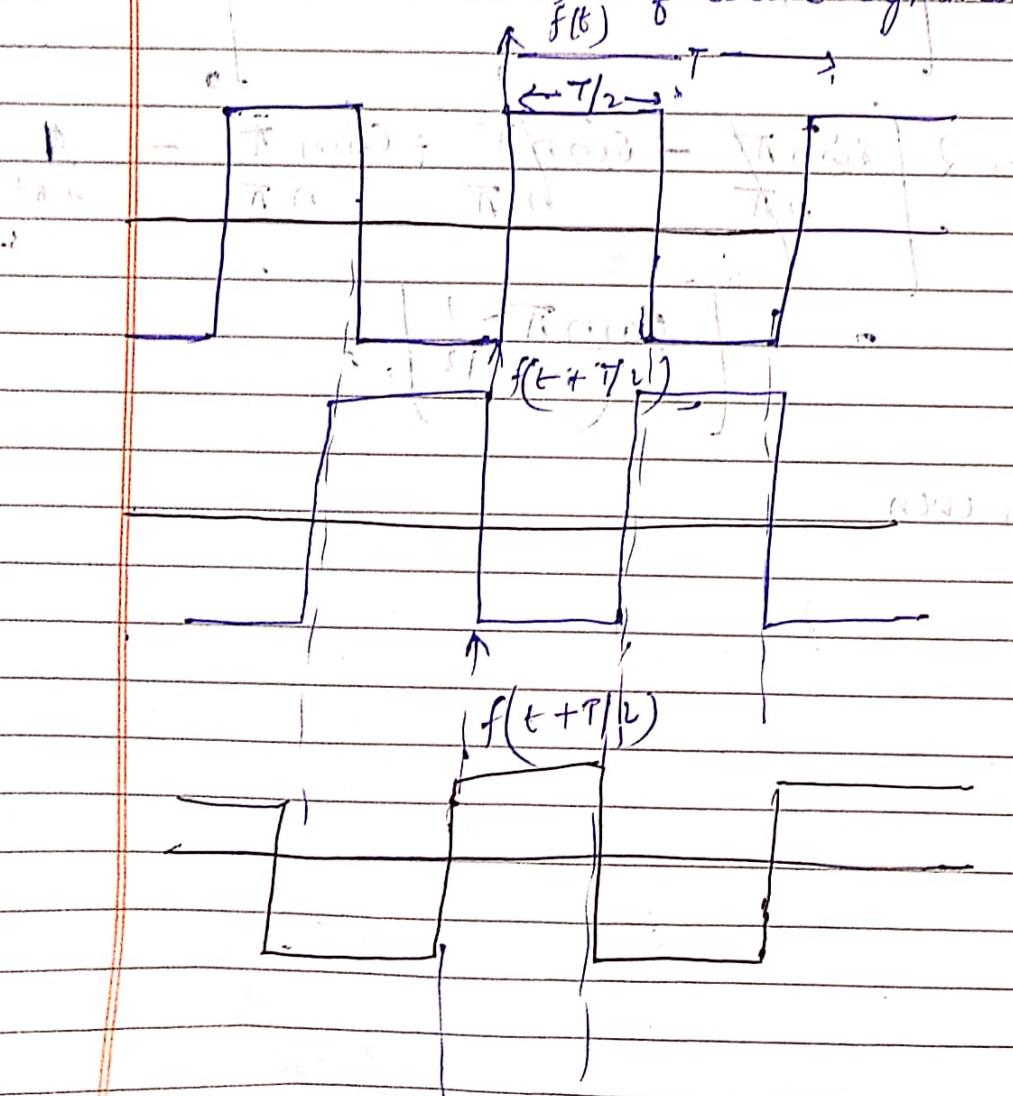2) Amplitude reversal:

$$f(t + T/2) \rightarrow -f(t + T/2),$$

If $-f(t + T/2)$ is same as $f(t)$, it is half wave symmetry.



Odd & HWS

odd

$$b_n \neq 0$$

$$a_n = 0$$

$$a_0 = 0$$

only sine term.

HWS.

only odd harmonics.

Only sine terms with odd harmonics.

Even & HWS

Even

$$a_n \neq 0$$

$$b_n = 0$$


only cosine terms,

HWS

only odd harmonics

Only Cosine terms with odd harmonics.

17/10/22

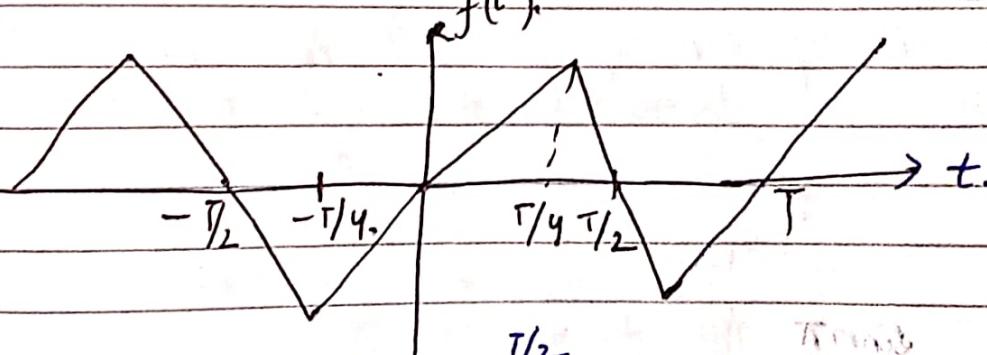

$$b_n = \frac{4}{\pi} \int_0^{T/2} f(t) \sin n \omega_0 t dt$$

$$\text{or } b_n = 2 \times \frac{4}{\pi} \int_0^{T/2} f(t) \sin n \omega_0 t dt$$

$$f(t) = \frac{y}{T} t.$$

$$\omega_0 T = 2\pi$$

$$\omega_0 = \frac{2\pi}{T},$$

$$b_n = \frac{2y}{T} \int_0^{T/2} \frac{y}{T} t \sin\left(\frac{2\pi}{T} t\right) dt$$

$$= \frac{y^2}{T^2} \int_0^{T/2} t \sin n \omega_0 t dt.$$

$$= \frac{y^2}{T^2} \left[t \cdot \left(-\frac{\cos n \omega_0 t}{n \omega_0} \right) - \left(\frac{\sin n \omega_0 t}{n^2 \omega_0^2} \right) \right]_0^{T/2}$$

$$= \frac{y^2}{T^2} \left[-I \cos \frac{2\pi}{T} t \right]_0^{T/2}$$

$$= \frac{y^2}{T^2} \left[-\frac{I}{2} \cos \frac{2\pi}{T} t - \left(\frac{\sin \frac{2\pi}{T} t}{n^2 \frac{4\pi^2}{T^2}} \right) \right]_0^{T/2}$$


$$b_n = \frac{I}{n^2 \pi^2} \frac{\sin n \pi}{2}$$

$$b_n = \frac{I}{n^2 \pi^2} \text{ for } n = 1, 5, 9, \dots$$

$$b_n = -\frac{I}{n^2 \pi^2} \text{ for } n = 3, 7, 11, \dots$$

$$f(t) = \frac{I}{2} \cos \omega_0 t + \frac{I}{4} \sin 5 \omega_0 t + \dots$$

$$f(t)$$

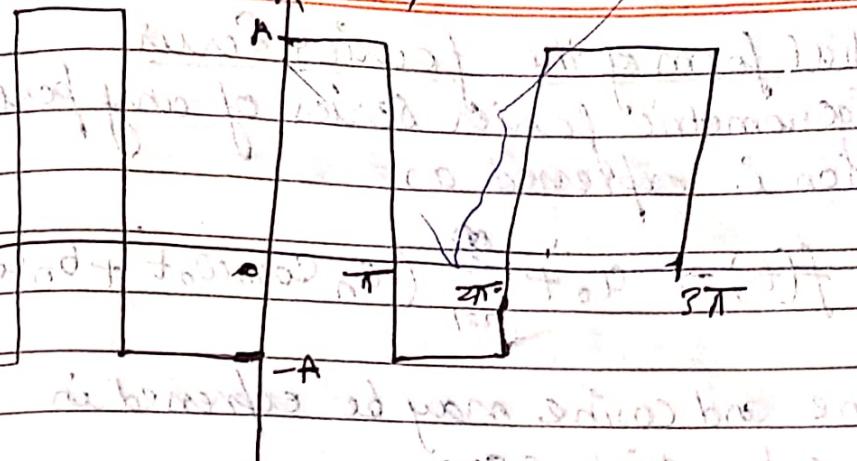

$$f(t) = A$$

$$\int_{-\pi}^{\pi} f(t) \sin n\omega_0 t dt. \quad \omega_0 = 2\pi/T.$$

$$b_n = A \int_{-\pi}^{\pi} \sin n\omega_0 t dt$$

$$= \frac{A}{2\pi} \int_{-\pi}^{\pi} -\cos n\omega_0 t dt$$

$$b_n = \frac{4}{T} \int_0^{\pi/2} A \sin n\omega_0 t dt$$

$$b_n = \frac{4A}{\pi} \int_0^{\pi/2} \sin n\omega_0 t dt$$

$$b_n = \frac{4A}{\pi} \left[-\frac{\cos n\omega_0 t}{n\omega_0} \right]_0^{\pi/2}$$

$$= \frac{4A}{\pi} \left[-\frac{\cos n\omega_0 \pi/2}{n\omega_0} \right]_0^{\pi/2}$$

$$= \frac{4A}{\pi n} \left[-\cos n\omega_0 \pi/2 \right]_0^{\pi/2} = \frac{4A}{\pi n}.$$

Exponential form of the Fourier Series

The trigonometric Fourier series of any periodic function is expressed as

$$f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega_0 t + b_n \sin n\omega_0 t) \quad \text{---(1)}$$

The sine and cosine may be expressed in terms of exponentials as

$$\cos n\omega_0 t = \frac{1}{2} (e^{jn\omega_0 t} + e^{-jn\omega_0 t})$$

$$\sin n\omega_0 t = \frac{1}{2j} (e^{jn\omega_0 t} - e^{-jn\omega_0 t}).$$

Substituting the above expressions in eq (1)

$$f(t) = a_0 + \sum_{n=1}^{\infty} \left[a_n \cdot \frac{e^{jn\omega_0 t} + e^{-jn\omega_0 t}}{2} + b_n \cdot \frac{e^{jn\omega_0 t} - e^{-jn\omega_0 t}}{2j} \right]$$

In order to simplify this eq, like exponential terms are grouped, also $1/j = -j$

$$f(t) = a_0 + \sum_{n=1}^{\infty} \left[\left(\frac{a_n - jb_n}{2} \right) e^{jn\omega_0 t} + \left(\frac{a_n + jb_n}{2} \right) e^{-jn\omega_0 t} \right]$$

To simplify this expression, a new coeff is introduced to replace a & b .

$$\bar{c}_n = \frac{a_n - jb_n}{2}, \bar{c}_{-n} = \frac{a_n + jb_n}{2}, c_0 = a_0.$$

The new form of eq is,

$$f(t) = \bar{c}_0 + \sum_{n=1}^{\infty} (\bar{c}_n e^{jn\omega_0 t} + \bar{c}_{-n} e^{-jn\omega_0 t})$$

Letting n take values from 1 to ∞ in this eq is equivalent to letting n range from $-\infty$ to ∞ (including zero) is compact eq.

$$f(t) = \sum_{n=-\infty}^{\infty} C_n e^{jn\omega_0 t}$$

The coeff \bar{C}_n can be easily evaluated in terms of a_n & b_n . Substituting the expression of a_n & b_n in the expression of \bar{C}_n

$$\bar{C}_n = a_n - j b_n, \text{ sub, } a_n = \frac{1}{T} \int_0^T f(t) \cos n\omega_0 t$$

$$+ b_n = \frac{1}{T} \int_0^T f(t) \sin n\omega_0 t$$


$$\bar{C}_n = \frac{1}{T} \int_0^T f(t) \cos n\omega_0 t dt = j \frac{1}{T} \int_0^T f(t) \sin n\omega_0 t dt$$

$$= \frac{1}{T} \int_0^T f(t) (\cos n\omega_0 t - j \sin n\omega_0 t) dt$$

$$\bar{C}_n = \frac{1}{T} \int_0^T f(t) e^{-jn\omega_0 t} dt$$

Exponential form has certain advantages over trigonometric form: Only one integral is exponential, simpler integration.

$$\text{Clue- } f(t)$$

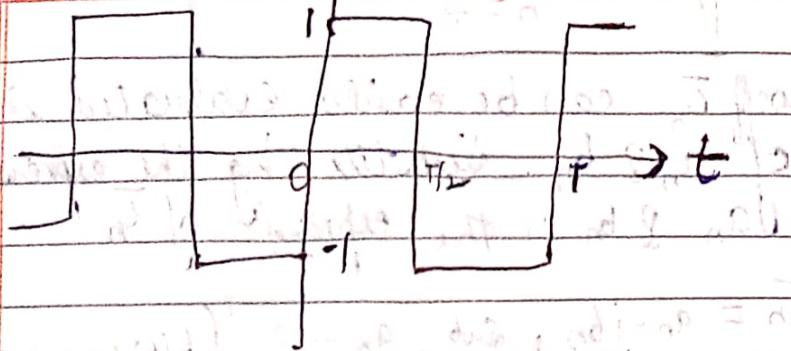

$$f(t) = 1 \quad \text{for } 0 < t < T/2$$

$$f(t) = -1 \quad \text{for } T/2 < t < T.$$

\bar{C}_n will be imaginary

$$\bar{C}_n = \frac{1}{T} \int_0^T f(t) e^{-jn\omega_0 t} dt$$

$$\begin{aligned} \bar{C}_n &= \frac{1}{T} \int_0^{T/2} 1 \cdot e^{-jn\omega_0 t} dt + \frac{1}{T} \int_{T/2}^T (-1) e^{-jn\omega_0 t} dt \\ &= \frac{1}{T} \left[\frac{e^{-jn\omega_0 t}}{-jn\omega_0} \right]_0^{T/2} + \frac{1}{T} \left[\frac{(-1)e^{-jn\omega_0 t}}{-jn\omega_0} \right]_{T/2}^T \end{aligned}$$

$$= \frac{1}{-jn\omega_0} \left[e^{-jn\omega_0 T/2} - e^0 \right]$$

$$= \frac{1}{-jn\omega_0} \left[-e^{-jn\omega_0 T} - e^{-jn\omega_0 T/2} \right]$$

$$\omega_0 T = 2\pi$$

$$e^{-jn\omega_0 T} = e^{-jn2\pi} = \cos 2\pi - j \sin 2\pi = 1$$

$$e^{-jn\omega_0 T/2} = e^{-jn\pi} = \cos \pi - j \sin \pi = (-1)^n$$

Hence,

$$\bar{C}_n = \frac{1}{-jn\omega_0} \left[(-1)^n - 1 \right] + \frac{1}{jn2\pi} \left[1 - (-1)^n \right]$$

$$= \frac{1}{j\pi 2\pi} \left[-(-1)^n + 1 + 1 - (-1)^n \right]$$

$$= \frac{1}{j\pi 2\pi} \left[2 - 2(-1)^n \right] = \frac{2}{j\pi 2\pi} \left[1 - (-1)^n \right]$$


$$\bar{c}_n = \frac{2}{j\pi n}, \text{ odd } n$$

$$\bar{c}_n = 0, \text{ even } n.$$

$$\bar{c}_0 = \frac{1}{T} \int_0^T f(t) dt = 0$$

Exponential Fourier series
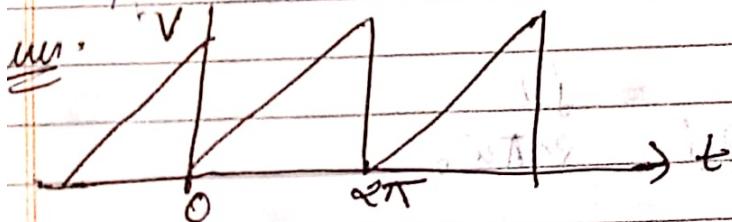
$$f(t) = \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t} = \frac{2}{\sqrt{\pi}} \sum_{n=-\infty}^{\infty} \frac{1}{n} e^{jn\omega_0 t}$$



$$f(t) = \frac{V}{\pi} [t - \lfloor \frac{t}{2\pi} \rfloor + \pi] = \frac{V}{\pi} t$$

$$\bar{c}_n = \frac{1}{T} \int_0^T f(t) e^{-jn\omega_0 t} dt$$

$$\bar{c}_n = \frac{V}{j\pi n} \int_0^{2\pi} \left(\frac{t}{2\pi} \right) e^{-jn\omega_0 t} dt$$

$$\bar{c}_n = \frac{V}{(2\pi)^2} \int_0^{2\pi} t^n dt$$

$$c_0 = \frac{V}{(2\pi)^2} \left[\int_0^{2\pi} t^2 e^{-j\omega_0 t} dt \right]$$

$$\int_0^{2\pi} t^2 e^{-j\omega_0 t} dt = 0$$

$$= \frac{V}{2} = 0.5V$$

$$c_n = \frac{V}{(2\pi)^2} \left[\int_0^{2\pi} t \cdot e^{-j\omega_0 t} dt \right] = \int_0^{2\pi} t \cdot e^{-j\omega_0 t} dt$$

$$= \frac{V}{(2\pi)^2} \int_0^{2\pi} t \cdot e^{-j\omega_0 t} dt$$

$$= e^{-j\theta} = \cos \theta - j \sin \theta$$

$$e^{-j2n\pi} = \cos 2n\pi - j \sin 2n\pi = 1.0 = 1$$

$$c_n = \frac{V}{(2\pi)^2} \left[\frac{2\pi}{j\omega_0} + \frac{1}{n\omega_0} - \frac{1}{n^2\omega_0^2} \right]$$

$$= -\frac{V}{2\pi n \omega_0 j}$$

$$= \frac{jV}{2\pi n \omega_0}$$

$$\omega_0 T = 2\pi \Rightarrow T = 2\pi / \omega_0$$

$$c_n = \frac{jV}{2\pi n}$$

$$f(t) = \sum_{n=-\infty}^{\infty} c_n e^{jn\omega_0 t} = \sum_{n=-\infty}^{\infty} \left(\frac{jV}{2\pi n} \right) e^{jn\omega_0 t}$$

$$f(t) = \sum_{n=-1}^{\infty} \left(\frac{jV}{2\pi n} \right) e^{jn\omega_0 t} = jV \sum_{n=1}^{\infty} \frac{1}{n} e^{jn\omega_0 t} + jV \sum_{n=0}^{\infty} \frac{1}{n} e^{jn\omega_0 t}$$

$$f(t) = \frac{V}{2} + \sum_{n=1}^{\infty} \left(\frac{-V}{n\pi} \right) \sin(n\omega_0 t)$$

$$f(t) = \frac{V}{2} - \frac{V}{\pi} \left(\sin t + \sin \frac{2}{1} t + \sin \frac{3}{3} t \right)$$

$$\omega_0 = \frac{V}{L}$$

PAGE NO. / 201

DATE: / /

- (Anscombe's form)

Trigonometric form from exponential form-

$$a_n = \bar{c}_n + \bar{c}_n^*$$

$$b_n = j(-\bar{c}_n - \bar{c}_n^*)$$

$$a_0 = c_0$$

$$\text{and } a_n = \frac{jV}{2n\pi} e^{jn\omega_0 t} = jV \neq 0$$

$$b_n = j \left(\frac{-jV}{2n\pi} - \left(\frac{-jV}{2n\pi} \right)^* \right) = j \left(\frac{2jV}{n\pi} \right)$$

$$\frac{2jV^2}{n\pi} = \frac{jV^2}{n\pi}$$



$$a_n = \frac{-V}{n\pi}$$

$$a_0 =$$

Amplitude Spectrum-

$$|\bar{c}_n| = \sqrt{\operatorname{Re}(\bar{c}_n) + \operatorname{Im}(\bar{c}_n)}$$
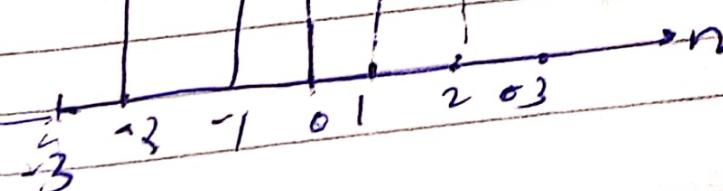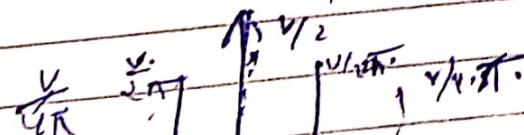
$$= \sqrt{0^2 + \left(\frac{V}{n\pi} \right)^2} = \frac{V}{n\pi}$$



Phase spectrum -

$$c_n = jv \text{ for } n \neq 0$$

$$\phi = \tan^{-1} \left[\frac{\text{Im}[c_n]}{\text{Re}[c_n]} \right]$$

$$n=1, c_1 = \frac{jv}{2\pi}$$


$$n=-1, c_{-1} = -\frac{jv}{2\pi}$$

$$\phi = \tan^{-1} \left[\frac{jv}{2\pi} \right]$$

$$\text{and } \phi = \tan^{-1} \left[\frac{jv}{2\pi} \right]$$


$$\phi = \tan^{-1}[\infty] \text{ or } \tan^{-1}[-\infty]$$
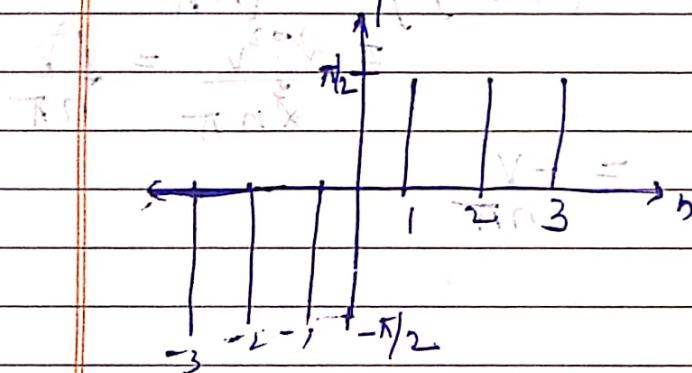
$$\phi \geq \pi/2 \Rightarrow \phi = -\pi/2.$$



$$(j+1)Y_{out} + (j^2 + j)Z_{out} = jW_{out}$$
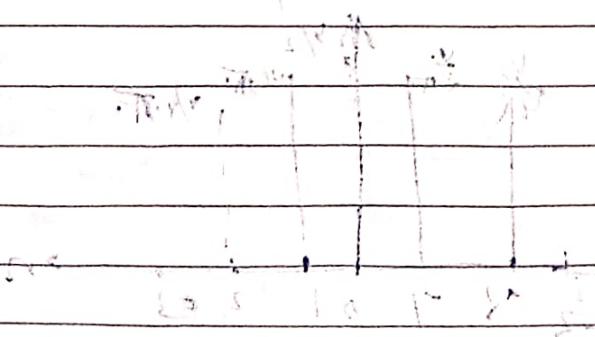
$$V = \begin{bmatrix} j+1 & 0 \\ j^2 + j & 0 \end{bmatrix} =$$



PAGE NO.
DATE: / / 2020


Fourier transform -

$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega,$$

Class $f(t) = e^{-at} u(t) \quad a > 0.$
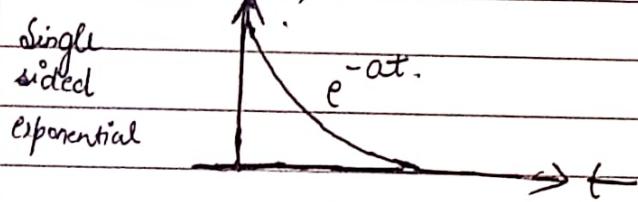
$$\begin{cases} e^{-\infty} = 0 \\ e^{\infty} = \infty \\ e^0 = 1 \end{cases}$$



$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_0^{\infty} e^{-at} e^{-j\omega t} dt$$

$$= \int_0^{\infty} e^{-(a+j\omega)t} dt$$

$$= -\frac{1}{a+j\omega} e^{-(a+j\omega)t} \Big|_0^{\infty}$$

$$= -\frac{1}{a+j\omega} [e^{\infty} - e^0]$$

$$F(j\omega) = \frac{1}{a+j\omega}$$

Amplitude Spectrum -

$$|F(j\omega)| = \sqrt{a^2 + \omega^2}$$


at $\omega = 0$, $|F(j\omega)| = \frac{1}{a}$


at $\omega = \infty$, $|F(j\omega)| = \frac{1}{\sqrt{2}a}$

Phase spectrum

$$\begin{aligned} F(j\omega) &= \frac{1}{a+j\omega} \times \frac{a-j\omega}{a-j\omega} = \frac{a-j\omega}{a^2 + \omega^2}, \\ &= \frac{a}{a^2 + \omega^2} - \frac{j}{a^2 + \omega^2}. \end{aligned}$$
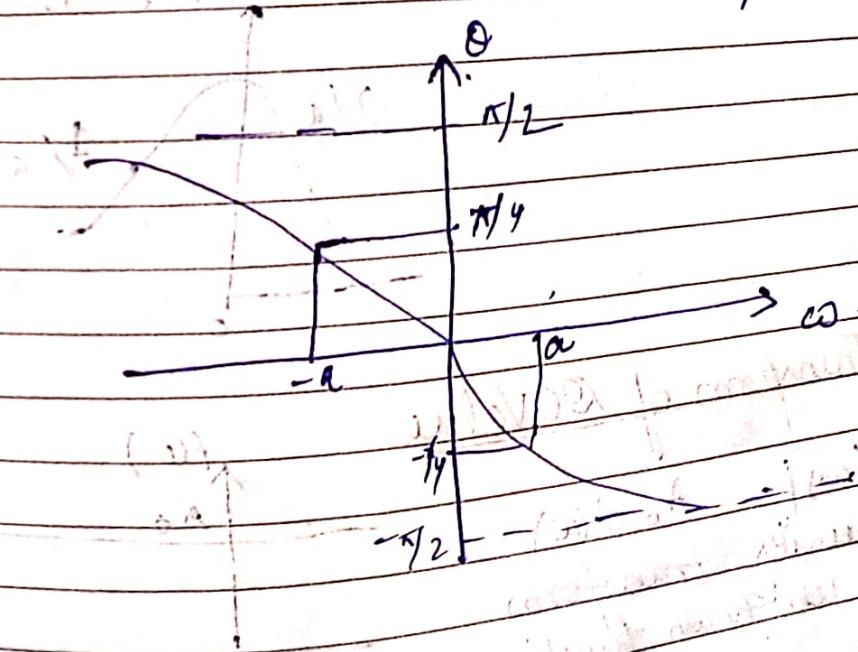
$$\theta = \tan^{-1} \frac{b}{a} = -\tan^{-1} \frac{\omega}{a} = -\tan^{-1} \frac{\omega}{a^2 + \omega^2}$$



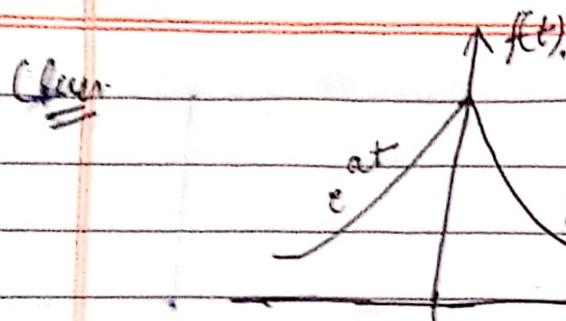


$$f(t) = e^{-|at|} \text{ for all } t \in \mathbb{R}$$

$$F(j\omega) = \int_{-\infty}^{\infty} e^{at} - e^{-at} e^{-j\omega t} dt + \int_0^{\infty} e^{-at} e^{-j\omega t} dt$$

$$= \frac{1}{a-j\omega} + \frac{1}{a+j\omega} = \frac{2a}{a^2+\omega^2}$$

$$\omega = 0, |F(j\omega)| \approx \frac{2}{a}$$

$$\omega = \infty, |F(j\omega)| \approx \frac{1}{a}, \frac{1}{|F(j\omega)|}$$

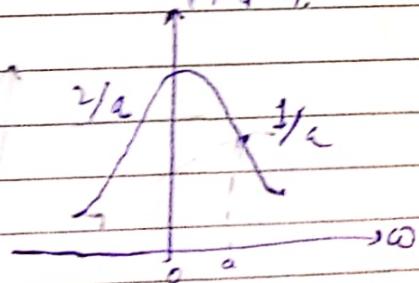


Fourier Transform of DC Value

Let $|F(j\omega)| = A_0 \delta(\omega)$

be the Fourier transform
of an unknown function
 $f(t)$.

$$F(j\omega) = A_0 \delta(\omega)$$
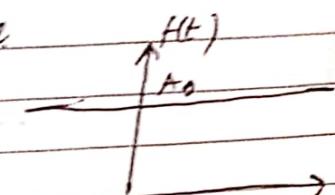
$$f(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega, \text{ i.e., it is not integrable.}$$



Here, the area under the curve = $A_0 \times \infty$, which is not defined

in integral.

$$z = \frac{1}{2\pi} \int_{-\infty}^{\infty} A_0 \delta(\omega) e^{j\omega t} d\omega$$

$$= A_0 \int_{-\infty}^{\infty} \delta(\omega) e^{j\omega t} d\omega$$

$$= \frac{A_0}{2\pi} \int_{-\infty}^{\infty} \delta(\omega - \omega_0) e^{j\omega t} d\omega$$

* Sampling property -

Multiplying a signal $x(t)$ by a unit impulse, samples the value of the signal at the point at which the impulse is located.

$$\int_{-\infty}^{\infty} \delta(t) dt = 1 \quad x(t)\delta(t) = x(t) \quad t \geq 0 \\ = x(0) \delta(t).$$

Using multiplication property of impulse.

$$f(t) \stackrel{?}{=} \frac{A_0}{2\pi} \cdot 1,$$

A_0 is the signal having fourier transform as $A_0 \delta(\omega)$

↓
by virtue of
this property,
 $e^{j\omega t} = 1$
in previous
formulae,

$$\frac{2\pi \times A_0}{2\pi} \stackrel{?}{=} 2\pi A_0 \delta(\omega)$$

$$A_0 \stackrel{?}{=} 2\pi A_0 \delta(\omega).$$

$$F.T \text{ of } A_0 = 2\pi A_0 \delta(\omega),$$


$$F.T \text{ of } 1 = 2\pi \delta(\omega)$$

$$\text{Defn } F(\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$F(\omega) = \int_{-\infty}^{\infty} \delta(t) e^{-j\omega t} dt$$

$F(\omega) = 1$
 According to Sampling property, multiplying a signal $f(t)$ by a unit impulse, samples the value of $f(t)$ at the point at which it is located.

Fourier transform of signum function -

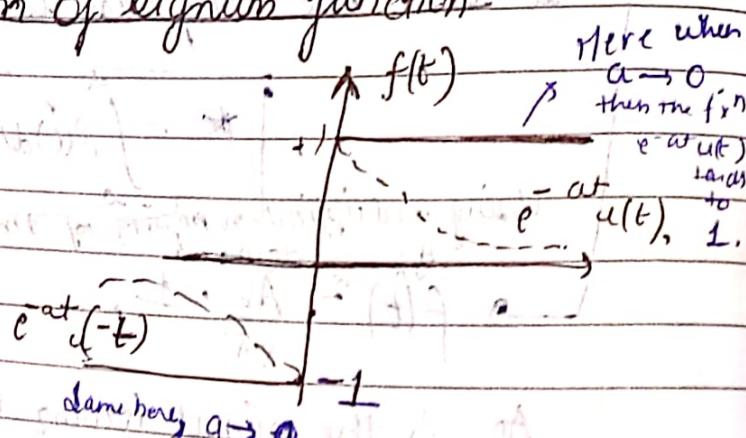

$$\lim_{a \rightarrow 0} [c^{-at} u(t) - e^{-at} u(-t)]$$

$$\lim_{a \rightarrow 0} \left[\frac{1}{a+j\omega} - \frac{1}{a-j\omega} \right]$$

$$\lim_{a \rightarrow 0} \left[\frac{-2j\omega}{a^2 + \omega^2} \right]$$


$$- \frac{2j\omega}{\omega^2} = \frac{2}{j\omega}$$

$$|F(j\omega)| = \sqrt{\frac{2}{\omega}}$$

$$\angle F(j\omega) = -\tan^{-1}\left(\frac{b}{a}\right) = -\frac{\pi}{2} \quad \omega > 0$$

$$\angle F(j\omega) = \frac{\pi}{2} \quad \omega < 0.$$

Fourier transform of Unit Step -

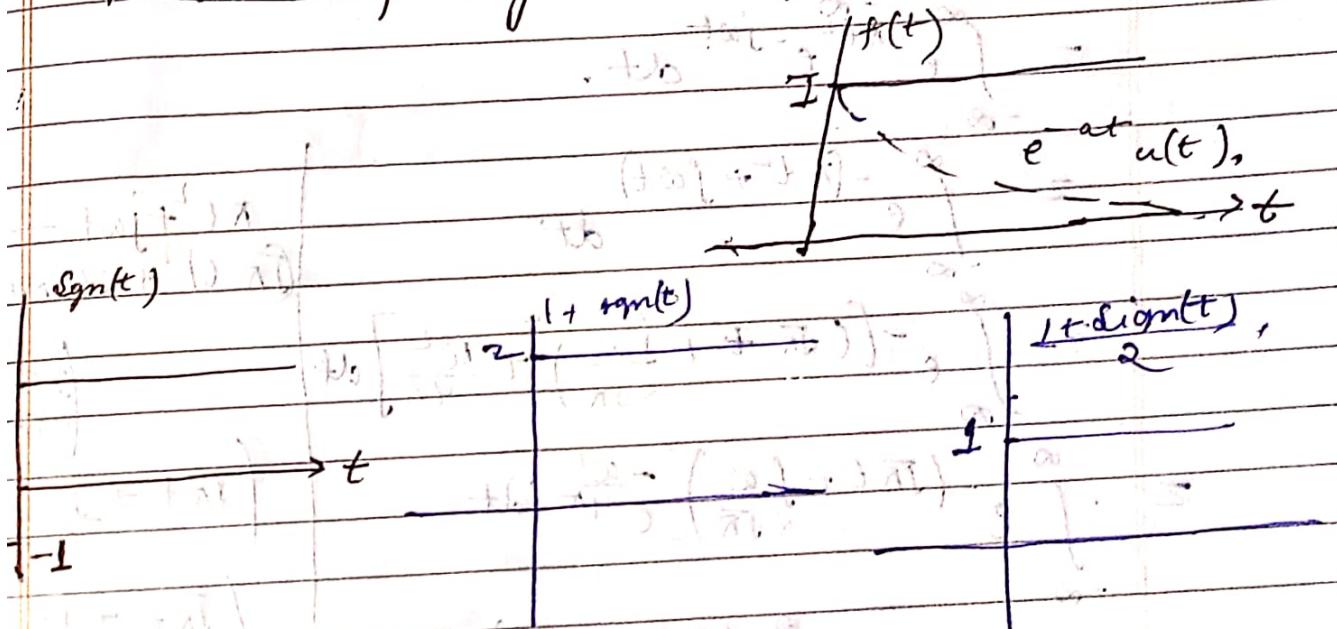

$$u(t) = \frac{1}{2} + \frac{1}{2} \text{sign}(t).$$

$$FT[u(t)] = FT\left[\frac{1}{2}\right] + \frac{1}{2} FT[\text{sign}(t)]$$

FT of $A_0 = 2\pi A_0$
 $\delta(\omega)$


$$A_0 = 1/2$$

$$FT[u(t)] = \frac{1}{2} \pi \delta(\omega) + \frac{1}{j\omega}$$

$$FT of \frac{1}{2} = \frac{1}{2} \pi \times \frac{1}{j\omega} \delta(\omega)$$

Fourier Transform Gaussian Pulse

PAGE NO:
DATE: / / 2016

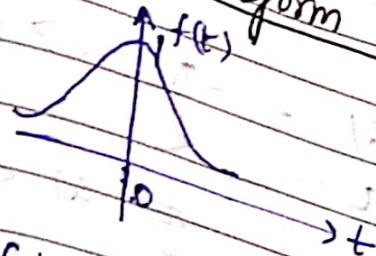

$$f(t) = e^{-\pi t^2}$$

$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_{-\infty}^{\infty} e^{-\pi t^2} e^{-j\omega t} dt$$

$$= \int_{-\infty}^{\infty} e^{-(\pi t^2 + j\omega t)} dt$$

$$= \int_{-\infty}^{\infty} e^{-\left[\left(\sqrt{\pi} + \frac{j\omega}{2\sqrt{\pi}}\right)^2 + \frac{\omega^2}{4\pi}\right]} dt$$

$$= \int_{-\infty}^{\infty} e^{-\left(\frac{(\sqrt{\pi} + j\omega)^2}{2\sqrt{\pi}} - \frac{\omega^2}{4\pi}\right)} dt$$

$$= e^{-\omega^2/4\pi} \int_{-\infty}^{\infty} e^{-\left(\frac{(\sqrt{\pi}t + j\omega)^2}{2\sqrt{\pi}}\right)} dt$$

$$\begin{aligned} \pi t^2 + j\omega t &\rightarrow (at+b)^2 \\ (\sqrt{\pi}t + j\omega)^2 + 2(\sqrt{\pi}t + j\omega)/2j\omega &\rightarrow \frac{2\sqrt{\pi}}{j\omega} \end{aligned}$$

$$\left(\frac{j\omega}{\sqrt{\pi}}\right)^2 - \frac{1}{4\pi}$$

$$\left(\frac{\sqrt{\pi}t + j\omega}{2\sqrt{\pi}}\right)^2 - \frac{j\omega^2}{4\pi}$$

$$\left(\frac{\sqrt{\pi}t + j\omega}{2\sqrt{\pi}}\right)^2 + \frac{\omega^2}{4\pi}$$

$$\text{Let } \sqrt{\pi}t + j\omega \geq u \quad \Rightarrow \quad u = \sqrt{\pi}t + j\omega$$

Also $u \rightarrow -\infty$ as $t \rightarrow -\infty$

$$\sqrt{\pi} dt = du \quad \Rightarrow \quad u \rightarrow \infty \text{ as } t \rightarrow \infty$$

$$dt = \frac{du}{\sqrt{\pi}}$$

$$\int_0^{\infty} e^{-u^2/\pi} du = \sqrt{\pi} \text{ as } u \rightarrow \infty$$

$$\therefore F(j\omega) = e^{-\omega^2/4\pi} \int_{-\infty}^{\infty} e^{-u^2/\pi} du$$

$$= \frac{e^{-\omega^2/4\pi}}{\sqrt{\pi}} 2 \int_0^{\infty} e^{-u^2/\pi} du$$


$$\text{evaluating, } \int_0^{\infty} e^{-u^2} du = \frac{\sqrt{\pi}}{2}$$

$$\therefore \frac{e^{-\omega^2/4\pi}}{\sqrt{\pi}} \times 2 \times \frac{\sqrt{\pi}}{2} = e^{-\omega^2/4\pi}$$

Sub $\omega = 2\pi f$

$$e^{-\frac{(2\pi f)^2}{4\pi}} = e^{-4\pi^2 f^2/4\pi} = e^{-\pi f^2}$$

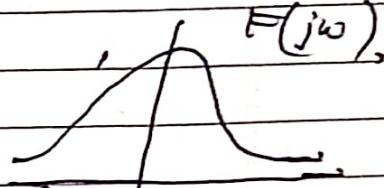Fourier transform of gaussian is gaussian.



$$f(t) = A \begin{cases} 0 & t < -T \\ \frac{t+T}{2T} & -T \leq t \leq 0 \\ 0 & t > 0 \end{cases}$$

07/11/22

$$F(j\omega) = \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt$$

$$= \int_0^T A \left(1 + \frac{t}{T}\right) e^{-j\omega t} dt + \int_{-T}^0 A \left(1 + \frac{t}{T}\right) e^{-j\omega t} dt$$

$$= \int_0^T A \left(1 + \frac{t}{T}\right) \cos \omega t dt + \int_0^T A \left(1 + \frac{t}{T}\right) \sin \omega t dt$$

$$= \int_0^T A \left(1 + \frac{t}{T}\right) e^{j\omega t} dt + \int_0^T A \left(1 + \frac{t}{T}\right) e^{-j\omega t} dt$$

$$= 2A \int_0^T \left(1 + \frac{t}{T}\right) \frac{e^{j\omega t} + e^{-j\omega t}}{2} dt$$

$$= 2A \int_0^T \left(1 + \frac{t}{T}\right) \cos \omega t dt$$

$$= 2A \left[\left(1 - \frac{t}{T} \right) \frac{\sin \omega t}{\omega} \right]^T - 2A \left(\frac{1}{T} \right) \int_0^T \sin \omega t dt$$

$$= 0 + \int_0^T -\frac{2A}{T} \cos \omega t \frac{1}{\omega^2} dt$$

$$= -\frac{2A}{\omega^2 T} [\cos \omega T - 1]$$

$$= -\frac{2A}{\omega^2 T} [\cos \omega T - 1]$$

$$= \frac{2A}{\omega^2 T} [1 - \cos \omega T]$$



$$= \frac{2A}{\omega^2 T} 2 \sin^2 \left(\frac{\omega T}{2} \right) = \frac{4A}{\omega^2 T} \sin^2 \left(\frac{\omega T}{2} \right) = \frac{4AT}{\omega^2 T^2} \sin^2 \left(\frac{\omega T}{2} \right)$$

$$= \frac{AT}{(\omega T)^2} \sin^2 \left(\frac{\omega T}{2} \right)$$

$$= AT \left[\sin \left(\frac{\omega T}{2} \right) \right]^2 = AT \sin^2 \left(\frac{\omega T}{2} \right)$$

Sinc function =


$$\text{sinc}(t) = \frac{\sin t}{t}$$

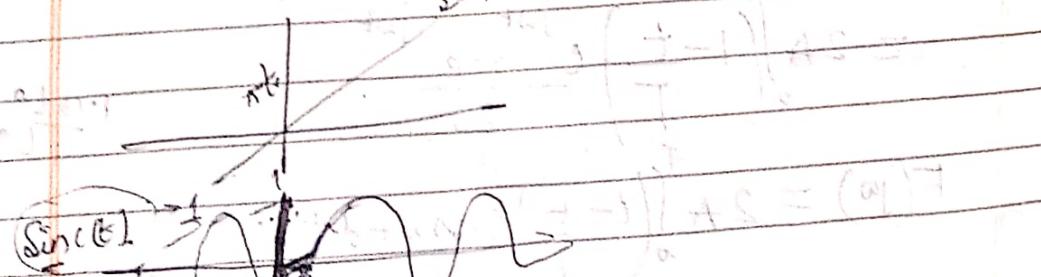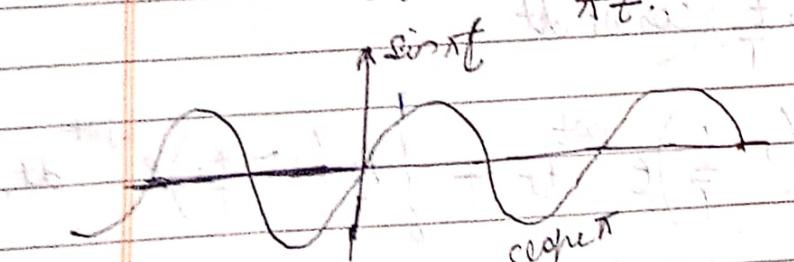

$$Q = I^2 R = 1.25$$

T. T. of Recitation
Due _____
PAGE No. _____
DATE _____

$$Q = I^2 R = 0.8$$

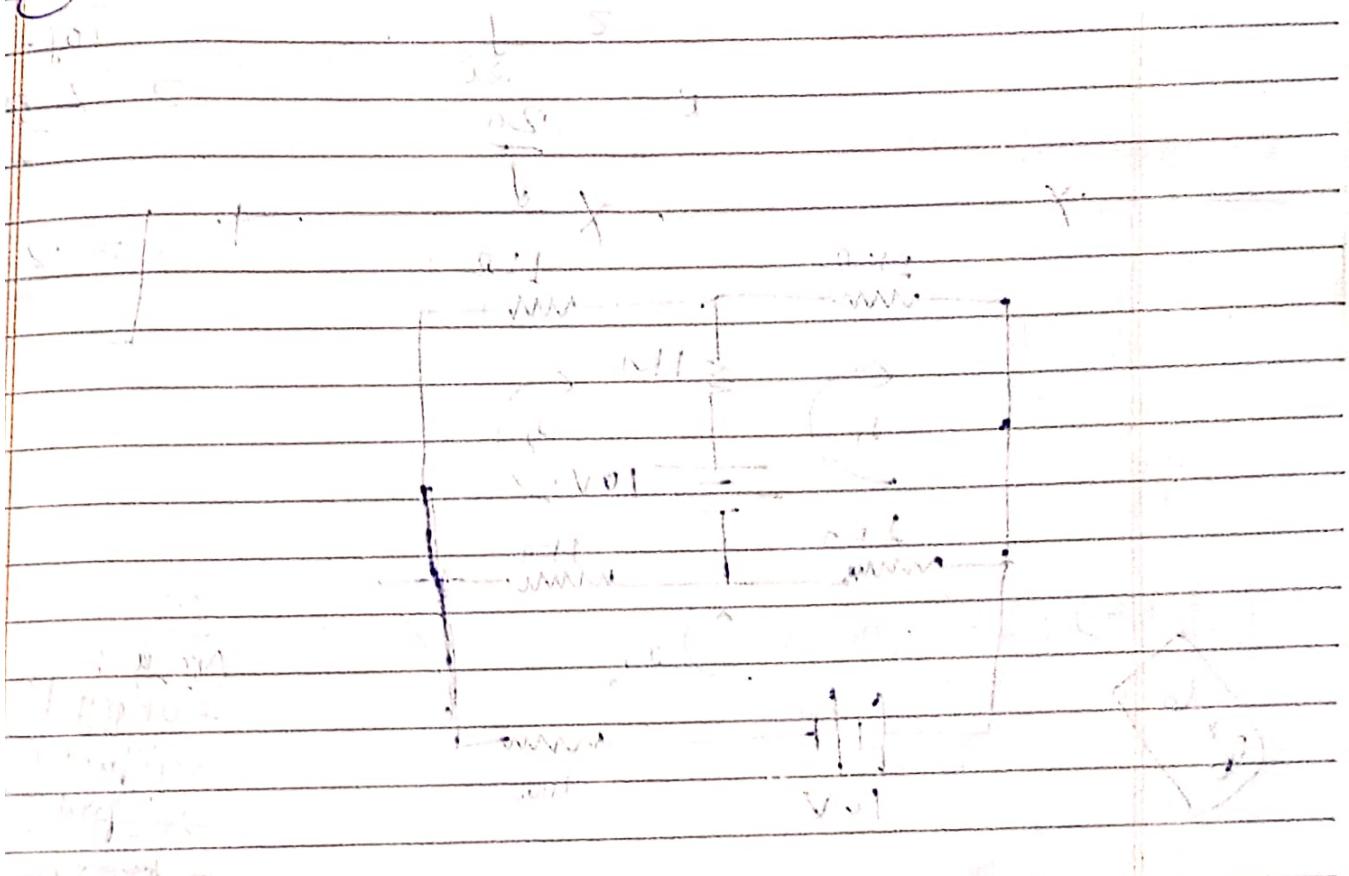

$$(xL - xE) - xL - (xL + x) = 0$$

$$xL - xL + xE - xL - xL - x = 0$$

$$xL - xL + xE + x = 0$$

$$(xL - xL) + xL - (xL - xL) = 0$$

$$xL - xL + xL - xL + xL - xL = 0$$

$$xL - xL + xL - xL + xL - xL = 0$$

ANSWER

Inverse fourier transform -

$$f(t) = \frac{1}{\sqrt{\pi}} \int_{-\infty}^{\infty} F(j\omega) e^{j\omega t} d\omega.$$

$$F(j\omega) = \delta(\omega)$$

$$f(t) = \frac{1}{\sqrt{\pi}} \int_{-\infty}^{\infty} \delta(\omega) e^{j\omega t} d\omega$$

Using Sampling property of Impulse function

$$x(t)\delta(t) = x(t) \Big|_{t=0} \quad \delta(t) = i(0)\delta(t).$$

Outer form

$$x(t)\delta(t-t_0) = x(t_0)\delta(t-t_0)$$

$$= \frac{1}{\sqrt{\pi}} e^{j\omega t} \Big|_{\omega=0}$$

$$F[\delta(\omega)] = \frac{1}{\sqrt{\pi}} \quad \text{or} \quad \delta(\omega) = F\left[\frac{1}{\sqrt{\pi}}\right]$$

$$\frac{1}{\sqrt{\pi}} \longleftrightarrow \delta(\omega),$$

now,

$$F(j\omega) = \delta(\omega - \omega_0)$$

$$F^{-1}[\delta(\omega - \omega_0)] = \frac{1}{\sqrt{\pi}} e^{j\omega_0 t}$$

$$\delta(\omega - \omega_0) = F\left[\frac{1}{\sqrt{\pi}} e^{j\omega_0 t}\right]$$

$$\left[\frac{1}{\sqrt{\pi}} e^{j\omega_0 t} \longleftrightarrow \delta(\omega - \omega_0) \right] \rightarrow \text{fourier transform pair}$$

Fourier Transform of $f(t) = \cos \omega_0 t$.

$$f(t) = \cos \omega_0 t = \frac{1}{2} (e^{j\omega_0 t} + e^{-j\omega_0 t})$$

$$F(j\omega) = F \left[\frac{1}{2} (e^{j\omega_0 t} + e^{-j\omega_0 t}) \right]$$

Since,

$$F[e^{j\omega_0 t}] = 2\pi \delta(\omega - \omega_0)$$

$$F[e^{-j\omega_0 t}] = 2\pi \delta(\omega + \omega_0)$$

$$F(j\omega) = \frac{1}{2} \times 2\pi \delta(\omega - \omega_0) + \frac{1}{2} \times 2\pi \delta(\omega + \omega_0)$$

$$\boxed{F(j\omega) = \pi [\delta(\omega - \omega_0) + \delta(\omega + \omega_0)]}$$

Fourier transform of $f(t) = \sin \omega_0 t$.

$$\begin{aligned} f(t) &= \sin \omega_0 t \\ &= \frac{1}{2j} (e^{j\omega_0 t} - e^{-j\omega_0 t}) \end{aligned}$$

$$\boxed{F(j\omega) = \pi j \delta(\omega - \omega_0)}$$

Ques. I.F.T.

$$F(j\omega) = \frac{j\omega + 3}{(j\omega + 1)^2} = \frac{j\omega + 2 + 1}{(j\omega + 1)^2}$$

$$= \frac{(j\omega + 1)}{(j\omega + 1)^2} + \frac{2}{(j\omega + 1)^2}$$

$$F(j\omega) = \frac{1}{(j\omega + 1)} + \frac{2}{(j\omega + 1)^2}$$

$$F(j\omega) = \frac{1}{j\omega + 1}$$

$$F(j\omega) = e^{-t} u(t) + 2t e^{-t} u(t)$$

I.F.T. of

$$t^n e^{-at} u(t) = \frac{1}{(a+j\omega)^{n+1}}$$

$$t^n e^{-at} u(t) = \frac{1}{(a+j\omega)^{n+1}}$$

$$t e^{-at} u(t) = \frac{1}{(a+j\omega)^2}$$

10/11/22.

Ques. I.F.T. -

$$F(j\omega) = \frac{1}{\omega^2 + 2j\omega + 9}$$

$$F(j\omega) = \frac{\omega^2 + 9}{1 + j2\omega}$$

$$\omega^2 + 9 = \frac{\omega^2 + 9}{\omega^2 + 4\omega + 13}$$

$$\omega^2 + 2j\omega = (\omega^2 + 9)(1 + j2)$$

*. F.T of $\delta(t) \rightarrow 1$.

$$\text{F.T of } e^{-at} = \frac{1}{a + j\omega}$$

$$\omega^2 + 2j\omega = \omega^2 + 9 + j12$$

$$\omega^2 + 2j\omega = \omega^2 + 9 + 12$$

$$= \frac{2(a)}{\omega^2 + (3)^2}$$

$$= \frac{2(3)}{\omega^2 + (3)^2}$$

F.T

$$= 1 + 2 \cdot \frac{2(3)}{\omega^2 + (3)^2}$$

$$f(t) = \mathcal{O}(t+1) e^{-\alpha t}.$$

$$\underline{\underline{f(j\omega)}} = \frac{j\omega+1}{(j\omega)^2 + 5j\omega + 6}$$

$$= \frac{(j\omega+1)}{(j\omega+2)(j\omega+3)}$$

$$F(j\omega) = \frac{k_1}{j\omega+2} + \frac{k_2}{j\omega+3}$$

$$j\omega^2 + 5j\omega + 6 = 0$$

~~jω² + 5jω + 6 = 0~~

$$j^2\omega^2 + 5j\omega + 6 = 0$$

$$j\omega^2 + 3j\omega + 2j\omega + 6 = 0$$

$$j\omega(j\omega+2)3(j\omega+2) = 0$$

$$(j\omega+2)^2 = 0$$

$$(j\omega+3)(j\omega+2) = 0$$

$$F(j\omega) = \frac{k_1}{j\omega+2}$$

$$j\omega^2 + 5j\omega + 6 = 0$$

$$k_1 = \frac{j\omega+1}{j\omega+2} \Big|_{j\omega=-2} = -1$$

~~jω² + 5jω + 6 = 0~~

$$k_2 = \frac{j\omega+1}{j\omega+2} \Big|_{j\omega=-3} = 2$$

$$F(j\omega) = \frac{-1}{(j\omega+2)} + \frac{2}{(j\omega+3)}$$

$$= -\frac{(j\omega+3)}{(j\omega+2)(j\omega+3)} + \frac{2}{(j\omega+3)}$$

$$= \frac{-j\omega-3 + 2j\omega+4}{(j\omega+2)(j\omega+3)}$$

$$= \frac{1+j\omega}{(j\omega+2)(j\omega+3)}$$

$$F(j\omega) = -e^{-2t}u(t) + 2e^{t+1}u(t)$$

$$\text{Ans. } F(j\omega) = -j\omega \frac{(j\omega)^2 + 3j\omega + 2}{(j\omega + 2)(j\omega + 1)}$$

$$F(j\omega) = -j\omega = \frac{j^2\omega^2 + 2j\omega + j\omega + 2}{(j\omega + 2)(j\omega + 1)} = \frac{(j\omega + 1)(j\omega + 2) + 2}{(j\omega + 2)(j\omega + 1)}$$

$$q_p(j\omega) = \frac{A}{(j\omega + 2)} + \frac{B}{(j\omega + 1)} = \frac{(j\omega + 1)(j\omega + 2) + 2}{(j\omega + 2)(j\omega + 1)}$$

$$\Rightarrow A(j\omega + 1) + B(j\omega + 2)$$

$$-j\omega = A_{j\omega} + B_{j\omega} + C_{j\omega} + D_{j\omega}$$

$$A + B = -1 \quad , \quad A = -2$$

$$C + D = 0 \quad , \quad C = 1$$

$$= \frac{-2}{(j\omega + 2)} + \frac{1}{(j\omega + 1)}$$

$$= -2e^{-2t}u(t) + e^{-t}u(t),$$

Steady state response of network to periodic signal -

In practice, many circuits are driven by non-sinusoidal periodic function. To obtain the steady state response of the circuit to a non-sinusoidal periodic function requires the application of Fourier analysis, the phasor analysis & superposition principle. The procedure involves following steps -


1. Express the excitation as fourier series.
2. Transform the circuit elements from time domain to frequency domain

$R \rightarrow R$, $L \rightarrow j\omega L$, $C \rightarrow \frac{1}{j\omega C}$ for n^{th} harmonic

3. Find the response of dc & ac component in fourier series.

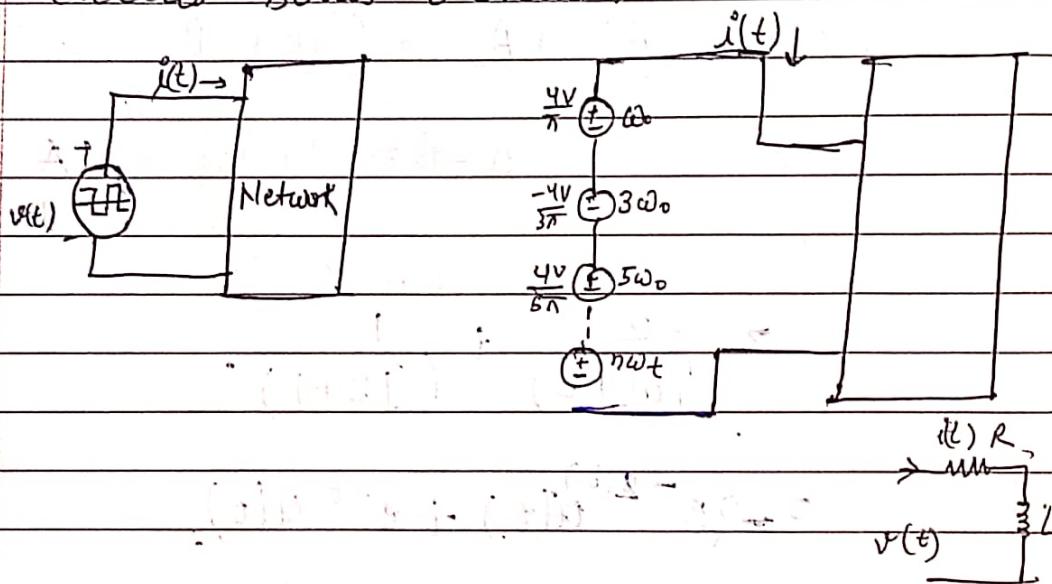4. Add the individual dc & ac response using the superposition principle.

Ques: Steady state response when a square wave source excites series RL circuit.



The fourier series is

$$v(t) = \frac{4V}{\pi} (\text{constant} - \frac{1}{3} \cos 3\omega_0 t + \frac{1}{5} \cos 5\omega_0 t + \dots)$$

If $\omega_0 = \pi$ & for simplicity ω_0 is ω . $\omega_0 = 1 \text{ rad/sec}$.

$$|A| \cos(\omega t + \phi) \leftrightarrow |A| e^{j\phi}$$

$$Ae^{j\phi}$$

$$V(t) = \cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t + \dots$$

The phasors corresponding to first three terms are.

$$V_1 = 1 e^{j0^\circ}, V_3 = \frac{1}{3} e^{-j100^\circ}, V_5 = \frac{1}{5} e^{j0^\circ}$$

$$\text{Let } R = 1 \Omega + Z = 1 H$$

$$\therefore Z(j\omega n) = R + j\omega nL \Rightarrow Y(j\omega n) = \frac{1}{R + j\omega nL}$$

$$Y(jn) = \frac{1}{R + jnL} = \frac{1}{1 + jn} = \frac{1}{1 + jn}$$

$$n=1; Y(j_1) = \frac{1}{1 + j_1} = \frac{1}{1 + j} \times \frac{1-j}{1-j} = \frac{1-j}{1-j^2} = \frac{1-j}{2}$$

$$= 0.5 - j0.5 \\ = 0.7071 - j0.7071$$

~~$$n=3; Y(j3) = \frac{1}{1+3j}$$~~

$$n=3; Y(j3) = \frac{1}{1+3j} = \frac{1}{1+3j} \times \frac{1-3j}{1-3j} = \frac{1-3j}{1-3j^2} = \frac{1-3j}{10} \\ = 0.1 - 0.3j \\ = 0.3162 \angle -71.56^\circ$$

$$n=5; Y(j5) = \frac{1}{1+j5} = \frac{1}{1+j5} \times \frac{1-j5}{1-j5}$$

$$= \frac{1-j5}{1-(j5)^2} = \frac{1-j5}{1-25} = \frac{1-j5}{26} = 0.038 - j0.195 \\ = 0.195 \angle -78.8^\circ$$

$$\text{Since } I = YV = I_1 + I_3 + I_5 + \dots$$

$$\& I_1 = Y_1 V_1 = 0.7071(-j0.7071) \times 1 e^{j0^\circ} = 0.707 e^{-j45^\circ}$$

$$= 0.707 e^{-j45^\circ}$$

$$I_3 = Y_3 V_3 = 0.3162 e^{-j71.56^\circ} \times 1 e^{-j180^\circ} = 0.3162 e^{-j251.56^\circ}$$

$$I_5 = Y_5 V_5 = 0.195 e^{-j78.8^\circ} \times \frac{1}{5} e^{j0^\circ} = 0.039 e^{-j78.8^\circ}$$

Then the total current has following first three terms.

$$i(t) = 0.707 \cos(t - 45^\circ) + 0.105 \cos(3t - 251.6^\circ) + 0.039 \cos(5t - 78.8^\circ) + \dots$$

EFFECTIVE VALUE / RMS VALUE

Let the periodic, non-sinusoidal waveform be represented by

$$f(t) = a_0 + a_1 \cos \omega t + a_2 \cos 2\omega t + \dots + b_1 \sin \omega t + b_2 \sin 2\omega t + \dots$$

$$\text{or } f(t) = a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t)$$

$$F_{\text{rms}} = \left\{ \int_0^{T/2} \left[a_0 + \sum_{n=1}^{\infty} (a_n \cos n\omega t + b_n \sin n\omega t) \right]^2 dt \right\}^{1/2}$$

$$= \sqrt{a_0^2 + \frac{1}{2} \left[(a_1^2 + a_2^2 + \dots) \right]}$$

Unit - IV

Laplace Transform

$$F(s) = \int_0^\infty f(t) e^{-\sigma t} e^{-j\omega t} dt.$$

Let $s = \sigma + j\omega$.

$$\boxed{L[f(t)] = F(s) = \int_0^\infty f(t) e^{-st} dt}$$

$$\boxed{L^{-1}[F(s)] = f(t) = \frac{1}{2\pi} \int_{\sigma-j\omega}^{\sigma+j\omega} F(s) e^{st} ds}$$

Basic Theorem

- The Laplace transform of sum of two functions equal to the sum of Laplace transform of the individual functions.

$$\begin{aligned} L[f_1(t) + f_2(t)] &= \int_0^\infty [f_1(t) + f_2(t)] e^{-st} dt \\ &= \int_0^\infty f_1(t) e^{-st} dt + \int_0^\infty f_2(t) e^{-st} dt \\ &\stackrel{def}{=} F_1(s) + F_2(s) \end{aligned}$$

- The Laplace transform of a constt. times a function is equal to the constt. times the Laplace transform

of the function.

$$\mathcal{L}[Kf(t)] = \int_0^{\infty} Kf(t)e^{-st} dt = K F(s).$$

3. Differentiation Theorem -

If a fxⁿ f(t) & its derivative are both Laplace transformable then the Laplace transform of the first derivative of a time fxⁿ f(t) is 's' times the Laplace transform of f(t) minus the limit of f(t) as $t \rightarrow 0^+$

$$\mathcal{L}\left[\frac{d f(t)}{dt}\right] = sF(s) - f(0^+)$$

$$\begin{aligned} \mathcal{L}\left[\frac{d^2 f(t)}{dt^2}\right] &= \mathcal{L}\left[\frac{d}{dt}\left[\frac{d f(t)}{dt}\right]\right] = s\mathcal{L}\left[\frac{d f(t)}{dt}\right] - \frac{d f(t)}{dt} \Big|_{t=0^+} \\ &= s[sF(s) - f(0^+)] - f'(0^+) = s^2 F(s) - sf(0^+) - f'(0^+) \end{aligned}$$

4. Differentiation by s -

Differentiation by s in complex frequency domain corresponds to multiplication by t in time domain. i.e.

$$\mathcal{L}[tf(t)] = -\frac{dF(s)}{ds}.$$

5. Integration Theorem -

The Laplace transform of the first integral of a function $f(t)$ w.r.t time t is the Laplace transform of $f(t)$ divided by s .

i.e.

$$\mathcal{L} \left[\int_0^t f(t) dt \right] = \frac{F(s)}{s}$$

6. Integration by s -

$$\mathcal{L} \left[\int_0^t \frac{f(t)}{t} dt \right] = \int_0^\infty F(s) ds$$

7. Initial Value Theorem -

If the Laplace transform of $f(t)$ is $F(s)$ & the first derivative of $f(t)$ is Laplace transformable then the initial value of $f(t)$ is

$$f(0^+) = \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} s F(s)$$

if time limit exists.

8. Final Value Theorem -

If the Laplace transform of $f(t)$ is $F(s)$ & if the ~~real part~~ s times $F(s)$ is analytic on the imaginary axis & is right half of s -plane then, limit

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s).$$

Ques. Find Laplace transform of

(1) $f(t) = e^{at}$

$$\therefore F(s) = \int_0^\infty f(t) e^{-st} dt$$

$$= \int_0^\infty e^{at} e^{-st} dt,$$

~~$$= e^{at} \text{ is } = \int_0^\infty e^{at - st} dt$$~~

$$= \int_0^\infty e^{-(s-a)t} dt,$$

$$= \frac{1}{s-a},$$

Ques. (2). $f(t) = u(t) = \begin{cases} 1 & \text{for } t > 0, \\ 0 & \text{for } t < 0. \end{cases}$

$$f(s) = \int_0^\infty 1 e^{-st} dt,$$

$$= \left[\frac{e^{-st}}{-s} \right]_0^\infty dt$$

$$= \left(\frac{e^{-\infty}}{-s} - \frac{e^0}{-s} \right).$$

$$= \frac{1}{s}.$$

(3) Step function

$$f(t) = k u(t)$$

$$f(s) = \int_0^\infty k u(t) e^{-st} dt. = \frac{k}{s},$$

Table

$$(v) f(t) = \sin \omega t$$

$$f(t) = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

$$\int_0^\infty f(t) e^{-st} dt$$

$$f(s) = \frac{1}{s-a}$$

$$f(s) = \int_0^\infty f(t) e^{-st} dt$$

$$= \int_0^\infty \frac{e^{j\omega t} - e^{-j\omega t}}{2j} e^{-st} dt$$

$$= \int_0^\infty \left(\frac{e^{j\omega t}}{2j} - \frac{e^{-j\omega t}}{2j} \right) e^{-st} dt$$

$$= \int_0^\infty K u(t) e^{-st} dt$$

$$= \int_0^\infty \sin \omega t e^{-st} dt$$

$$= \frac{s}{s^2 + \omega^2}$$

$$= \int_0^\infty \frac{e^{j\omega t} - e^{-j\omega t}}{2j} e^{-st} dt$$

$$= \int_0^\infty \frac{e^{j\omega t - st} - e^{-j\omega t - st}}{2j} dt$$

$$= \frac{1}{2j} \int_0^\infty e^{j\omega t - st} - e^{-j\omega t - st}$$

$$= \frac{1}{2j} \left[e^{j\omega t - st} - e^{-j\omega t - st} \right]_0^\infty$$

$$= \frac{1}{2j} \left[e^{j\omega t} \right]_0^\infty$$

$$= \frac{1}{2j} \left[\left[e^{j\omega t} \right]_0^\infty - \left[e^{-j\omega t} \right]_0^\infty \right]$$

$$= \frac{1}{2j} \left[\left[\frac{e^{(j\omega - s)t}}{j\omega - s} \right]_0^\infty - \left[\frac{e^{-(j\omega + s)t}}{j\omega + s} \right]_0^\infty \right]$$

$$= \frac{1}{2j} \left[\frac{1}{j\omega - s} \right] - \left[\frac{-1}{j\omega + s} \right]$$

$$= \frac{1}{2j} \left[\frac{1}{j\omega - s} + \frac{1}{j\omega + s} \right]$$

$$= \frac{1}{2j} \left[\frac{(j\omega + s) + (j\omega - s)}{(j\omega - s)(j\omega + s)} \right]$$

$$= \frac{1}{2j} \left[\frac{2j\omega}{(j\omega)^2 - s^2} \right] =$$

$$= \frac{\omega}{s^2 - \omega^2}$$

(Max effect)

Table

$$f(t) \quad f(s)$$

$$e^{at} \quad 1/s-a$$

$$u(t) \quad 1/s$$

$$K u(t) \quad K/s$$

$$\sin \omega t \quad \omega / s^2 + \omega^2$$

$$\cos \omega t \quad s / s^2 + \omega^2$$

$$\sinh at \quad \frac{a}{s^2 - a^2}$$

$$L[u(t)] \quad \frac{1}{s}$$

$$\cosh at \quad \frac{s}{s^2 - a^2}$$

$$L[t^n] \quad \frac{n!}{s^{n+1}}$$

$$L[e^{-st}, t^2] \quad \frac{2}{(s+1)^3}$$

$$L[e^{-st}, t^q] \quad \frac{q!}{(s+a)^{q+1}}$$

$$L[\delta(t)] = 1 \quad (s+a)^{q+1}$$

Ans. $f(t) = \cos wt$

Ques. Find Laplace transform of Hyperbolic sine,
 $f(t) = \sinh at \equiv \frac{1}{2} (e^{at} - e^{-at})$

$$f(s) = \int f(t) e^{-st} dt$$

$$= \int_0^\infty \frac{1}{2} (e^{at} - e^{-at}) e^{-st} dt$$

$$= \frac{1}{2} \int_0^\infty (e^{at} - e^{-at}) e^{-st} dt$$

$$= \frac{1}{2} \int_0^\infty (e^{at} \cdot e^{-st} - e^{-at} \cdot e^{-st}) dt$$

$$= \frac{1}{2} \int_0^\infty (e^{at-st} - e^{-at-st}) dt$$

$$= \frac{1}{2} \int_0^\infty (e^{(a-s)t} - e^{-(a-s)t}) dt$$

$$= \frac{1}{2} \left[\frac{e^{(a-s)t}}{a-s} \right]_0^\infty - \left[\frac{e^{-(a-s)t}}{-a-s} \right]_0^\infty$$

$$= \frac{1}{2} \left[\frac{e^{(a-s)\infty}}{a-s} - \frac{e^{-(a-s)0}}{-a-s} \right]$$

Cours: Hyperbolic Conv.

$$f(t) \approx f_0 / (e^{at} + e^{-at})$$

Topics:

Formula of L.T.

advantages.

Basic Theorems - differentiation

- Integration
- Initial value
- Final Value

- Standard function

Property: e^{-as} times the function

$$\mathcal{L}\{t^n\}$$

Numericals

Singularity function: - Unit Ramp, Parabolic $f(x)$,
Unit Step, Unit Impulse

Shifting & Scaling

Shifting theorem $\mathcal{L}[f(t-a) U(t-a)] = e^{-as} F(s)$

Waveform synthesis

L.T. of waveform

L.T. of gate $f(x)$, sawtooth wave, $\delta(t)$, $f(x)$ etc,

L.T. of periodic $f(x)$:-

Transform ckt, application of L.T. to electrical ckt.

Ques: Damped sine $f(t) = e^{-at} \sin \omega t$,

$$\begin{aligned}&= L \left[\frac{1}{2j} \left[e^{-at} (e^{j\omega t} - e^{-j\omega t}) \right] \right] \\&= \frac{1}{2j} \left[e^{-(a-j\omega)t} - e^{-(a+j\omega)t} \right] \\&= \frac{1}{2j} \left[\frac{1}{s+a-j\omega} - \frac{1}{s+a+j\omega} \right] \\&\approx \frac{\omega}{(s+a)^2 + \omega^2}\end{aligned}$$

Property -

e^{-at} times a function

$$L[e^{-at} f(t)] = \int_0^\infty e^{-at} f(t) e^{-st} dt,$$

$$= \int_0^\infty f(t) e^{-(s+a)t} dt$$

$$\boxed{L[e^{-at} f(t)] = F(s+a)}$$

$$\text{e.g. } L[e^{-at} \sin \omega t] = \frac{\omega}{(s+a)^2 + \omega^2}$$

$$\cos^2 t = \frac{1 + \cos 2t}{2}$$

Ans: $f(t) = \cos^2 t.$

$$\therefore f(t) = \frac{1 + \cos 2t}{2}$$

$$f(s) = \int_0^\infty f(t) e^{-st} dt$$

$$f(s) = \int_0^\infty \frac{1 + \cos 2t}{2} e^{-st} dt.$$

$$f(s) = \int \frac{1}{2} [1] + \int \frac{1}{2} [\cos 2t] dt$$

$$= \frac{1}{2} s^{-1} + \frac{1}{2} \left[\frac{\sin 2t}{2} \right] \Big|_0^\infty$$

$$= \frac{1}{2} s^{-1} + \frac{1}{4} [\cos 2t].$$

$$= \frac{1}{2s} + \frac{1}{4s} \sin 2s$$

$$\text{If } f(t) = t^n$$

$$\mathcal{L}[t^n] = \int t^n e^{-st} dt$$

$$= t^n \left[\frac{e^{-st}}{-s} \right]_0^\infty - \int_0^\infty n t^{n-1} \frac{e^{-st}}{-s} dt.$$

$$= -\frac{1}{s} \left[t^n e^{-st} \right]_0^\infty + \frac{n}{s} \int_0^\infty t^{n-1} e^{-st} dt.$$

$$= -\frac{1}{s} \left[s^n e^{-s \cdot 0} - 0 \right]$$

$$= -\frac{1}{s} [\infty - 0 - 0]$$

Ques. $F(s) = \frac{100(s+3)}{(s+6)(s^2+6s+25)}$

$$= \cancel{\frac{A}{s+6}} + \frac{b}{(s-3+4i)} + \frac{c}{s-3-4i} \cdot \boxed{s^2+6s+25}$$

$$\Rightarrow A = (s+6)(s-3+4i) \cdot \begin{matrix} s+6 = -6+4i \\ s = -6 \end{matrix}$$

$$= \frac{A}{s+6} + \frac{B}{-3+4i} + \frac{C}{-3-4i}$$

$$A = (-3+4i)(-3-4i)$$

$$2 = -2 + 2i$$

$$2 + 2 - 2i =$$

$$\text{Clue: } F(s) = \frac{1}{s^2 + 4s + 8}$$

$$s^2 + 4s + 8$$

$$= -2 + 2i$$

$$s^2 + 4s + 8$$

$$x_1 = -2 + 2i$$

$$x_2 = -2 - 2i$$

$$z = A + Bi$$

$$s - 2 + 2i = s - 2 - 2i$$

$$\frac{1}{(s+2+2i)(s+2-2i)}$$

$$A = 1$$

$$[-2+2i+2+2i]$$

$$A = -0.25i$$

$$B = 1$$

$$-2-2i-2+2i$$

$$B = -0.25$$

$$\Rightarrow f(s) = \frac{-0.25i}{(s-2+2i)} + \frac{(-0.25)}{s-2-2i}$$

$$\frac{-i}{s-2+2i} + \frac{-1}{s-2-2i}$$

$$(s-2+2i) (s-2-2i)$$

$$j/4 \left(e^{-2+2i} - e^{-2-2i} \right)$$

$$2 - j/4 \left($$

$$(Ques) \quad F(s) = \frac{2s^2 + 5s + 2}{(s+1)^3}$$

$$P(s) = \frac{A_0}{(s+1)^3} + \frac{A_1}{(s+1)^2} + \frac{A_2}{(s+1)}$$

$$\frac{1}{s!} \frac{d^L}{ds^L}$$

$$\frac{1}{J!} \frac{d^J}{ds^J}$$

$$A_0 = (s+1)^3 \cdot F(s) \Big|_{s=1} = \frac{(2s^2 + 5s + 2)}{(s+1)^3} \Big|_{s=1} = -1$$

$$A_1 = (s+1)^2 \cdot F(s) \Big|_{s=1} = \frac{d}{ds} (2s^2 + 5s + 2) \Big|_{s=1} = 1$$

$$A_2 = (s+1) \cdot F(s) \Big|_{s=1}$$

$$A_2 = \frac{1}{2!} \frac{d^2}{ds^2} (s+1)^3 \cdot F(s) \Big|_{s=1} = 2$$

$$\# \quad \mathcal{L}[e^{-at} f(t)] = F(s+a)$$

$$t = \frac{1}{s}$$

$$\mathcal{L}[e^{-t} \cdot t] = \frac{1}{(s+1)^2}$$

$$(Ques) \quad F(s) = \frac{2s^3 - 9s^2 + 4s + 10}{s^2 - 3s - 4}$$

~~$$\begin{array}{r}
 s^3 - 3s - 4 \\
 \times 2s^3 \\
 \hline
 2s^3 - 9s^2 + 4s + 10 \\
 \hline
 -6s - 8 \\
 + + \\
 -9s^2 + 10s + 18
 \end{array}$$~~

~~$$(s^3 - 3s - 4)(2) + (-9s^2 + 10s + 18) = (2s^3 - 9s^2 + 4s + 10)$$~~

2-5. 2

2-3

$$(s^2 - 3s - 4)$$

$$\begin{array}{r} 2s^3 - 9s^2 + 4s + 10 \\ \underline{- 2s^3 + 6s^2 - 8s} \\ -3s^2 + 12s + 10 \end{array}$$

PAGE No. / DATE: / 201

$$3s - 2$$

$$= (s^2 - 3s - 4)(2s - 3) + (3s - 2)$$

$$F(s) = 2[s] - 3 \cdot 1 + \frac{1}{s+1} + \frac{2}{s-4}$$

$$f(t) = 2 \cdot \frac{d}{dt} \delta'(t) - 3 \cdot \delta(t) - e^{-t} + 2e^{4t}$$

Ques $F(s) = \frac{s^2 + s - 3}{s^2 + 3s + 2}$ *(first long division & then partial fraction constt.)..*

$$\text{Ans} = \delta'(t) - 3e^{-t} + e^{-2t},$$

Singularity Function

1. Unit Step

$$u(t) = \begin{cases} 1, & t \geq 0 \\ 0, & t < 0 \end{cases}$$

2. Unit impulse (Dirac Delta δ^n)

$$\delta(t) = \begin{cases} 0, & t \neq 0 \\ \infty, & t = 0 \end{cases}$$

3. Unit ramp

$$r(t) = t u(t) = t \begin{cases} 1, & t \geq 0 \\ 0, & t < 0 \end{cases}$$



Laplace Transform -

$$\mathcal{L}[u(t)] = \int 1 \cdot e^{-st} dt = \frac{1}{s}$$

$$\mathcal{L}[\delta(t)] = \int \delta(t) e^{-st} dt = e^{-st} \Big|_{t=0} = e^{s \cdot 0} = 1$$

$$\mathcal{L}[t u(t)] = \int_0^\infty t e^{-st} dt = \frac{1}{s^2}$$

(use integration by parts)

$$\mathcal{L}[t^n u(t)] = \frac{n!}{s^{n+1}}$$


(use induction)

Scaling
Time amplitude.

Time scaling: Expansion or Compression

$$x(t) \xrightarrow{\text{TS.}} y(t) = x(\alpha t) \quad \alpha \neq 0$$

~~defn~~ $|\alpha| > 1$ e.g. $\alpha = 2$, $|\alpha| < 1$ e.g. $\alpha = 0.5$

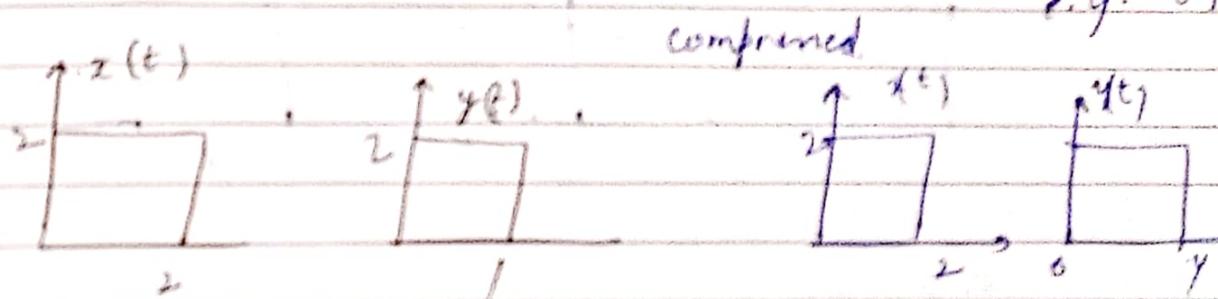

Amplitude Scaling

$$x(t) \xrightarrow{\text{AS.}} y(t) = \beta x(t)$$

$|\beta| > 1$; if $\beta = 2$ $|\beta| < 1$; if $\beta = 0.5$,




Shifting
Time amplitude.

Time shifting

$$x(t) \xrightarrow{\text{TS.}} y(t) = x(t+k)$$


$k > 0$ (+ve, advance)

$k < 0$ (-ve, delay)

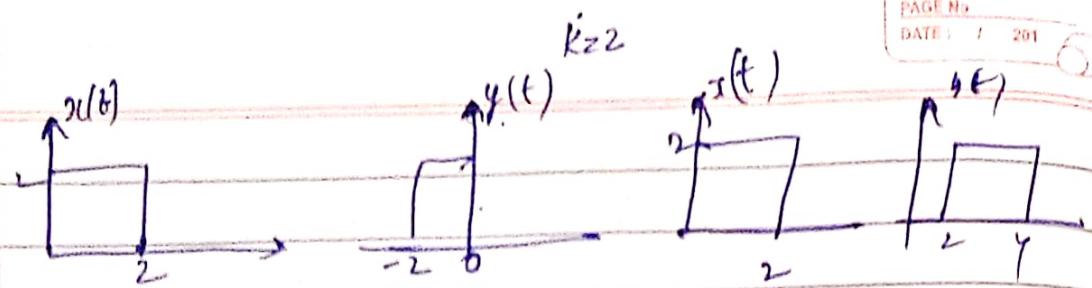

Amplitude Shifting -

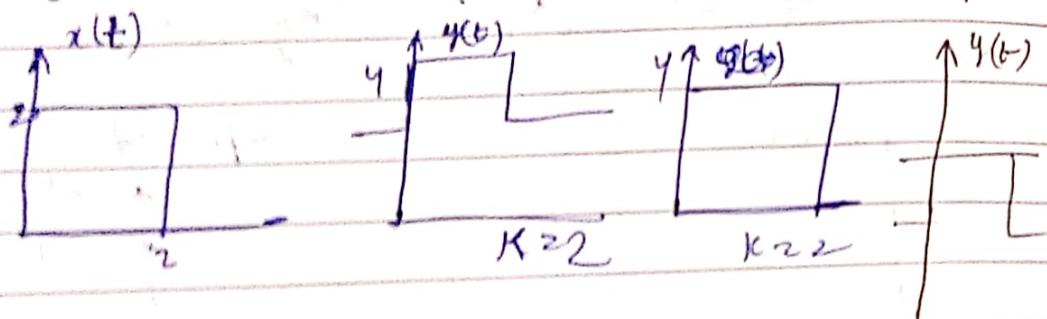
$$x(t) \xrightarrow{\text{A.S.}} y(t) = x(t) + k$$



Reversal

Time Reversal (sp. case of time scaling with $\alpha=-1$)
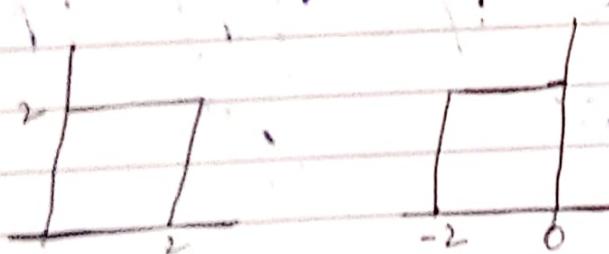
$$x(t) \xrightarrow{\text{T.R.}} y(t) = x(-t)$$




Shifting Theorem -

The Laplace transform of any function shifted or delayed by a time interval of ' a ' is e^{-as} times the transform of the function i.e.


$$\mathcal{L}[f(t-a)U(t-a)] = e^{-as}F(s).$$

$$f(t) = \sin \omega t$$

$$F(s) = \frac{\omega}{s^2 + \omega^2}$$

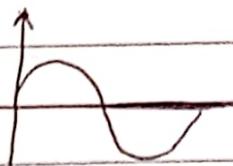


1)

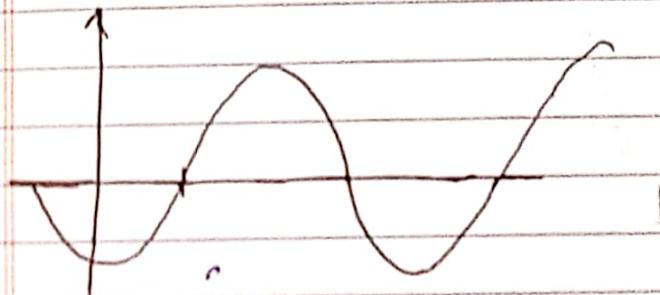

$$\begin{aligned} f(t-t_0) &= \sin \omega(t-t_0) \\ &= \omega \left[\sin \omega t \cos \omega t_0 - \cos \omega t \sin \omega t_0 \right] \\ &= \omega \cos \omega t_0 - s \sin \omega t_0 \end{aligned}$$


2)

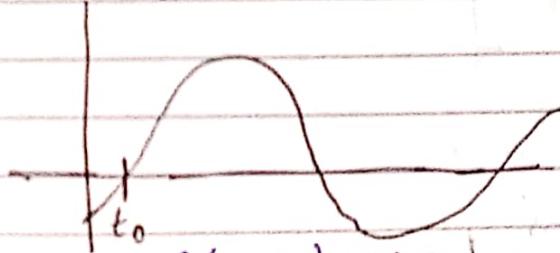

$$f(t-t_0)U(t) = \sin \omega(t-t_0)U(t).$$

$$F(s) = \frac{\omega \cos \omega t - s \sin \omega t}{s^2 + \omega^2}, \quad (\because L.T. \text{ is for } 0 < t < \infty)$$

3)

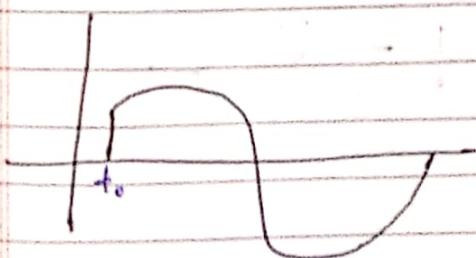


$$f(t)U(t-t_0) = \sin \omega t U(t-t_0).$$

$$f(t)U(t-t_0) = \int_{t_0}^t \sin \omega t' dt' = \frac{-1}{\omega} e^{-j\omega t} - e^{-j\omega t_0} U(t-t_0)$$

$$f(s) = e^{-t_0 s} [c_0 \cos \omega t_0 + s \sin \omega t_0]$$

$s^2 + \omega^2$

(4)

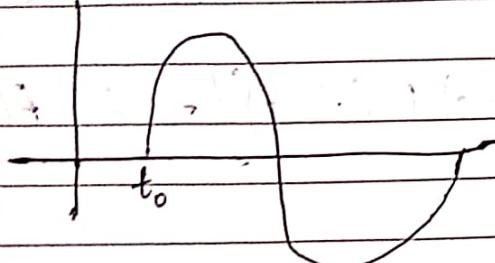

$$f(t-t_0) u(t-t_0)$$

$$= \sin \omega (t-t_0) u(t-t_0)$$

$$F(s) = e^{-t_0 s} \cdot \frac{1}{s^2 + \omega^2} [\sin \omega t]$$

$$= e^{-t_0 s} \cdot \frac{\omega}{s^2 + \omega^2}$$

$\int L[u(t)] = \frac{1}{s}$

singularity function $L[r(t)] = \frac{1}{s^2}$,
 $L[\delta(t)] = 1$


shifting theorem.

$$L[u(t-a)] = e^{-as} \frac{1}{s}$$

$$L[r(t-a)] = e^{-as} \frac{1}{s^2}$$

$$L[\delta(t-a)] = e^{-as} \cdot 1$$


Unit

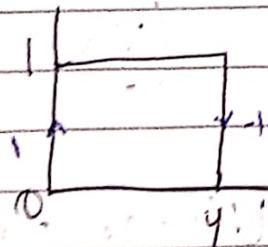

$$1 \cdot u(t) - 1 \cdot u(t-a)$$


$$u(t) - u(t-a)$$

$$= \frac{1}{s} - e^{-as} \frac{1}{s}$$

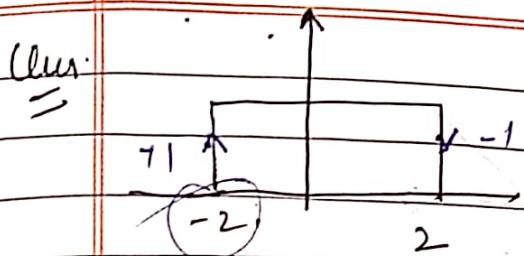


$$u(t+2) = v(t-2)$$

(3)

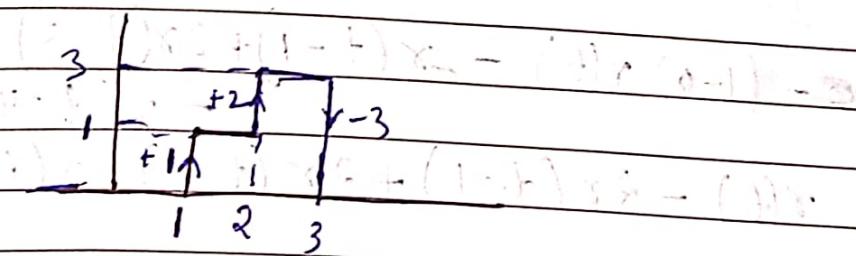


~~$u(t+3) = u(t+1) + 2u(t-2) + 3u(t-3)$~~

(4)

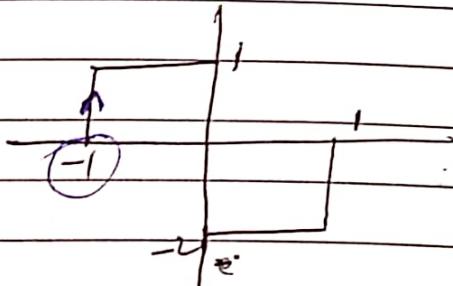

$$u(t+1) = 3u(t) + 2u(t-1)$$

(5)

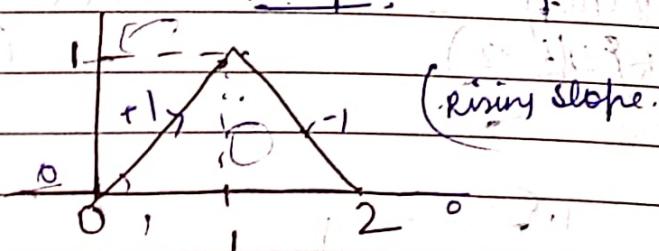


(rising slope), (falling slope).

(Present - Previous slope)

$$(1-0)r(t) + (-1-(+1))r(t-1) + (0-(-1))r(t-2)$$

$$r(t) - 2r(t-1) + 1r(t-2)$$

(6)

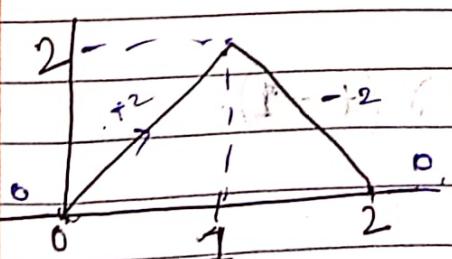


$$(-2-0)r(t-0) + (-2-(+2))r(t-2)$$

$$+ (0-(-2))$$


$$\approx 2r(t) - 4r(t-2) + 2r(t-2)$$

Cum
=

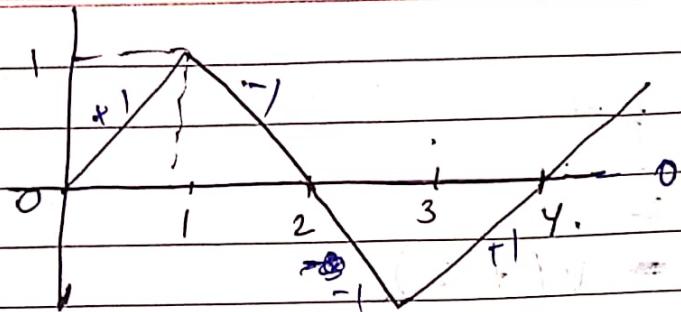


$$\begin{aligned}
 & \textcircled{a} (1-\delta) r(t) - 2\delta(t-1) + 2\delta(t-3) \\
 & = r(t) - 2r(t-1) + 2r(t-3) - r(t-4)
 \end{aligned}$$

Cum
=

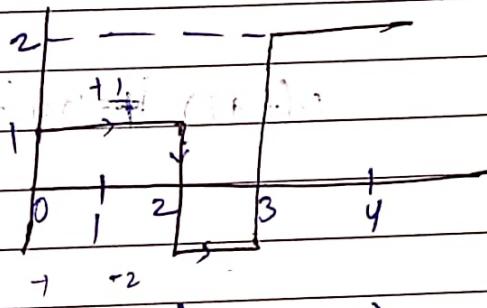

$$\begin{aligned}
 & \cancel{u(t) - 2u(t-1)} = u(t) - 3u(t-2) + 4u(t-3) \\
 & \cancel{u(t) - 2u(t-2)}.
 \end{aligned}$$




Cum
=

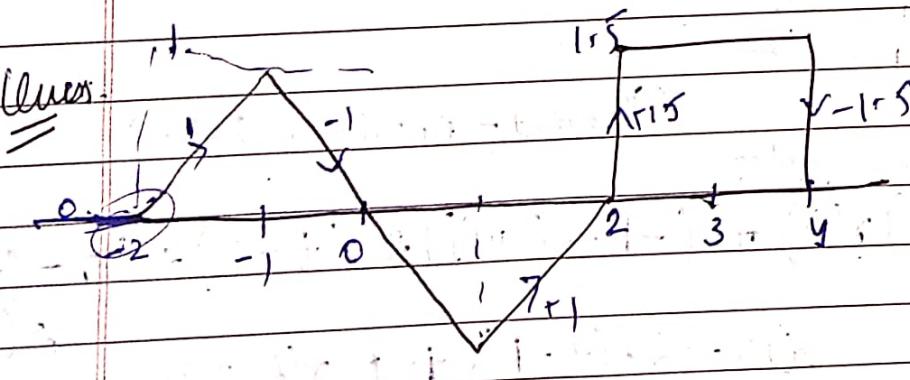

(1) (2) (3)

$$(1-\delta) r(t+2) - r(t-2)$$

Ques. Find L.T of

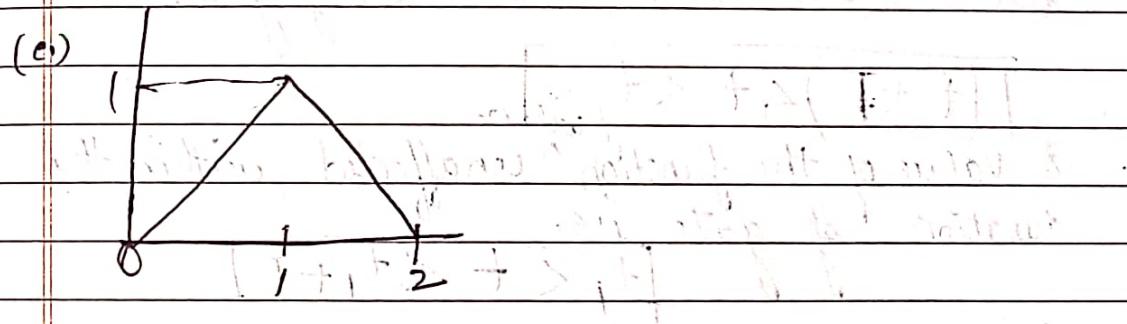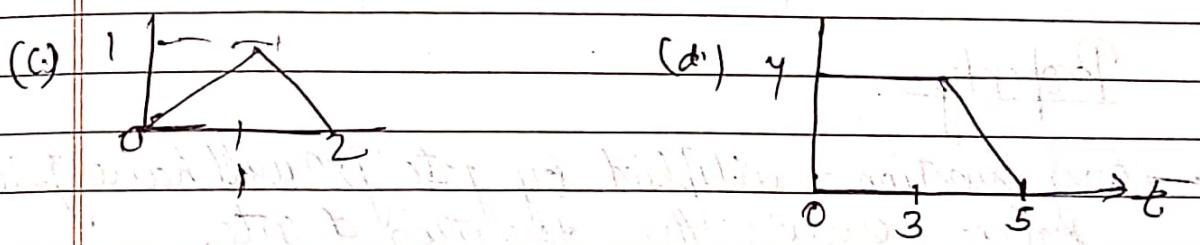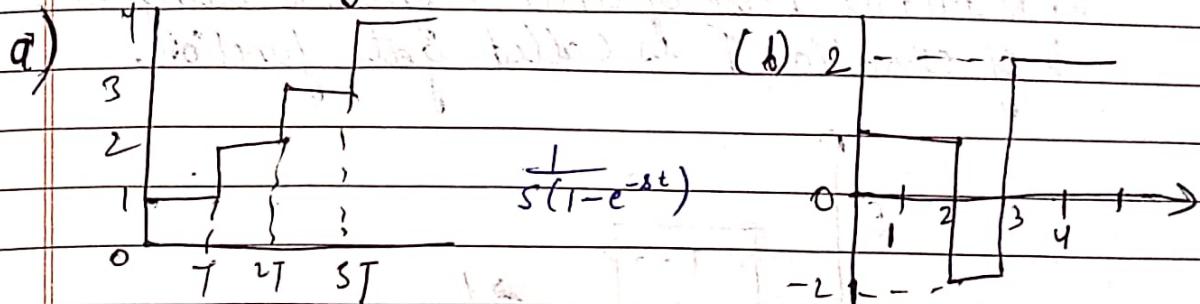

$$(1-s)-s^2 - (1-s)^2 = (1-s)(1-s-s^2)$$

$$(1-s)^2 - s^2 = (1-s)(1+s)$$


$$\frac{1-s}{s} - \frac{1}{s} = \frac{(1-s)(1+s)}{s}$$

Ans. $L.T = \frac{1-s}{s} - \frac{1}{s} = \frac{(1-s)(1+s)}{s}$

$$L.T = (1-s) - \frac{1}{s} + (1-s)\frac{1}{s} - \frac{1}{s} = (1-s) - \frac{1}{s} + (1-s) - \frac{1}{s} = (1-s) - \frac{2}{s}$$

Gate function

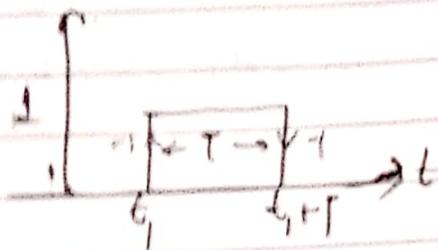A rectangular Pulse of unit height starting at $t=t_1$, & of duration T is called gate function.




Property

→ Any function multiplied by gate $f(t) \cdot h(t)$ will have zero value, outside the duration of gate.

$\int_{t_1}^{t_1+T} f(t) \cdot h(t) dt$ will be
the value of the function unaffected within the duration of gate i.e. $[t_1 < t < t_1 + T]$

$$\star G_{U_1}(T) = U(t - t_1) - U(t - t_1 - T)$$

$$\rightarrow G_U(T) = U(t) - U(t - T)$$

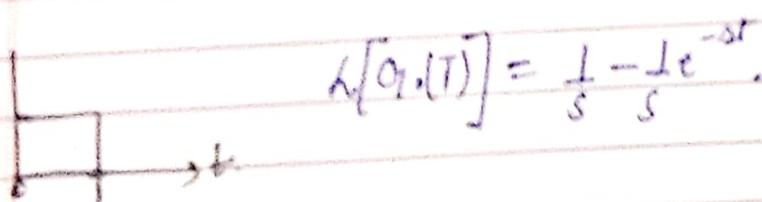

$$\mathcal{L}[G_U(t)] = \frac{1}{s} - \frac{1}{s} e^{-st}$$



Find L.T. of saw-tooth wave.

$$\text{Method I} - f(t) = \left(\frac{E-0}{T}\right) u(t) + \left(0 - \frac{E-0}{T}\right) \tau(t-T) - E u(t)$$

$$\Rightarrow \frac{E}{T} v(t) = \frac{E}{T} u(t-T) - E u(t-T).$$

$$= \frac{E}{T} \frac{1}{s^2} - \frac{E}{T} \frac{1}{s^2} e^{-Ts} - \frac{E}{s} e^{-Ts}.$$

Method II - Using gate function -

$$f(t) = \frac{E}{T} t \times g_{10}(T) = \frac{E}{T} t [v(t) - v(t-T)].$$


$$= L\left[\left(\frac{E}{T} t\right) v(t) - L\left[\left(\frac{E}{T} t\right) v(t-T)\right]\right].$$

$$= \frac{E}{T} \frac{1}{s^2} - L\left[\frac{E}{T} (t-T+\tau)\right] v(T-T)$$

$$= \frac{E}{Ts^2} - L\left[\frac{E}{T} ((t-T)+T)\right] v(t-T)$$

$$= \frac{E}{Ts^2} - L\frac{E}{T} (t-T)v(t-T) - L\frac{E}{T} T v(t-T),$$
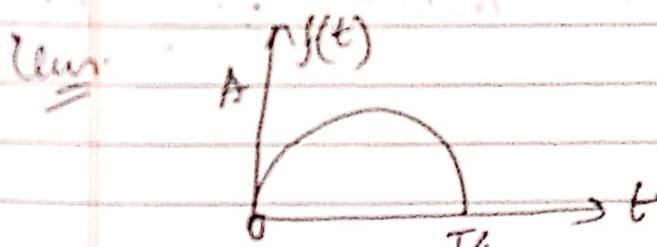
$$= \frac{E}{Ts^2} - \frac{E}{Ts^2} e^{-Ts} - \frac{E}{s} e^{-Ts},$$



$$\sin \omega t = \frac{\omega}{s + j\omega}$$

$$f(t) = A \sin \omega t \cdot g_{10}\left(\frac{T}{2}\right).$$

$$F(t) = A \sin\left(\frac{2\pi}{T} t\right) t [v(t) - v(t-\frac{T}{2})]$$


$$= A L\left[\sin\left(\frac{2\pi}{T} t\right) t \cdot v(t)\right] - A L\left[\frac{\sin\left(\frac{2\pi}{T} t\right) t}{T} \cdot v(t)\right]$$

$$= A \cdot \left(\frac{\pi i}{T}\right)^2 - A \cdot \sin\left[\frac{\pi i}{T} + \frac{\pi}{2}\right] U(t - \frac{T}{2})$$

$$= -A \left[\sin\left(\frac{\pi i}{T} - \frac{\pi}{2}\right) - 1 \right] U(t - \frac{T}{2}).$$

$$+ A \left[\sin\left(\frac{\pi i}{T} + \frac{\pi}{2}\right) \cdot U(t - \frac{T}{2}) \right]$$

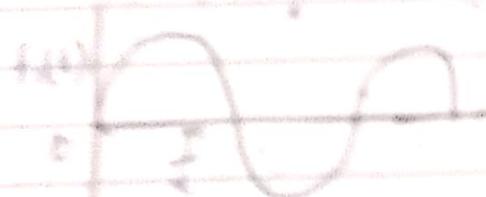
$$\frac{A(\frac{\pi i}{T})^2}{T^2(\frac{\pi i}{T})^2} + \frac{A \cdot \frac{2\pi}{T}}{\sin^2(\frac{\pi i}{T})} e^{-\frac{i\pi}{2}}$$



$$f(t) = f_1(t) + f_2(t)$$


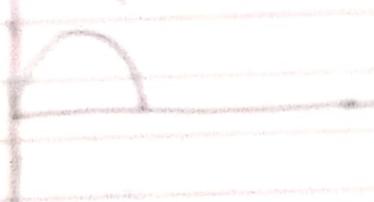
$$f_1(t) = A \cos(\omega t) + A \cos(\frac{\omega}{2}t)$$



$$f_2(t) = A \sin(\frac{\omega}{2}(t - \frac{T}{2})) U(t)$$




I.T. of periodic function =

The Laplace transform of a periodic function with period T

Ques A series RLC circuit

$$R = 3\Omega, L = 1H, C = 0.5F.$$

Obtain expression for current,

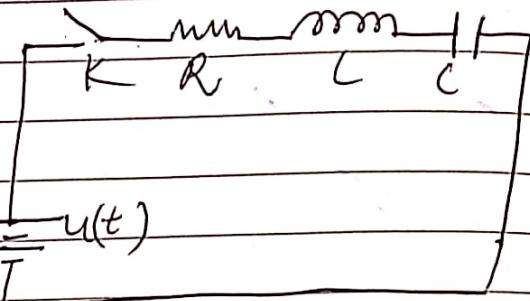

$$u(t) = L \frac{di}{dt} + \frac{1}{C} \int i(t) dt + R i(t).$$

$$\frac{1}{s} = L \left[s I(s) - i(0^-) \right] + \frac{1}{C} \left[\frac{I(s)}{s} + \frac{i(0^+)}{s} \right] + R I(s).$$

$$\frac{1}{s} = L s I(s) + \frac{1}{C} \frac{I(s)}{s} + R I(s).$$

$$\Rightarrow I(s) \left(Ls + \frac{1}{Cs} + R \right) = \frac{1}{s}$$

$$\Rightarrow I(s) = \frac{1}{\left(Ls + \frac{1}{Cs} + R \right)}$$


$$= \frac{1}{\left(1s + \frac{1}{0.5s} + 3 \right)}$$

$$I = R \\ V = sR$$

$$= \frac{1}{\left(\frac{0.5s^2 + 1 + 1.5s}{0.5s} \right)}$$

$$= \frac{0.5s}{0.5s^2 + 1 + 1.5s}$$
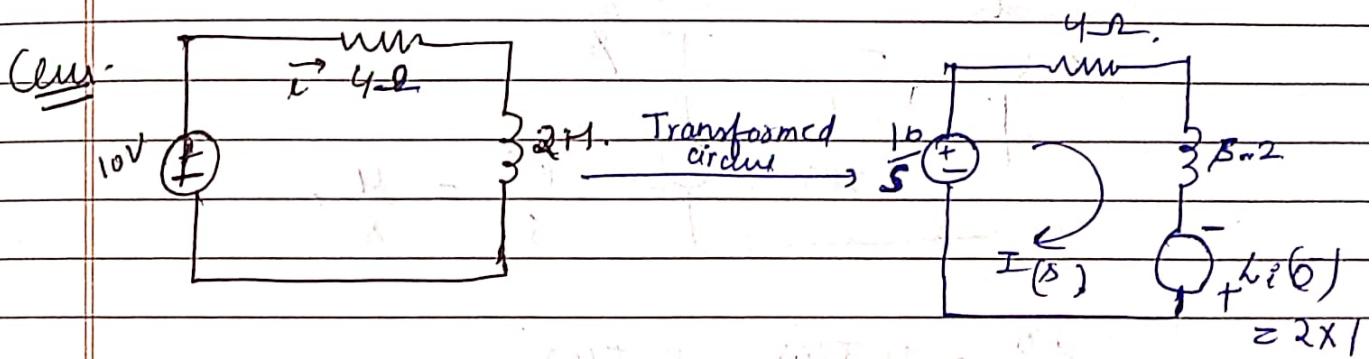
$$Z = \frac{0.5s}{(0.5s^2 + 1 + 1.5s)} \quad I(s) = \frac{1}{s+1} - \frac{1}{s+2}$$




$$\frac{10}{s} - 4I(s) - 2sI(s) + 2 = 0$$

$$I(s) = \frac{5+s}{s(s+2)} = \frac{k_1 + k_2}{s(s+2)}$$

$$= \frac{5}{2s} - \frac{3}{2(s+2)}$$

$$I(s) = \frac{5}{2s} - \frac{3}{2(s+2)} e^{-st}$$



Method-2

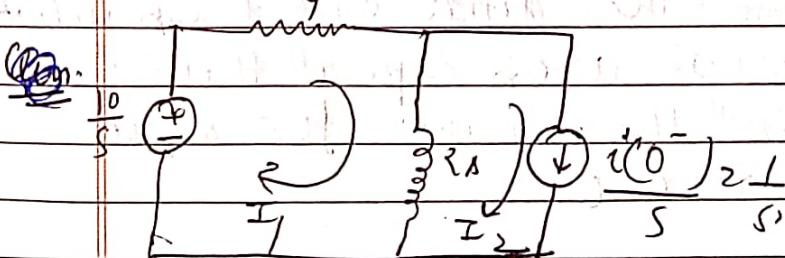

$$I_2(s) = \frac{1}{s} -$$


$$\frac{I_0}{s} = 4I(s) - 2s(I_1(s) - I_2(s)) = 0$$



$$I_1(s) = \frac{s+5}{s(s+2)}$$

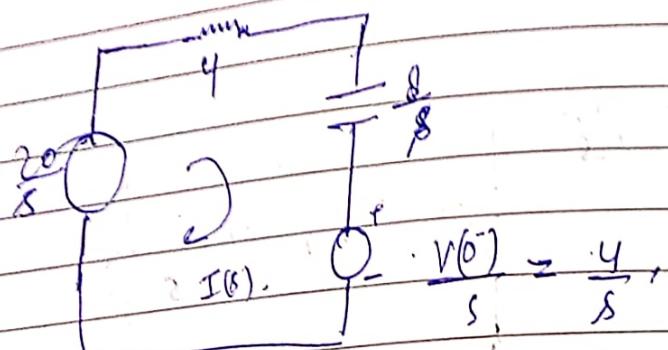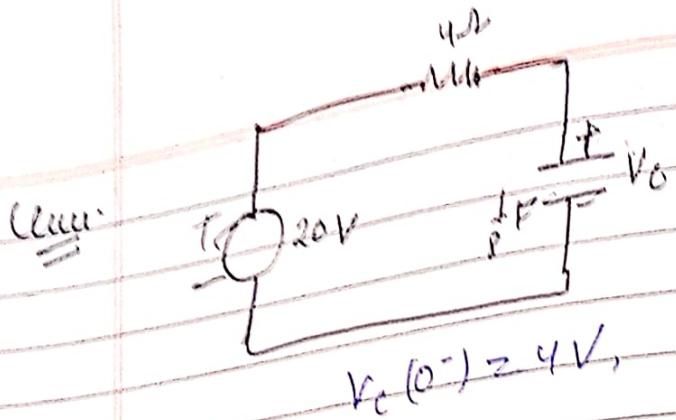

$$\frac{20}{8} - 4I(0^-) - \frac{8}{s}I(0^-),$$

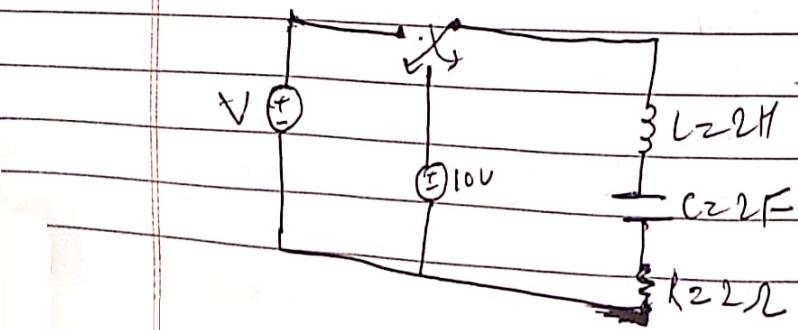(Ans) In series RLC ckt, the switch is moved from position 1 to 2 at $t=0$ initially it remain at position for along time; the initial current in inductor is $\frac{10}{2}A$ & voltage across cap. at that instant is $4V$. Find the expression for inductor current at $t=0$, (Ans)




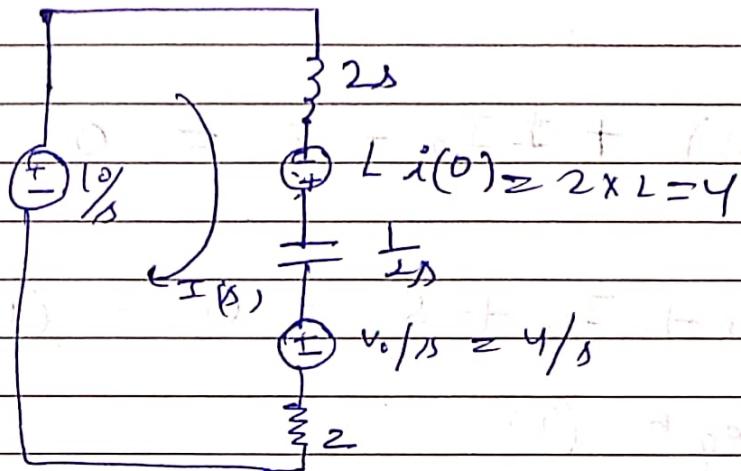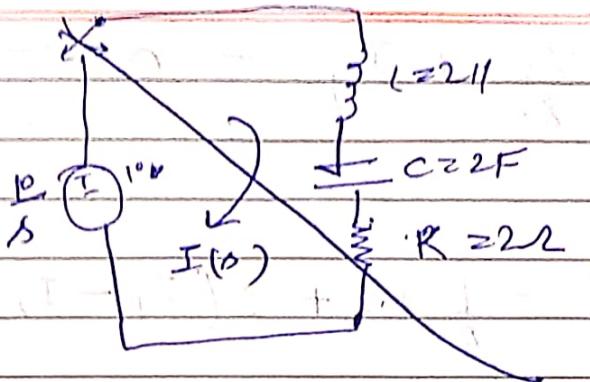

$$2) \frac{10}{s} - 2s I(s) + 4 - \frac{1}{2s} I(s) - \frac{4}{s} - 2 I(s) = 6$$

$$I(s) = \frac{12+8s}{4s^2+4s+1} = \frac{2(8+s)}{(s+\frac{1}{2})^2} = \frac{2\left(\frac{s+1}{2}\right) + 1}{\left(\frac{s+1}{2}\right)^2}$$

Determine voltage 'V'

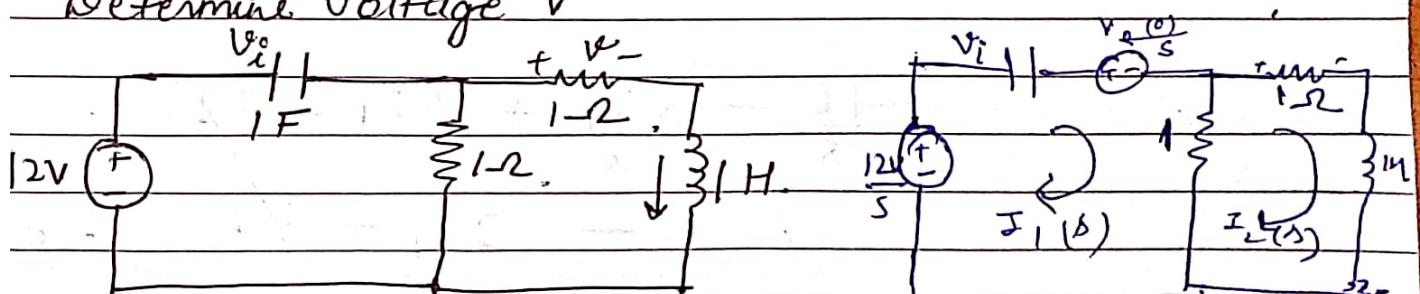

$$V_i(0) = 4V$$

$$i(0) = 2A.$$

$$\Rightarrow \frac{12}{8} - \frac{12}{8} + \frac{V_1}{8} + I_1 = 0 \quad (7)$$

$$-\frac{12}{8} + \frac{4}{8} - \frac{1}{8} I_1 + 1(I_1 - I_2) = 0 \quad (8)$$

In mesh 2,

$$1(I_2 - I_1) + \frac{1}{8} I_2 + \frac{8}{8} = 0 \quad (9)$$

$$\Rightarrow I_2 - I_1 + I_2 + \frac{8}{8} = 0 \quad (10)$$

Taking eqⁿ (10).

$$- \frac{12}{8} + \frac{4}{8} - \left(\frac{1}{8} I_1 \right) + I_1 - I_2 = 0$$

$$\Rightarrow - \frac{12}{8} + \frac{4}{8} - \left(\frac{1}{8} I_1 \right) + I_1 - I_2 = 0$$

$$\times 8 \quad - \frac{12}{8} - \frac{I_1}{8} + I_1 - I_2 = 0 \quad (11)$$

$$-8 - \cancel{\frac{I_1}{8}} + I_1 + 2I_2 = 0$$

$$- \frac{16}{8} - \frac{2I_1}{8} + 2I_1 - 2I_2 = 0$$

$$-8 - I_1 + 2I_2 = 0$$

$$- \frac{16}{8} - \frac{2I_1}{8} - I_1 = 0$$

$$-\frac{16}{s} - \frac{2I_1}{s} - s + I_1 = 0$$

$$-16 - 2I_1 - s - I_1 = 0,$$

~~$$-\frac{16}{s} - \frac{2I_1}{s} = s$$~~

$$-16 - s - 3I_1 = 0$$

$$-3I_1 = 16 + s$$

$$I_1 = -\frac{16+s}{3}$$

$$\frac{12}{s} - \frac{1}{s} I_1(s) - \frac{4}{s} = 1(I_1(s) - I_2(s)) = 0$$

$$\left(\frac{1}{s} + 1\right) I_1(s) - I_2(s) = \frac{8}{s} \quad \textcircled{1}$$

$$-1(I_2(s) - I_1(s)) - 1I_2(s) - 5I_2(s) + 2 = 0,$$

$$I_1(s) - I_2(s) \quad (\cancel{2 \neq 8}) = -2 \quad \textcircled{2}$$


$$\Delta = \begin{vmatrix} \frac{1}{s} + 1 & -1 \\ 1 & -2-s \end{vmatrix} \quad \Delta_2 = \begin{vmatrix} \frac{1}{s} + 1 & \frac{8}{s} \\ 1 & -2 \end{vmatrix}$$

$$I_2(s) = \frac{\Delta_2}{\Delta} = \frac{2s+10}{s^2+2s+2}$$

$$V = 1 \times I_2(s) = \frac{2s+10}{s^2+2s+2} = 2 \sqrt{\frac{s+1}{(s+1)^2+1}} + 8 \sqrt{\frac{1}{(s+1)^2+1}}$$

$$v(t) = 2e^{-t} \cos t + 8e^{-t} \sin t$$

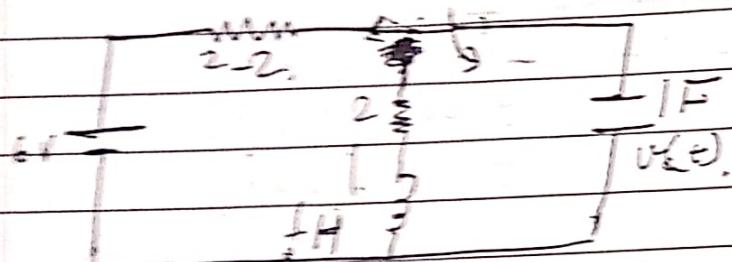Ques: In the circuit shown with S is in position for a long time & moved to position Q at $t=0$. find the voltage across the capacitor for $t \geq 0$.



$$\frac{1}{s} \left(\frac{1}{2s} + \frac{1}{s} \right) = \frac{1}{s}$$

$$-\frac{1}{2}s I(s) - I(s) - \frac{1}{s} - \frac{1}{s} I(s) = 0$$

~~$\frac{1}{2}s^2 + s + 1$~~

$$-I(s) - \left(\frac{1}{2}s + \frac{1}{s} + \frac{1}{s} \right) I(s) = 0$$

~~$\frac{s^2 + 12 + 2}{2s}$~~

$$-I(s) - \left(\frac{s^2 + 12 + 2}{2s} \right) I(s) = 0$$

$$-I(s) - \frac{s^2 + 12 + 2}{2s} I(s) = 0$$


$$-I(s) - \frac{s^2 + 12 + 2}{2s} I(s) = 0$$

$$-I(s) - s^2 I(s) - 12 I(s) = 0$$

$$I(s) = s^2 - 14$$

$$I(s) = -12$$

$$s^2 + 2s + 2$$

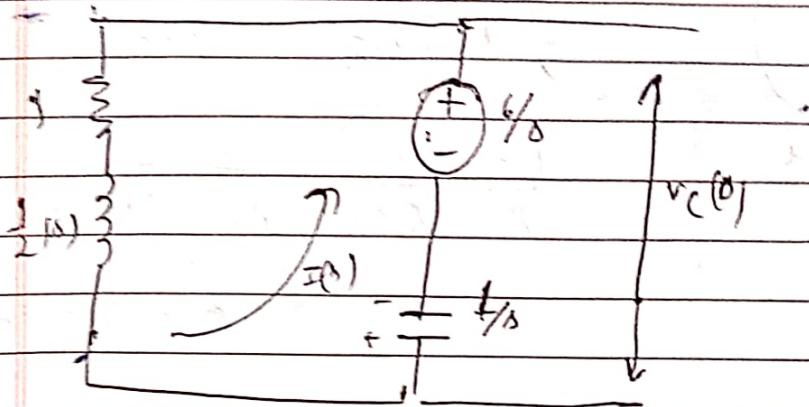

$$-\frac{1}{s} I(s) + \frac{6}{s} - v_c(s) = 0,$$



or

$$-\frac{1}{s} I(s) + \frac{6}{s} \geq v_c(s).$$


$$v_c(s) = \frac{6(s^2 + 2s + 12)}{s(s^2 + 2s + 12)} - 12s$$

30/11/22

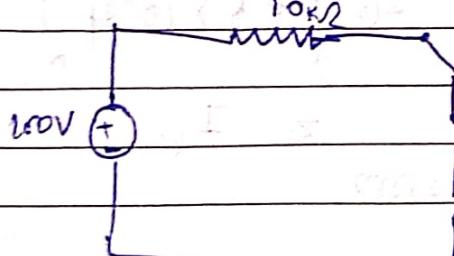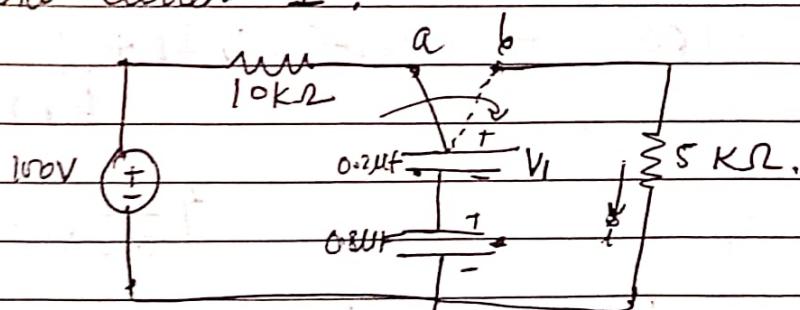Ques. In circuit shown, has been in position A for a long time at $t=0$, the switch is thrown to position B. Find current I .



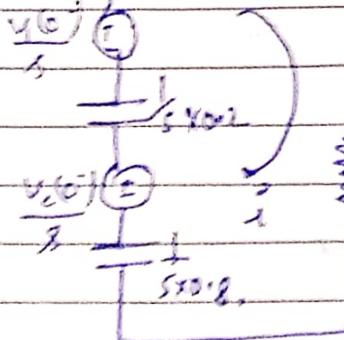Initial vol across both capacitors is 100V.



$$\frac{100}{5} + \frac{1}{5 \times 10^{-2}} i + \frac{1}{5 \times 10^{-2}} = 5i = 0$$

$$\frac{100}{5} + \frac{1}{5 \times 10^{-2} \times 10^2} i + \frac{1}{5 \times 10^{-2} \times 10^2} = 5i = 0$$

$$+ 5 \cancel{\frac{1}{100} i} = 0$$

~~Q1 & Q2~~

$$\frac{V_1(0^-)}{5} - 5 \times 10^3 I(0) - \frac{1}{5 \times 10^{-2} \times 10^{-6}} I(0) + \frac{V_2(0^-)}{5} - \frac{1}{5 \times 10^{-2} \times 10^{-6}} I(0)$$

$$\frac{1}{5} \left[V_1(0^-) + V_2(0^-) - 5 \times 10^3 I(0) - \frac{1}{0.5 \times 10^{-6}} I(0) - \frac{1}{0.2 \times 10^{-6}} I(0) \right] = 0$$

$$\frac{1}{5} \left[100 - 5 \times 10^3 I(0) - \frac{1}{0.5 \times 10^{-6}} I(0) - \frac{1}{0.2 \times 10^{-6}} I(0) \right] = 0$$

~~$$100 - 100 = - 5 \times 10^3 I(0) + \frac{1}{0.8 \times 10^{-6}} I(0)$$~~

~~cancel~~

$$4 \frac{1}{0.2 \times 10^{-6}} I(0) =$$

$$160 = I(0) \left(-5 \times 10^3 \right) + \frac{1}{0.8 \times 10^{-6}} + \frac{1}{0.2 \times 10^{-6}}$$

$$\frac{160}{(-5 \times 10^3) \times 10^{-6} + 6.25 \times 10^{-6}} = I(0)$$




$$I(s) = \frac{0.02}{s+10} V$$

PAGE NO.
DATE / / 201

$$I(\Delta) =$$




Ques: The ckt shown in fig. is initially under steady state condition the switch is moved from position ① to position ② at $t=0$. Find the current after switching.

=)

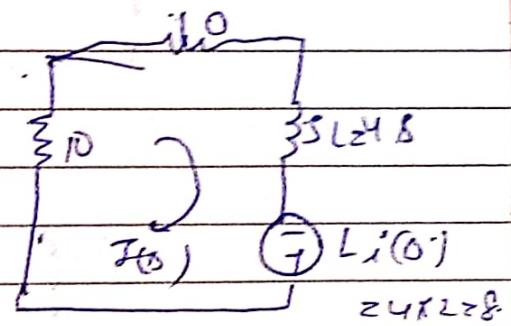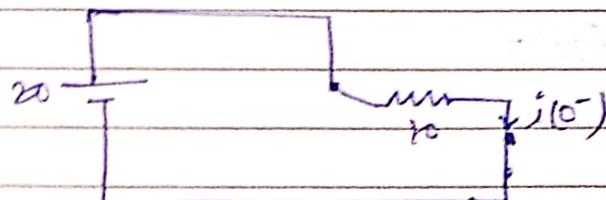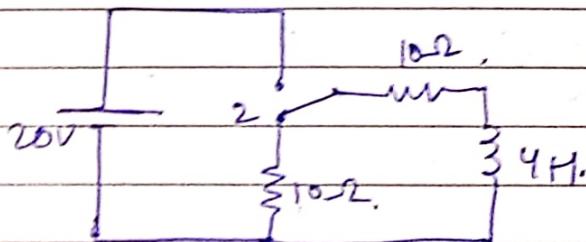

z)

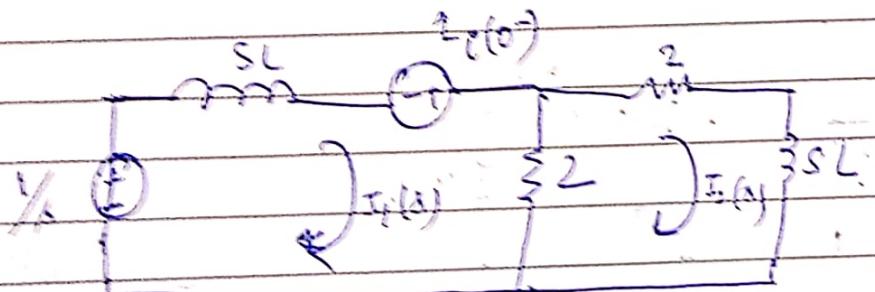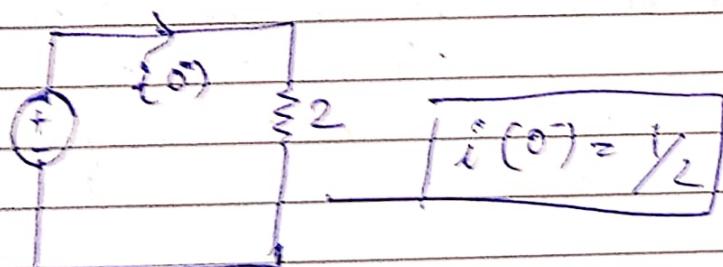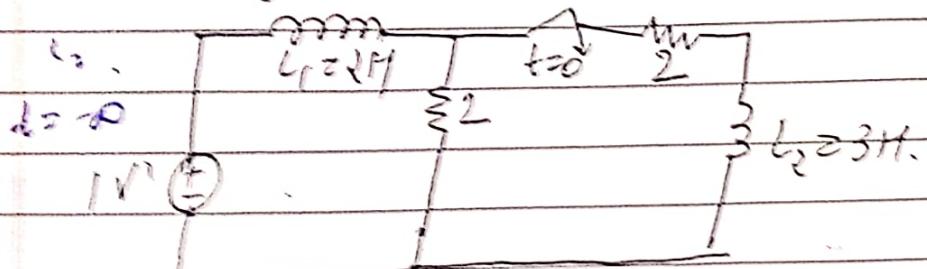Ques Determine the current in inductor L_2 is shown in fig after the switch is closed at $t = 0$. Assume the voltage is applied at $t = -\infty$.



$$I_2(t) = ?$$

$$\Rightarrow \frac{1}{L_2} = \frac{1}{3}$$

Ques Define initial value & final value theorem.

Ans- Initial value theorem states that if the Laplace transform of $f(t)$ is $F(s)$ & the first derivative of $f(t)$ is Laplace transform then the initial value of $f(t)$ is

$$f(0^+) = \lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} [s F(s)].$$

If time limit exists.

Final Value theorem states that

If the L.T. of $f(t)$ is $F(s)$ & if the s times the $F(s)$ is analytic on the imaginary axis & in right half of s -plane then, $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} [s F(s)]$.

Ques Verify initial value theorem.

(a) $f(t) = 5e^{-4t}$

$f(0) = 5e^0 = 5$

$F(s) = \frac{5}{s+4}$

$sF(s) = \frac{5s}{s+4}$

$$\boxed{\begin{aligned} f(0) &= sF(0) \\ \lim_{t \rightarrow 0} f(t) &\quad \lim_{s \rightarrow \infty} sF(s) \end{aligned}}$$

$$5e^{-4t} = \lim_{s \rightarrow \infty} \frac{5}{\frac{1+s}{s}}.$$

$s = 5$

H.P.

$$(b) f(t) = 2 - e^{st}$$

$$f(s) = \frac{2-1}{s+s+5}$$

$$f(s) = \frac{2(s+5) - s}{(s)(s+5)}$$

$$= \frac{2s + 10 - s}{(s)(s+5)} = \frac{s+10}{s(s+5)}$$

$$s f(s) = \frac{s(s-10)}{s(s-5)} = \frac{(s-10)}{(s-5)}$$

$$\lim_{s \rightarrow \infty} \frac{\left(1 - \frac{10}{s}\right)}{(s-5)} = 0$$

(Q) Verify final value theorem -

$$f(t) = 2 + e^{-3t} \cos 2t$$

$$f(s) = \frac{2}{s} + \frac{s+3}{(s+3)^2+4}$$

$$s f(s) = 2 + \frac{s^2 + 3s}{(s+3)^2 + 4}$$

$$\lim_{t \rightarrow \infty} [2 + e^{-3t} \cos 2t] = 2$$

$$\lim_{t \rightarrow \infty} \left[\frac{2 + \frac{s(s+3)}{(s+3)^2+4}}{1} \right] = \frac{2(s+3)^2 + 4 + s + 4}{(s+3)^2 + 4} = 2$$

(Ques) Verify final value theorem

$$\begin{aligned}f(t) &= 6(1 - e^{-t}), \\f(\infty) &= 6 - 6e^{-\infty}, \\&\approx \frac{6}{\cancel{e^{\infty}}} - \cancel{6e^{\infty}} \\&\approx \frac{6}{\infty} - \frac{6}{\infty+1}\end{aligned}$$


$$\begin{aligned}f(t) &= 6(1 - e^{-\infty}) \\(1-t \rightarrow \infty) &\approx 6.\end{aligned}$$

$$\approx \frac{6}{\infty} - \frac{6}{\infty+1}$$

$$\begin{aligned}f(s) &= \left(\frac{6s}{s} - \frac{6s}{s+1} \right) \\ \text{as } s \rightarrow 0 &\approx \left(6 - \frac{6s}{s+1} \right) \\ &\approx 6\left(\frac{6(s+1)}{s+1} \right) \\ &\approx 6.\end{aligned}$$

Unit - 5

Terminal pair or port.

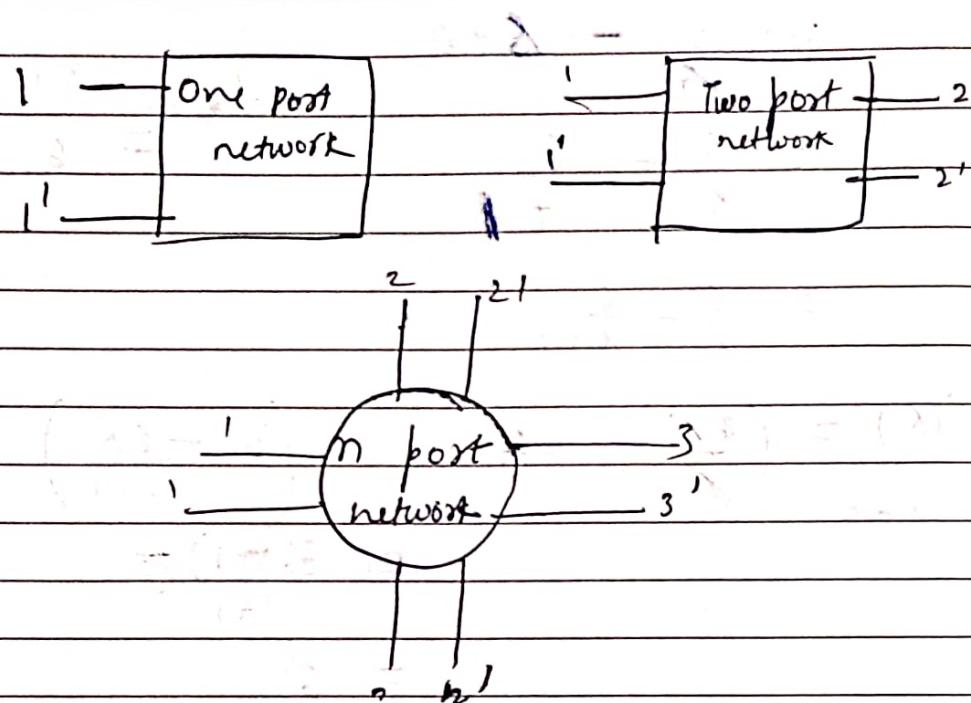

Network functions-

Transform Impedance

The transform impedance at a port has been defined as the ratio of voltage transform to current transform for a network in zero state (no initial condition).

$$Z(s) = \frac{V(s)}{I(s)}$$

Transform Admittance,

$$Y(s) = \frac{I(s)}{V(s)} = \frac{1}{Z(s)}$$

The voltage transform & current transform that define transfer impedance & admittance must relate to the same port

$$R + sL + \frac{1}{sC}$$


PAGE No.
DATE / / 201

for fig. 11', 22'


The impedance or admittance found at a given port is called driving point impedance or admittance.

→ Impedance is a common name which can be used for both impedance and admittance.

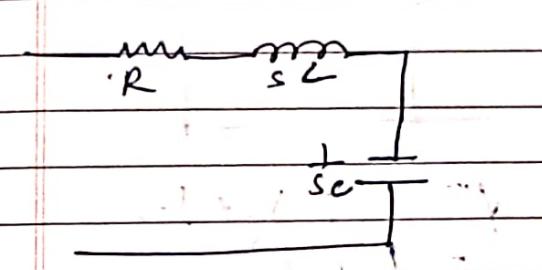Ques. Obtain the driving point impedance or transform impedance for the network shown.




$$Z(s) = R + sL + \frac{1}{sC}$$

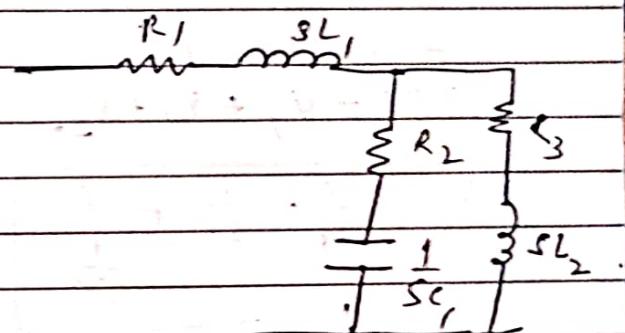

$$Z(s) = (R + sL_1) + \left(R_2 + \frac{1}{sC} \right)$$
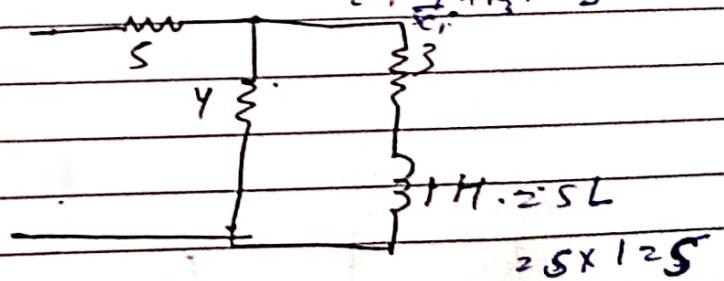
$$= (R + sL_1) + \left(R_2 + \frac{1}{sC} \cdot R_3 + sL_2 \right)$$



$$= s \times 1 = sL$$

$$(R + sL) + \frac{1}{sC}$$

$$R + sL + \frac{1}{sC}$$

$$Z(s) = s + (4/3 + s)$$


$$\left(s + \frac{4 \times 3 + s}{4 + 3 + s} \right) = 6 + s$$

$$Z(s) = \frac{s+4}{s+7}$$

Cases: Obtrain $Y(s)$.

In parallel

$$Y = Y_1 + Y_2$$

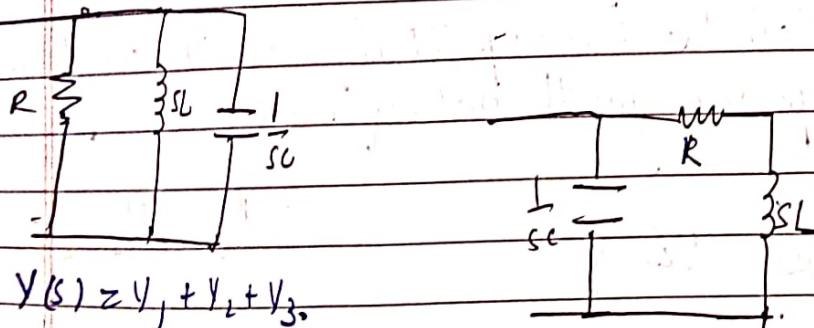

$$Y(s) = Y_1 + Y_2 + Y_3.$$

$$Y(s) = \frac{1}{R} + \frac{1}{sC} + \frac{1}{sL}$$


$$\begin{aligned} Y(s) &= Y_1 + Y_2 + Y_3. \\ &= \frac{1}{sC} + \frac{1}{(R+sL)} \end{aligned}$$

$$Y(s) = \frac{SL + R + s^2 RLC}{sCR}$$

\approx Resistor R .
 $(sCR = st)$

$$= \frac{RSC + (s^2 LC) + 1}{R + sL}$$

Cases:

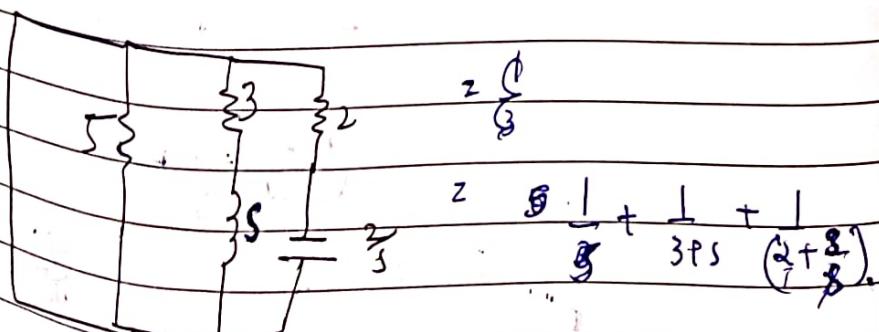

$$Z = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}}$$

$$\frac{2s^2}{s^2 + 2}$$

$$= \frac{1}{5} + \frac{1}{3+s} + \frac{2}{(4+s)}$$

$$= \frac{1}{5} + \frac{1}{(3+s)(4+s)}$$

$$= \frac{1}{5} + \frac{1}{3+s} + \frac{1}{\left(2 + \frac{2}{s}\right)}$$

$$= \frac{1+6+3s+0-s^2}{3+4s+s^2}$$

$$(s+3+s)\left(2-\frac{s}{s}\right)$$

07/12/22

Network function

The Ratio of Output to Input quantity \Rightarrow It may be either voltage or current or impedance or Admittance.

Voltage transfer Ratio-

$$G_{121}(s) = \frac{V_1(s)}{V_2(s)}$$

$$G_{112}(s) = \frac{V_1(s)}{V_2(s)}$$

Current transfer

$$\alpha_{21}(s) = \frac{I_2(s)}{I_1(s)}$$

$$\alpha_{12}(s) = \frac{I_1(s)}{I_2(s)}$$

3. Transfer Impedance -

$$Z_{21}(s) = \frac{V_2(s)}{I_1(s)}$$


$$Z_{12}(s) = \frac{V_1(s)}{I_2(s)}$$

4. Transfer Admittance -

$$Y_{12}(s) = \frac{I_1(s)}{V_2(s)}$$

$$Y_{21}(s) = \frac{I_2(s)}{V_1(s)}$$

Cum. Find voltage transfer function.

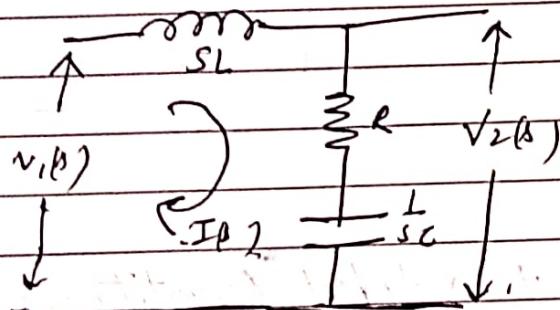


$$G_{21}(s) = \frac{V_2(s)}{V_1(s)} = \frac{I(s)(R + \frac{1}{SC})}{I(s)(R + SL + \frac{1}{SC})}$$


$$= \frac{SRC + 1}{SC}$$

$$= \frac{SRC + 1}{SRC + SLC + 1}$$

$$= \frac{SRC + 1}{SRC + S^2LC}$$

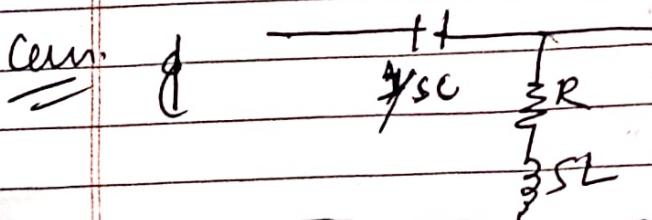
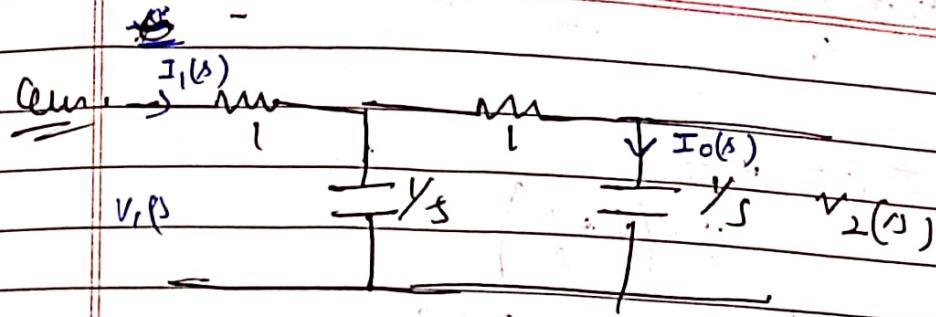
$$= \frac{\frac{1}{SC} + R + \frac{SL}{SC}}{1 + RSC + \frac{1}{SC} + S^2LC}$$



$$G_{12} = \frac{V_2(s)}{V_1(s)} =$$

$$Z(s) = \left(1 + \frac{1}{s}\right) // \left(1 + \frac{1}{s}\right) \Rightarrow \cancel{\left(\frac{s+1}{s}\right) // \left(\frac{s+1}{s}\right)}$$

$$\text{or } Z(s) = I_1(s) \cdot Z(s) = 1 + \frac{1}{s} // \left(1 + \frac{1}{s}\right)$$

$$= \left(1 + \frac{1}{s}\right) // \left(\frac{s+1}{s}\right)$$

$$= 1 + \frac{1}{s} \times \frac{s+1}{s}$$

$$\left(1 + \frac{1}{s}\right) \left(\frac{s+1}{s}\right)$$

$$Z = \frac{s+1}{s} * \frac{s+1}{s} = \frac{(s+1)^2}{s^2}$$

$$= \frac{s+1}{s} + \frac{s+1}{s} = \frac{8(s+1) + s(s+1)}{s^2}$$

$$Z = \frac{8^2 + 3s + 1}{s(s+2)}$$

$$Z = \frac{(s+1)^2}{(s+1)(s+2)}$$

$$Z = \frac{s+1}{2s}$$

$$V(s) = I(s) \cdot Z(s)$$

$$V(s) = I(s) \cdot \frac{s+1}{2s} : \frac{8^2 + 3s + 1}{s(s+2)}$$


$$V_2(s) = I_0(s) \times \frac{1}{s} = \frac{I_0 s}{s+2} \times \frac{1}{s}$$

$$I_0(s) = I_1(s) \times \frac{1}{s} \times \frac{1}{\frac{1}{s} + \left(\frac{1+1}{s} \right)}$$

$$\frac{2 I_1 s^2}{\left(\frac{1}{s} + \frac{s+1}{s} \right)} = \frac{I_1(s)}{1+s+1} \times \frac{I_1 s^2}{s+2}$$

$$g_{21}(s) = \frac{V_2(s)}{V_1(s)} = \frac{1}{s^2 + 3s + 1}$$

Circuit

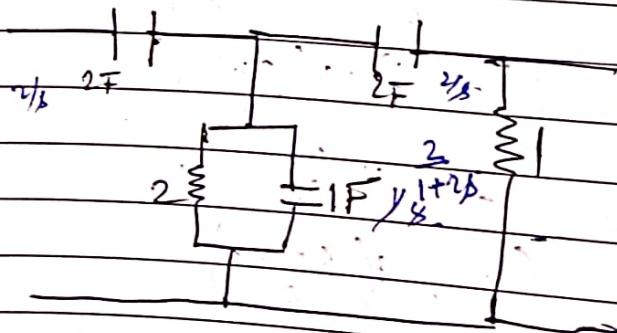

$$g_{21}(s) = ?$$

$$\frac{2+1}{2+1} = 3$$

$$Z(s) = \frac{2}{s} + 1 \left(\frac{2+1}{1+\frac{1}{s}} \right) \parallel \left(\frac{2+1}{s} \right)$$

$$= \frac{2}{s} \parallel \left(\frac{2s+1}{s} \right) \parallel \left(\frac{2+s}{s} \right)$$

$$= \frac{2}{s} \times \frac{2s+1}{s} \times \frac{s}{2+s}$$

$$= \frac{2(2s+1)(2+s)}{s^2 + 2s + 1}$$

$$= \frac{2(2s+1)(2+s)}{s^2 + 3s + 1}$$

38.

$$z(s) = \frac{s^2 + 12s + 1}{2s(4s^2 + 8s + 1)}.$$

PAGE No. _____
DATE / / 2014

$$= \frac{(4s+2)(2+s)}{3s(s^3)} = \frac{8s + 4s^2 + 4 + 2s}{3s \cdot s^3}.$$

$$= \frac{10s + 4s^2 + 4}{3s \cdot s^3}.$$

$$z(s) = \frac{1}{2s} + \frac{2}{1+2s} + 1/(2s + 1).$$

$$= \frac{1}{2s} + \frac{2}{1+2s} + 1/(2s + 1).$$

$$= \frac{1}{2s} + \left(\frac{\frac{2}{1+2s} \times \frac{2+s}{2s}}{\frac{2}{1+2s} + \frac{2+s}{2s}} \right)$$

$$= \frac{1}{2s} + \left(\frac{4+2s}{s+2s^2} \right) \cancel{(2s + (2+s)(1+2s))} \cancel{(1+2s)s}$$


$$= \frac{1}{2s} + \left(\frac{4+2s}{2s + 2 + 4s + s + 2s^2} \right)$$

$$= \frac{1}{2s} + \left(\frac{4+2s}{2s^2 + 2 + 7s} \right)$$

$$= \frac{1}{2s} + \frac{4+2s}{2s^2 + 2 + 7s}$$

$$= \frac{1}{2s} + \left(\frac{\frac{2}{1+2s} \times \frac{1+2s}{2s}}{\frac{2}{1+2s} + \frac{1+2s}{2s}} \right)$$

sXL

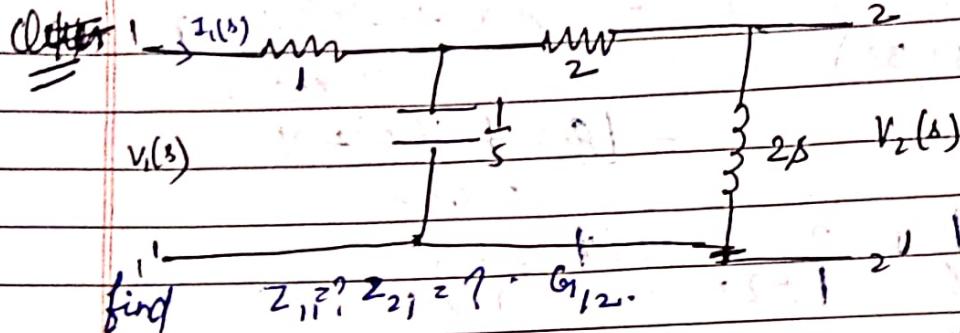 $\frac{1}{sC}$ 

$$\text{find } Z_{11}(s), Z_{21}(s) = ? \quad G_{12} = ?$$

$$I_C(s) = \frac{V_2(s)}{Z_{21}(s)}$$

Vol. across capacitor,

$$V_C(s) = V_2(s) + V_{2-2} = V_2(s) + 2I_2(s)$$

$$V_C(s) = V_2(s) + V_{2-2} = V_2(s) + 2I_2(s) = V_2(s) + 2 \cdot \frac{V_2(s)}{2s} = V_2(s) \left[1 + \frac{1}{s} \right]$$

$$I_C(s) = \frac{V_C(s)}{Z_{21}(s)} = \frac{V_2(s)(s+1)}{2s} = \frac{(s+1)V_2(s)}{2s}$$

$$I_1(s) = I_C(s) + I_L(s) = (s+1)V_2(s) + \frac{V_2(s)}{2s} = V_2(s) \left(s+1 + \frac{1}{s} \right)$$

$$= \left(\frac{2s^2 + 2s + 1}{2s} \right) V_2(s)$$

$$V_1(s) = V_C(s) + i \times I_1(s)$$

$$V_1(s) = V_2(s) \left(\frac{s+1}{s} \right) + \left[\frac{2s^2 + 2s + 1}{2s} \right] V_2(s) = V_2(s) \left(\frac{2s^2 + 4s + 1}{2s} \right)$$


$$= V_2(s) \left(\frac{s+1}{s} \right)$$

$$\begin{cases} Z_{11} = \frac{V_1(s)}{I_1(s)} \\ Z_{21}(s) = V_2(s) \end{cases}$$

$$G_{12}(s) = \frac{V_1(s)}{V_2(s)}$$


Ans.

Circuit

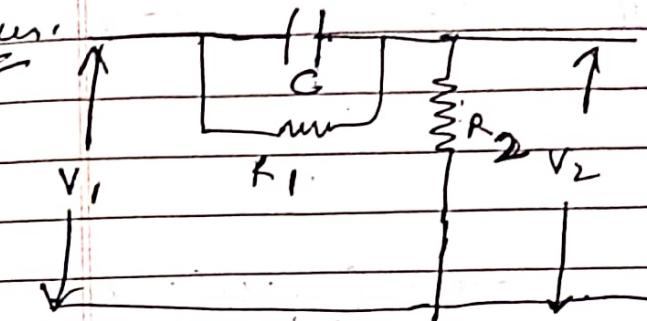

$$\text{find } G_{21}(s) = \frac{V_2(s)}{V_1(s)}$$

$$= \frac{I \cdot R_2}{I \cdot Z}$$

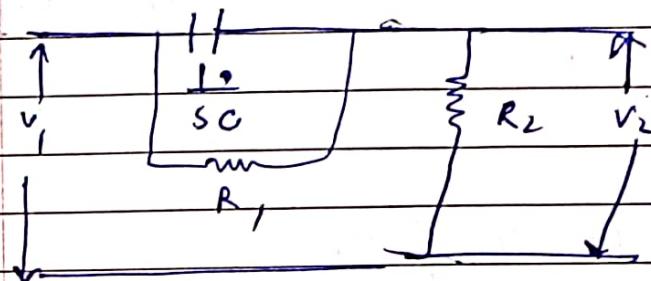

$$V_2 = V_1(s) R$$

$$Z = \left(\frac{1}{sC} + \frac{1}{R_1} \right)$$

$$Z = \left(\frac{R_1 + sC}{sC R_1} \right)$$

$$G_{21}(s) = \frac{s + \frac{1}{CR_1}}{s + \frac{1}{CR_1} + \frac{1}{CR_2}}$$


$$s + \frac{1}{CR_1} + \frac{1}{CR_2}$$

Poles & Zeros of Network function

$$T(s) = \frac{k(s-z_1)(s-z_2) \dots (s-z_m)}{(s-p_1)(s-p_2) \dots (s-p_n)}$$

Z → Zeros \times
P → Poles, \times

Pole-Zero Plot → imag.

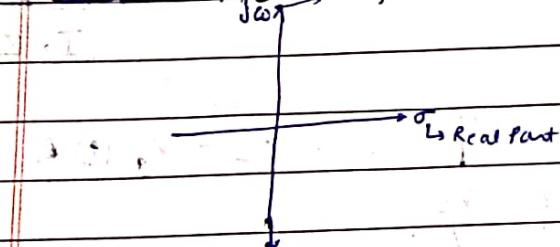

$$T(s) = \frac{(2s+4)(s+4)}{s(s+1)(s+3)}$$

Ques. Obtain Pole & Zero location for $f(x^n)$.

(i) $f(t) = e^{-st}$.

$$f(s) = \frac{1}{s + \sigma}$$

$$\sigma = 0$$

$$z = -\sigma$$


(ii) $f(t) = \cos \omega t$

$$f(s) = \frac{s}{s^2 + \omega^2}$$

$$z =$$

$$\sigma = 0$$

$$z = \pm j\omega$$

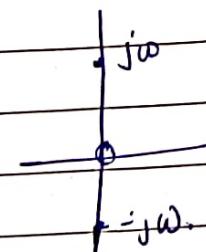


Examp

(i)

(iii) $f(t) = e^{-\sigma t} \cos \omega t$:

$$f(s) = \frac{s + \sigma}{\omega^2 + (s + \sigma)^2}$$

$$z = (-\sigma \pm j\omega)$$

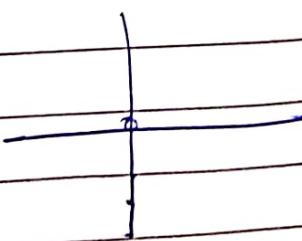

(iii)

(i)

(ii)

Necessary Conditions for Transfer Functions (with common factors in $N(s)$ & $D(s)$, cancelled).

The coefficients in the polynomials $N(s)$ & $D(s)$ of $T = N/D$ must be real & those for $D(s)$ must be positive.

Poles & zeroes must be conjugate if imaginary or complex.

The Real Part of poles must be negative or zero. If the real part is zero, then that pole must be simple. This includes the origin.

The polynomial $D(s)$ may not have any missing term between that of highest & lowest degrees, unless all even or all odd terms are missing.

The polynomial $N(s)$ may have terms missing, & some of the coefficients may be negative.

The degree of $N(s)$ may be as small as zero independent of the degree of $D(s)$.

for G_1 & α : The max. degree of $N(s)$ is equal to the degree of $D(s)$.

for Z and Y : The max. degree of $N(s)$ is equal to the degree of $D(s)$ plus one.

- Check whether given functions are suitable in representing the transfer functions or not.

$$(i) \alpha_{21}(s) = \frac{2s^2 + 5s + 1}{s + 7}$$

$$G_{21}(s) = \frac{3s+2}{5s^3 + 4s^2 + 1}$$

$$(iv) G_{11}(s) = \frac{2s^4 + 5}{3s^2 + 9s + 1}$$

$$Z_{21}(s) = \frac{1}{s^2 + 2s}$$

No; coefficient is missing in polynomial $D(s)$.


No; coefficient is missing in polynomial $D(s)$.

(iii) Yes, all cond. are satisfied.
(iv) Yes, , , , , , ,

PAGE No
DATE: / /

Ch-2

Two part network

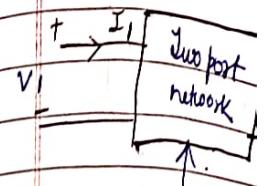

$$\text{Open circuit para} \\ \begin{cases} V_1 \\ V_2 \end{cases} = \begin{cases} z_1 \\ z_2 \end{cases}$$

$$V_1 = Z_{11} I_1 +$$

$$V = Z_{12} \cdot I_2$$

Car I-, $I_2 = 0$

$$\text{If driving point impedance: } Z_{II} = \frac{V_I}{I_I}$$

$$(ij) \cdot \gamma^{(i)} = \frac{15(1^3 + 2^3)^2 + 3ab^4}{a^4 + 8a^3b^2 + 6a^2b^4}$$

$$\frac{z_2}{z_1} = \frac{y_2}{x_1}$$

forward
transfer
Competence

Case II - I, P, A

$$R_{12} = \frac{V}{I}$$

~~Example~~

Example

$$\text{Ex) } 25x_1 = \frac{4x_1^4 + x_2^2 - 3x_3x_4}{x_1^3 + 2x_2^2 + 2x_3x_4}$$


$$E(B) = \frac{1+1+2}{2+1+1+1}$$

卷之三十一

111

Gini Verma

5-

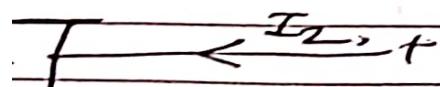


parameters (Z parameters).

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$+ Z_{12} I_2 = 0 \quad (1)$$

$$+ Z_{21} I_1 = 0 \quad (2)$$

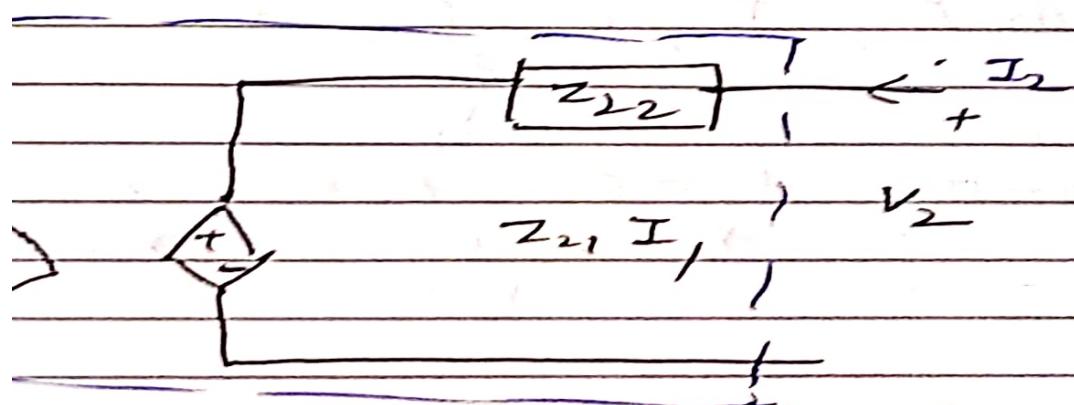

(output port open circuit).

$$I_2 = 0$$

$$I_1 = 0$$

(S/P Port is open circuit).

$$\frac{V_1}{I_2} \Big|_{I_1=0} \quad \text{reverse transfer impedance.}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

output driving point impedance.

15 | 12/22

γ Parameter $[Y] - (\text{short circuit parameter})$

$$I = [Y][V]$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Case

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$


Case I - ; $V_2 = 0$ Port 2 is shorted.

$$Y_{11} = \frac{I_1}{V_1}, \quad Y_{21} = \frac{I_2}{V_1}$$

Case II - $V_1 = 0$, Port 1 is shorted.

$$Y_{11} = \frac{I_1}{V_2}, \quad Y_{21} = \frac{I_2}{V_2}$$

Ques Find Z parameter -

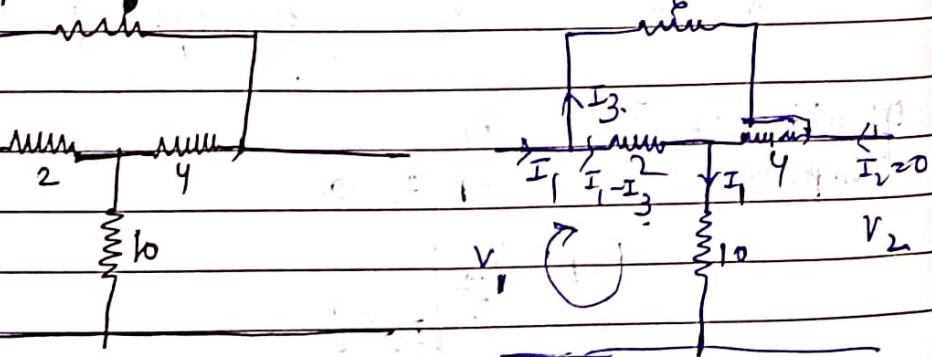

$$\Rightarrow -V_1 - 2(I_1 - I_3) - 10I_1 = 0 \quad \text{--- (1)}$$

$$-V_1 - 2I_1 + 2I_3 - 10I_1 = 0$$

$$\text{Re-arranging, } -V_1 - 12I_1 + 2I_3 = 0$$

$$V_1 = 4I_3 + 10I_1 \quad \text{--- (2)}$$

$$I_3 = I_1 \times \frac{2}{2 + (6 + 4)} = \frac{I_1}{6}$$

$$V_1 = 12I_1 - 2I_3 \quad \text{--- (1)}$$

$$V_1 = \frac{35}{3} I_1$$


$$V_2 = \frac{32}{3} I_1$$

$$\therefore Z_{11} = \frac{35}{3}$$

$$Z_{21} = \frac{32}{3}$$

~~$$III. I_1 = 0$$~~

~~$$\rightarrow V_1 - 2(I_1 - I_3) =$$~~

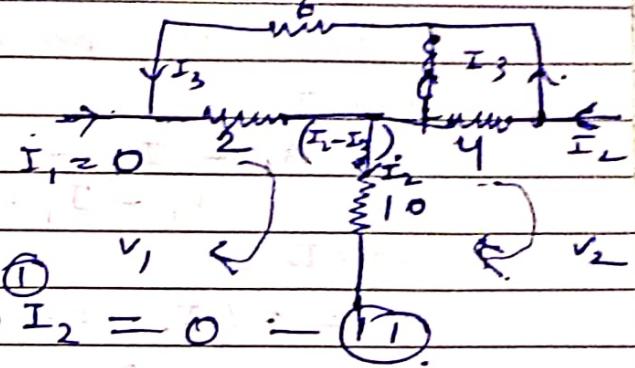

~~$$R_{23} = 0, I_3 = I_2 \times \frac{4}{12}$$~~

$$R + (6+4)$$

$$= I_2 \times \frac{4}{12}$$

$$I_3 = \frac{I_2}{3}$$

$$V_1 = 2I_3 + 10I_2$$


$$2I_2 + 10I_2$$

$$2I_2 + \frac{10I_2}{3}$$

$$2I_2 + \frac{30I_2}{3}$$

$$2 + \frac{32}{3} I_2$$

$$V_2$$

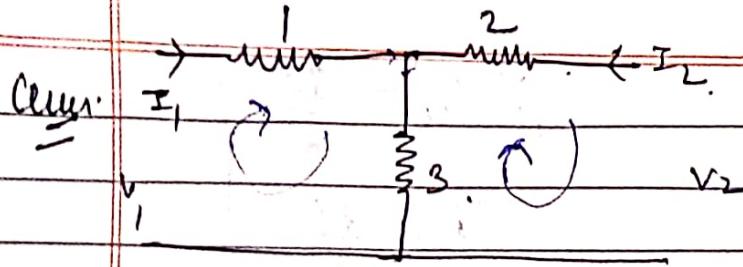

Find Z parameter.

case I -

$$V_1 - I_1 - 3(I_1 - I_2) = 0 \quad \text{--- (1)}$$

$$V_1 - I_1 - 3I_1 + 3I_2 = 0 \Rightarrow V_1 - 4I_1 + 3I_2 = 0$$

case II - $V_1 = 4I_1 + 3I_2 \quad \text{--- (2)}$

$$\therefore 3(I_2 - I_1) = 2I_2 + V_2 = 0 \quad \text{--- (1)}$$

$$-3I_2 + 3I_1 + 2I_2 + V_2 = 0$$

$$-5I_2 + 3I_1 + V_2 = 0$$

$$\therefore V_2 = 5I_2 + 3I_1 \quad \text{--- (2)}$$

Take I_1 as 0

$$V_1 = 3I_2$$

$$Z_{11} = V_1 / I_1$$

$$3I_2$$

$$I_1 = \frac{V_1}{3}$$

$$Z = V_1$$

$$Z_{11} = 4$$

$$Z_{22} = 5$$

Take I_2 as 0

$$V_1 = 4I_1$$

$$\text{Eq. } \frac{V_1}{4} = I_1$$

$$\text{from eq. } \textcircled{2}$$

$$I_2 = \frac{V_2 - 3I_1}{5}$$

Sub. I_2 in eq. (1)

$$V_1 = 4I_1 + 3I_2 \\ \approx 4I_1 + 3\left(\frac{V_2 - 3I_1}{5}\right)$$

$$V_1 = \frac{4I_1 + 3V_2 - 9I_1}{5}$$

$$= \frac{20I_1 + 3V_2 - 9I_1}{5}$$

$$V_1 = \frac{11I_1 + 3V_2}{5}$$

$$V_1 - 5V_1 = 11I_1 + 3V_2$$

$$I_1 = \frac{5}{11}V_1 - \frac{3}{11}V_2$$

$$Y_{11} \quad Y_{12}$$

write eqn ① in terms of ~~eqn ②~~

Put I_1 in eqn ②,

$$V_2 = 5I_2 + 3\left(\frac{5}{11}V_1 - \frac{3}{11}V_2\right)$$

$$V_2 = 5I_2 + \left(\frac{15}{11}V_1 - \frac{9}{11}V_2\right)$$

$$V_2 = 5I_2 + 3\left(V_2 - \frac{5}{3}I_2\right)$$

$\frac{11}{4}$

$$I_2 = -3I_1$$

$$\frac{5}{3}V_2$$

$$3$$